



PageNO.

1. 1 to 85 -----Mid Term
2. 86 to 196----- Final Term

MD IFTAKHAR KABIR SAKUR

25th BATCH

COMPUTER AND COMMUNICATION ENGINEERING

International Islamic University Chittagong

COURSE CODE OCE-1103

COURSE TITLE Basic Electrical Engineering

COURSE TEACHER:

Mohammed Jashim Uddin

Associate Professor in Electronic and Communication

Electrical part 1 Date: - 20.07.20

Basic concepts - Chapter - 1

Electrical circuit theory

System of unit :-

Quantity	Basic Unit	Symbol
<u>Length</u>	<u>meter</u>	<u>m</u>
<u>Mass</u>	<u>Kilogram</u>	<u>kg</u>
<u>Time</u>	<u>second</u>	<u>s</u>
<u>Electric current</u>	<u>ampere</u>	<u>A</u>
<u>Thermodynamic Temperature</u>	<u>Kelvin</u>	<u>K</u>
<u>Luminous intensity</u> (जलदास तीज)	<u>Candela</u>	<u>cd</u>

System of Units (2)

The derived units commonly used in electric circuit theory.

Quantity	Unit	Symbol
Electric Charge	Coulomb	C
Electric potential (वोल्ट्स फील्ड)	volt	V
Resistance (ओह्म)	ohm	Ω
Conductance (सिमेंस)	Siemens	S
Inductance (हेनरी)	henry	H
Capacitance (फैराड)	Farad	F
Frequency (हर्ट्ज)	Hertz	Hz

Quantity	Unit	Symbol
Force (बल)	Newton	N
Energy, work (ऊर्जा)	Joule	J
power	watt	W
Magnetic Flux (चुंबकीय प्रवाह)	weber	Wb
Magnetic Flux density (चुंबकीय प्रवाह घनत्व)	tesla	T

Capacitors

Change in electrical property of a system due to addition of which number of electrons is contained.

वैद्युत गुणधर्म में परिवर्तन को उत्पन्न करने वाले कणों की संख्या को इलेक्ट्रॉनों की संख्या कहते हैं।

Factor	prefix	Symbol
10^9	giga	G
10^6	mega	M
10^3	kilo	K
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p

Charge

Charge is an electrical property of the atomic particles of which matter consists, measured in Coulombs (C).

चार्ज शक्ति प्रकृति वैद्युतिक बल सम्बन्धित आवृत्तान्ति

কম্পন বৈদ্যুতিক ক্ষেত্র নিয়ে হাচ্চি। একে e দ্বারা প্রকাশ করা হয়।

⇒ The charge e on one electron is negative & equal in magnitude to $1.602 \times 10^{-19} \text{ C}$

which is called as electronic charge.

The charges that occur in nature are integral multiples of the electronic charge.

⇒ চার্জ e এর মান $-1.602 \times 10^{-19} \text{ C}$ মাত্র।

electronic charge বলা হয়। (এটা মূলতঃ একই)

কোন প্রকৃতিতেই যেকোনো মাত্রার চার্জগুলি বৈদ্যুতিক


চার্জের একক অবিচ্ছেদ্য।

Current (I)

- ~~DC (Direct current) is more dangerous than the AC~~
- AC is more dangerous than DC.
- A.C is five times more dangerous than D.C.

[Note]

Direction of Current & Electron:-

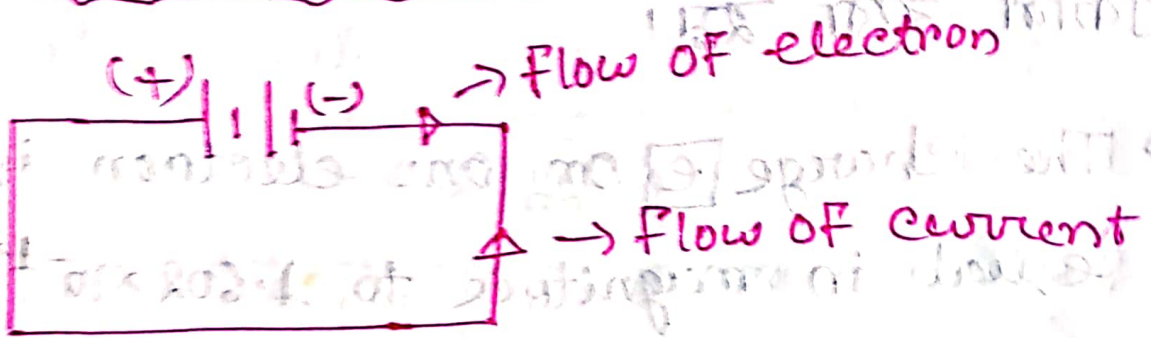

- (-) থেকে (+) এ গোল power gain
 - (+) থেকে (-) এ গোল power loss
- } Battery.

Measurement of current:-

(৩. বিদ্যুতের মাপ)

One ampere (amp) is that current which will cause

(1) throw

of (Direct current) is more dangerous than the AC

Alexander-Sadiku

(Current-1)

Electrical current:

$$i = \frac{dq}{dt}$$

$$F = \frac{2 \times 10^{-7} I^2 L}{s}$$

F = Force in Newton
 I = Current in Ampere
 L = parallel length in meter
 s = Distance of wire in meter

- The unit of ampere can be derived as


$$1 A = 1 C/s$$

প্রতি সেকেন্ডে 1C চার্জের আদান-প্রদানকে 1 অ্যাম্পিয়ার বলে।

□ A direct current (dc) is a current that remains constant with time.


□ An alternating current (AC) is a current that varies sinusoidally with time. (reverse direction)

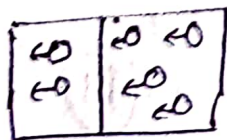□ The direction of current flow:- (Current-2)



(+)

positive ions

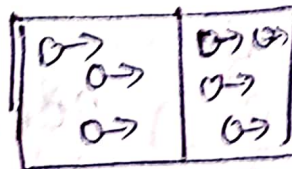

(-)

Negative ions

A conductor has a constant current of 5 A.

How many electrons pass a fixed point on the conductor in one minute?

Ans:- we know,

$$1 \text{ A} = 1 \text{ C/s.}$$

$$\therefore 5 \text{ A} = 5 \text{ C/s.} \quad \text{--- (i)}$$

$$1 \text{ min} = 60 \text{ s.}$$

$$1 \text{ min} = \frac{1 \text{ min}}{60} \quad \text{--- (ii)}$$

(ii) merging with (i) $\frac{\text{min}}{\text{electron}}$

$$5 \text{ A} = \frac{5 \text{ C}}{\frac{1 \text{ min}}{60}}$$

$$= \frac{5 \times 60 \text{ C}}{1 \text{ min}} = 300 \text{ C/min} \quad \text{--- (iii)}$$

$$1 \text{ electron} = 1.602 \times 10^{-19} \text{ C}$$

$$\therefore \frac{1}{1.602 \times 10^{-19}} = \frac{1 \text{ electron}}{1 \text{ C}}$$

$$\therefore \frac{300 \frac{\text{e}}{\text{min}}}{1.602 \times 10^{-19} \frac{\text{e}}{\text{electron}}}$$

$$= \frac{300}{1.602 \times 10^{-19}} \times \frac{\text{e}}{\text{min}} \times \frac{\text{min electron}}{\text{e C}}$$

$$= \frac{300}{1.602 \times 10^{-19}} \text{ electron/Coulomb min}$$

$$= 1.87 \times 10^{21} \text{ electrons/min}$$

voltage (V)

⇒ Voltage (potential difference) is the energy
विद्युत-वर्तक

required to move a unit charge through
an element, measured in volts (V).

कोला एकक चार्ज के इलेक्ट्रॉन कोला विद्युत

দ্বারা কামুহা পরিবর্তন কল্পনে তাকে ভোল্টেজ (V) বলে।

□ Mathematically,

$$V_{ab} = \frac{d(w)}{dq} \text{ volt}$$

→ w is energy in joules (J) and q is charge in ~~col~~ Coulomb (C)

⇒ Electric voltage, V_{ab} is always across the circuit element or between two points in a circuit.

(তড়িৎ বিল, V_{ab} অবসমম সাকিটে এত উদাদানে নমুণে সাকিটে দুইটি পয়েন্টের মাঝে থাকে)

→ $V_{ab} > 0$; that means the potential (বিল) of a is higher than potential of b.

→ $V_{ab} < 0$; that means the potential of a is lower than potential of b.

Power of Energy

power is the time rate of expending

Or absorbing energy,


measured in watts (w).

Mathematical expression:-

$$P = \frac{d(w)}{dt} = \frac{d(w)}{dq} \cdot \frac{dq}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt}$$


Note:

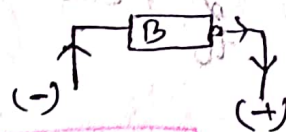(-) থেকে (+) এ হোল কারেন্ট power gain (অর্জন) করে।



(+) থেকে (-) এ হোল কারেন্ট power

loss (ক্ষয়) - করে।

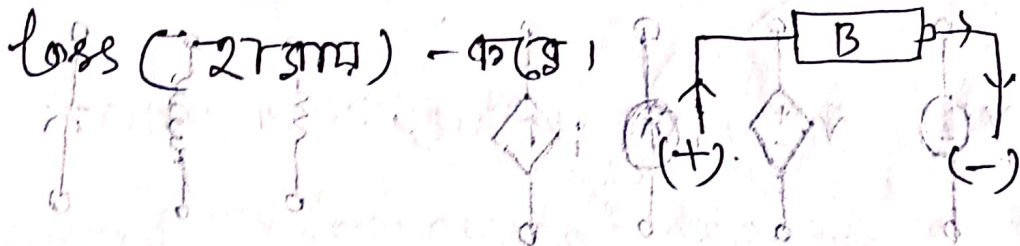

Power & Energy

(कमता व कार्य)

1] The law of Conservation of energy

$$\sum P = 0 \quad (\text{कार्य निरंतर है})$$


2] Energy is the capacity to do work, measured in joules (J)

(कार्य कराने की क्षमता को कार्य कहते हैं)
[एक एक शला कुल]

3] Mathematical expression

$$W = \int_{t_0}^{t_1} P dt = \int_{t_0}^{t_1} v i dt$$

Circuit elements

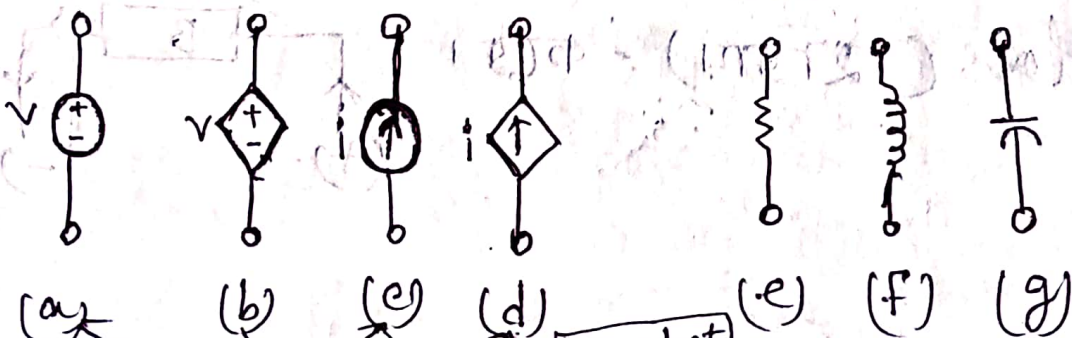

Independent

Active Elements


passive Elements

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

∴ Example 02 find current I

Obtain the voltage v in the branch shown

in Figure 2.1.1P for $i_2 = 1A$

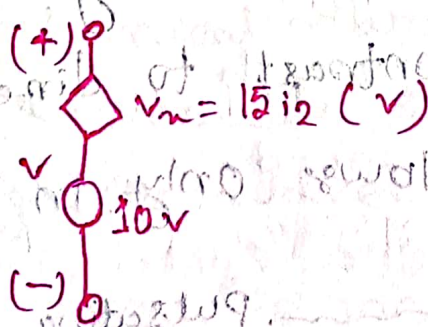

Ans: - voltage v is the sum of the current independent & dependent voltage source v_x .


Note that the Factor 15 multiplying the Control Current carries the units Ω .

Therefore, $v = 10 + 15i$
 $= 10 + 15(4) = 25 \text{ V}$

(Ans)

Alternating Current (AC) :-

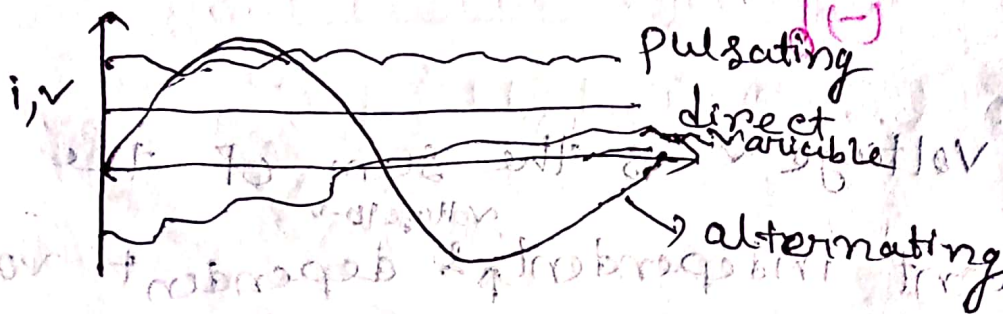Alternating Current (AC) is an electric current which periodically reverses direction, in contrast to direct current (DC) which flows only in one direction.



It actually delivered to businesses, residences.

Formula:-

1. $\omega = 2\pi f$

2. $f = \frac{1}{T}$

3. $\theta = \omega t$

Period:- A length of or proportion of time.

The interval of time between successive occurrences of the same state in an oscillatory or cyclic phenomenon, such as a mechanical vibration, an alternating current, a variable star, or an electromagnetic wave.

Cycle:- A cycle is one complete repetition of the sine wave pattern. It is produced by one complete revolution (360 degree) of the AC generator.

An oscillation or cycle, of the AC (Alternating Current) is defined as a single change from up to down to up, or as a change from positive to neg. to pos. this is what said to be as a cycle.

Cycle.

Frequency:-

Alternating Current (AC) Frequency is the number of cycles per second in an AC sine wave. Frequency is the rate at which current changes direction per second. Hertz (Hz) = One hertz is equal to one cycle per second.

Cycle = One complete wave of

AC or voltage.

Formula:-

$$i = I_m \sin \omega t$$

$$Or\ i = I_m \sin 2\pi f t$$

$i = I_m$ Current in ampere
(amp) (maximum)
 i = Current in Ampere
(amp) (minimum)
 ω = Frequency.

f = Force in Newton
(cycle/sec)

Math

* Sine have many angle when it value will reach $-\frac{1}{2}$ or -0.5 like 210° , 330° , 570° & so on.

Frequency:-

Audio Frequency range = $20\text{ Hz} - 20\text{ kHz}$

Radio Frequency range = $10\text{ kHz} - 300\text{ GHz}$
or $20\text{ kHz} - 300\text{ GHz}$

Other Frequencies

Low Frequency \rightarrow (10 to 1) km \rightarrow ~~30-300 MHz~~
(LW) \rightarrow (30 to 300) kHz

Medium Frequency \rightarrow (1 km to 100 m) \rightarrow 300 kHz to 3 MHz
(MF)

High Frequency \rightarrow (100 to 10) m \rightarrow (3-30) MHz
(HF)

Very High Frequency \rightarrow (10 to 1) m \rightarrow (30-300) MHz
(VHF)

Ultra High Frequency \rightarrow (1 m to 10 cm) \rightarrow 300 MHz to 3 GHz
(UHF)

Super High Frequency \rightarrow (10 cm to 1 cm) \rightarrow (3 to 30) GHz

Quantity of Electricity

The Quantity of electricity is represented by Coulomb.

Coulomb:- One Coulomb is that quantity of electricity which passes a reference

point on a conductor in 1 second when the conductor carries a steady current

1 amp. The relation between current & Coulomb is defined by the following equation:

$$Q = IT$$

where,

Q = Quantity of Electricity

I = Current

T = Time

Resistance:

The property of a conductor which requires the expenditure of energy by the moving electrons is called resistance.

The unit of resistance is Ohm defined.

Ohm:- One ohm is the resistance of a conductor in which energy is lost at the rate of 1 Joule/sec. (1 watt) when the current is 1 amp. The relation

between energy and resistance is

$$P = I^2 R$$

- P = Power (watt)
- R = Resistance (ohm)
- I = Current

Potential Differences:-

Potential Difference is the gain or loss of energy per unit quantity of electricity.

Electromotive Force:-

The rise in potential associated with battery generator or other device in which energy is imparted to move charges will, in what follows, be called an electromotive force (emf) denoted by "e".

Voltage Drop:- The fall in ~~resistance~~ potential associated with a resistance, in which energy is given up by the moving of positive charges, will be a voltage drop denoted by v .

All of the above definition units are volt.

Volt:- One volt is the potential difference between two points on a circuit when the energy involved in moving 1 Coulomb

From one point to the other in 1 Joule.
Potential difference is defined by the
equation,

$$E \text{ or } V = \frac{W}{Q}$$

where,
 $E = V =$ potential difference
 $W =$ Energy
 $Q =$ Quantity of
(Electricity)

Chapter - 13

Power & Energy Calculation:-

We know from potential difference

$$E \text{ or } V = \frac{W}{Q} \quad \text{--- (1)}$$

Also, definition from quantity of
electricity

$$Q = IT \quad \text{--- (2)}$$

From,

$$E = \frac{W}{IT}$$

$$\therefore W = EIT \quad \text{--- (3)}$$

$$\text{Or, } W = VIT \quad \text{--- (4)}$$

power is defined as the time rate of doing work,

$$P = \frac{W}{T} = \frac{VIT}{T} = VI$$

$$\therefore P = VI$$

If we know the resistance, power can also be calculated as,

$$R = \frac{P}{I^2}$$

$$\therefore P = I^2 R \quad \text{--- (6)}$$

P = power
I = ampere
R = resistance

$$= \left(\frac{P}{V}\right)^2 R$$

So,

$$\therefore R = \frac{P^2}{V^2} \cdot R$$

$$\text{or, } P = \frac{V^2}{R} \quad \text{--- (7)}$$

So, Summary of all equation be like

$$P = VI = I^2 R = \frac{V^2}{R}$$

Ohm's law:

We know,

$$P = VI \quad \text{--- (1)}$$

$$\text{Also, } P = I^2 R \quad \text{--- (2)}$$

From (1) & (2)

$$VI = I^2 R$$

$$\text{or, } V = IR \quad \text{--- (3)}$$

$$\text{or, } R = \frac{V}{I} \quad \text{--- (4)}$$

$$\text{or, } I = \frac{V}{R} \quad \text{--- (5)}$$

(3), (4) & (5) are all maintained mathematical representation of ohm's law.

It stated that,

The current in a metal conductor which is maintained at a constant temperature is proportional to the potential difference between its terminals. (প্রায়)

কোনো পরিবাহী দ্রব্যে যে ভোল্টের পার্থক্য রাখা হয় তাই প্রায় একই পরিমাণে প্রবাহিত হয়।
তদমাত্রই অনুপাতের সমান।


Series

Linear & Non-Linear Circuit

Series CKF :-

Kirchhoff's voltage law :-

A series circuit can be represents as,

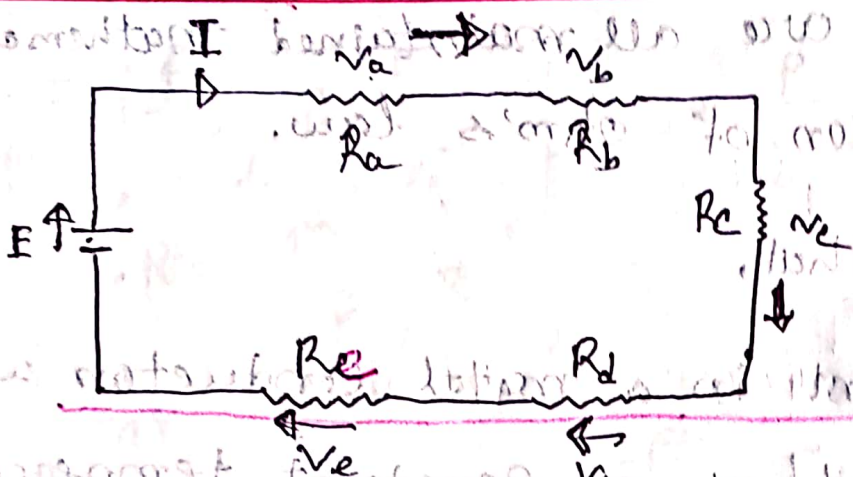

Let the energy gained by the electron passing through the battery be w_1 and let the energy lost in the various resistances be w_a, w_b, w_c, w_d, w_e respectively.

So, from the law of Conservation of energy,

Note:- The law of Conservation of energy states that energy can neither be created nor destroyed. - only converted from one form of energy to another. This means that a system always has the same amount of energy, unless,

something added from outside).

$$\therefore W = W_a + W_b + W_c + W_d + W_e \quad \text{--- (1)}$$

Dividing both side by the quantity of

electricity in Q ,

$$\frac{W}{Q} = \frac{W_a}{Q} + \frac{W_b}{Q} + \frac{W_c}{Q} + \frac{W_d}{Q} + \frac{W_e}{Q} \quad \text{--- (2)}$$

But $\frac{W}{Q}$ is the definition of the electro-
motive force of the battery,

and $\frac{W_a}{Q}$ is the voltage drop V_a across

the resistance, R_a and so on.

So, equation (2) can be written as,

$$E = V_a + V_b + V_c + V_d + V_e \quad \text{--- (3)}$$

If the current (I) flows through the
circuit then we can write,

$$V_a = IR_a \quad \text{and so on.}$$

So, (Kirchhoff's voltage law) $E = IR_a + IR_b + IR_c + IR_d + IR_e$ (4)

$$E = IR_a + IR_b + IR_c + IR_d + IR_e \quad (4)$$

This relationship is known as

"Kirchhoff's voltage law (KVL)"

Also,

Around any complete circuit the algebraic sum of the electromotive forces equal the algebraic sum of the voltage drops.

OR, can be written as,

$$\sum E_i = \sum V_i$$

Equivalent Resistance :- (সমতুল্য) (বোধ)

We know

$$E = IR_a + IR_b + IR_c + IR_d + IR_e$$

$$\text{Or, } E = I (R_a + R_b + R_c + R_d + R_e)$$

Sum. of resistance can be written as,


$$R_0 = R_a + R_b + R_c + R_d + R_e$$

So, R_0 = equivalent resistance of series circuit.

The equivalent resistance of a series circuit is the sum of the individual resistance.

Internal Resistance of emf source :-

(অতিরিক্ত চালক অন্তর্গত অভ্যন্তরীণ বোধ)

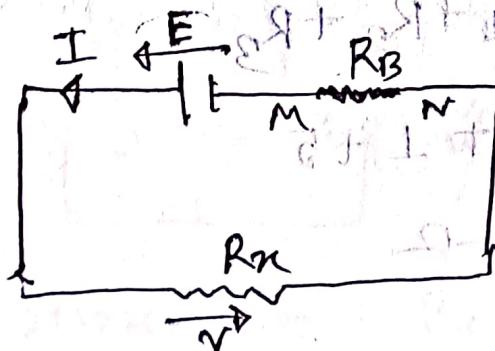

Applying KVL in CKF,

$$E = IR_B + IR_x \quad \text{--- (1)}$$


$$\text{ii, } E = IR_B + V \quad \text{--- (2)}$$

$$\text{iii, } V = E - IR_B \quad \text{--- (3)}$$

From, (1)

$$I = \frac{E}{(R_B + R_x)} \quad \text{--- (4)}$$

Example

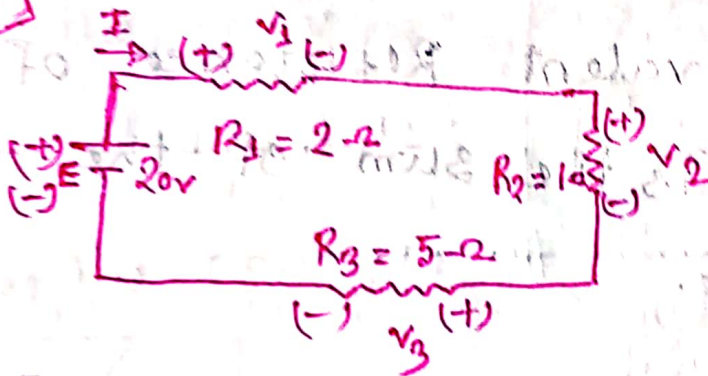


Q Find the total resistance for the series

($R_1 + R_2 + R_3$)

Ans :- $R_0 = R_1 + R_2 + R_3$

$$= 2 + 1 + 5$$

$$= 8\Omega$$

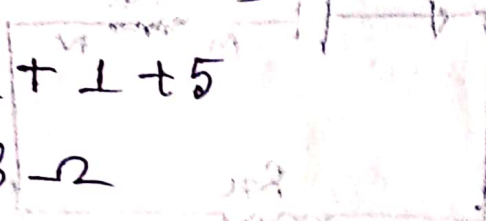

b) Calculate the Current I :-

$$I = \frac{E}{R_0} = \frac{20}{8} = \frac{5}{2} \text{ A} = 2.5 \text{ A}.$$

c) Determine the voltage V_1, V_2 & V_3 ,


$$V_1 = IR_1 = 2.5 \times 2 \text{ V} = 5 \text{ V}.$$

$$V_2 = IR_2 = 2.5 \times 1 = 2.5 \text{ V}.$$

$$V_3 = IR_3 = \frac{5}{2} \times 5 = \frac{25}{2} = 12.5 \text{ V}.$$

(Ans)

Voltage divider Rule (Boylstad)

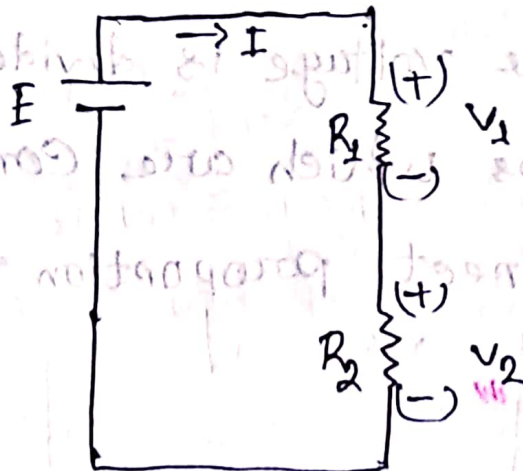

Total Resistance, $R_T = R_1 + R_2$

and, $I = \frac{E}{R_T}$ Similarly, $V_2 = IR_2$ (d)

Also, $V_1 = IR_1$

$V_2 = IR_2$
 $= \frac{E \cdot R_2}{R_T}$

$V_1 = \frac{E}{R_T} \cdot R_1$ positive voltage across it (e)

Or, $V_1 = \frac{R_1}{R_T} \cdot E$

Or, $V_2 = \frac{R_2}{R_T} \cdot E$

In note format we can write,

$V_n = \frac{R_n}{R_T} \cdot E$


→ Voltage divider rule

- R_n = The value of resistor
- R_T = Total Resistance
- E = Value of Energy

Voltage divider rule :-


The main concepts of this voltage divider

rule is "the voltage is divided between two resistors which are connected in series in direct proportion to their resistance."


 Symbol mean ground / Earth & potential



Circuit representation:-

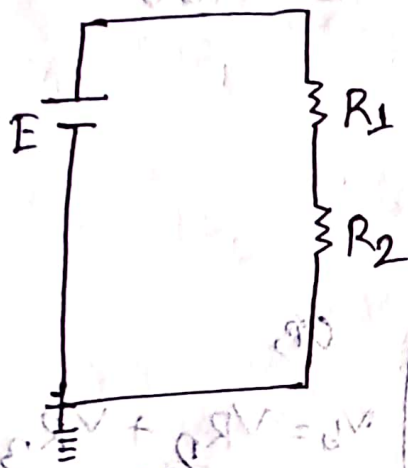


Or,

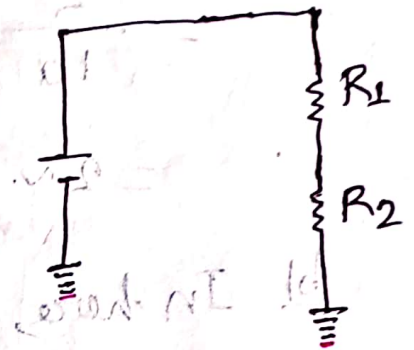

Example

For the network of following figure calculate:

- a) V_{ab}
- b) V_b
- c) V_c

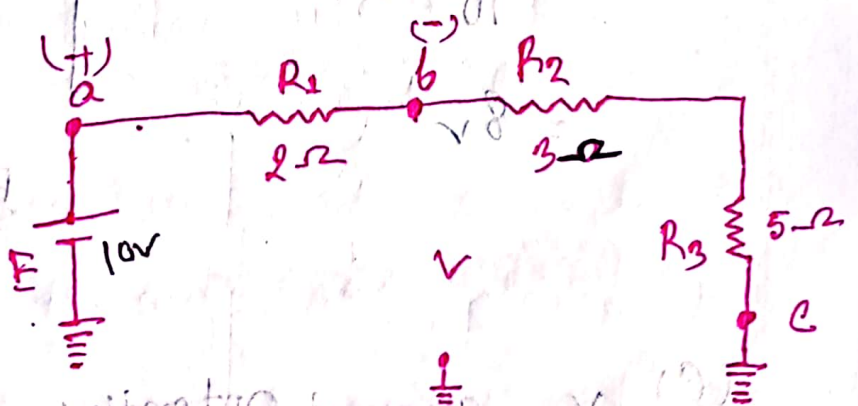

$I = 2A$

Solution:-

a)

$$V_{ab} = \frac{R_1}{R_T} \cdot E$$

$$= \frac{2}{10} \cdot 10$$

$$= 2 \text{ V}$$

$$R_T = (2 + 3 + 5) \Omega$$

$$= 10 \Omega$$

$R_1 = 2 \Omega$

$$E = 10 \text{ V}$$

b) In here,

$$V_b = \frac{R_2 + R_3}{R_T} \cdot E$$

$$= \frac{3 + 5}{10} \cdot 10$$

$$V_b = V_{R_2} + V_{R_3}$$

$$= \frac{R_2}{R_T} \cdot E + \frac{R_3}{R_T} \cdot E$$

$$= \frac{(R_2 + R_3)}{R_T} \cdot E$$

$$E = V_{ab} + V_b$$


$$V_b = E - V_{ab}$$

$$= 10 - 2$$


$$= 8 \text{ V}$$

c) $V_c =$ ground potential
 $= 0 \text{ V}$

(Ans)

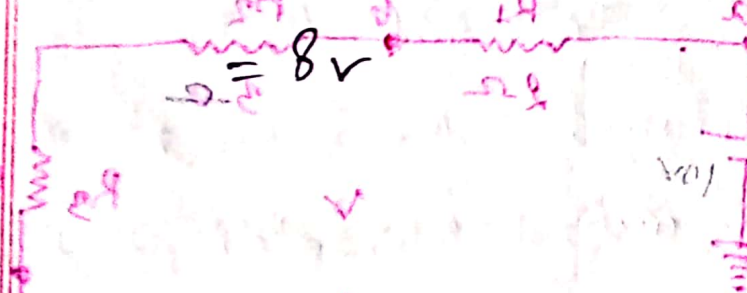

Q] Voltage sources in series:-

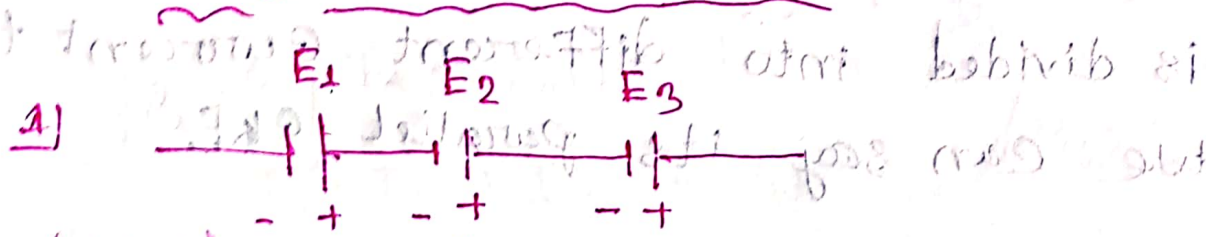


(Ans) $10V + 6V + 2V = 18V$

$$E_T = E_1 + E_2 + E_3$$

$$= (10 + 6 + 2)V$$

$$= 18V$$

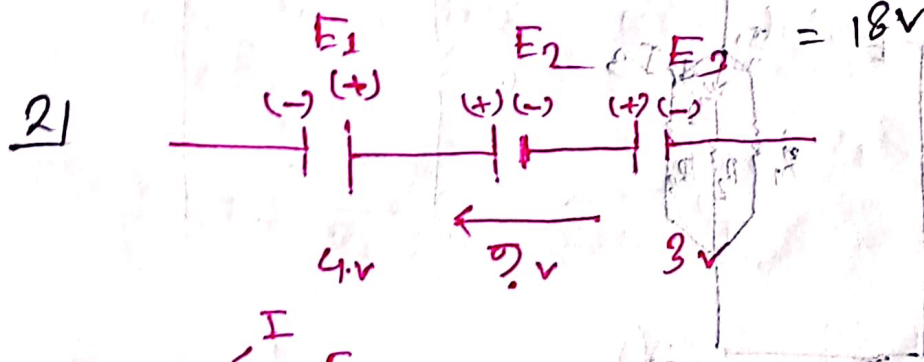

$$E_T = E_2 + E_3 - E_1$$

$$= 9 + 3 - 4$$

$$= 8V$$


Q] parallel circuit (समाकुल सर्किट):-

If two elements, branches or networks are connected in a common point this is called parallel circuit.

Or, If the total current of the circuit is divided into different current then we can say its parallel ckt.

Kirchhoff's Current Law (KCL)

A parallel circuit can be represent.

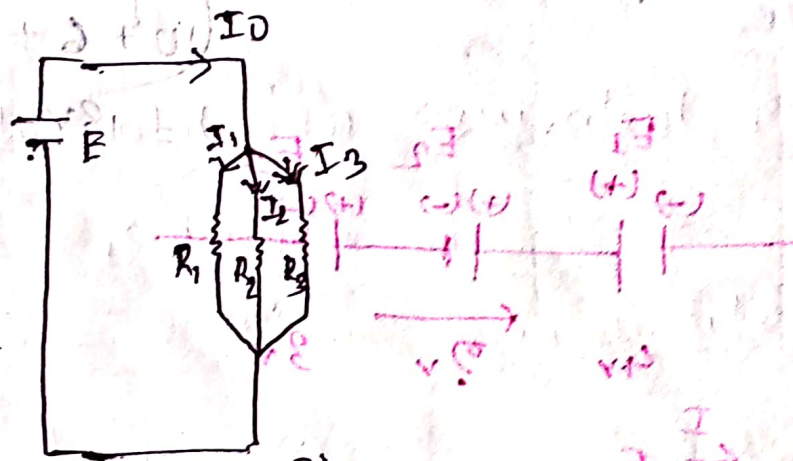

Ppe-3

So, Kirchhoff's current law can be stated that, at any junction point, the sum of the currents entering the point equals the sum of the currents leaving the point. In a symbolic manner,

$$\sum I_i = \sum I_o$$

where,

I_i = Incoming current

I_o = Outgoing "

So, According to KCL, From the picture we

Can write:-

$$I_0 = I_1 + I_2 + I_3 \quad \text{--- (1)}$$

If we apply KVL in Φ for individual branch, then we can write,

$$E = I_1 R_1$$

$$\text{or, } I_1 = \frac{E}{R_1} \quad \text{--- (2)}$$

$$\text{and, } E = I_2 R_2$$

$$\text{or, } I_2 = \frac{E}{R_2} \quad \text{--- (3)}$$

$$\text{and, } E = I_3 R_3$$


$$\text{or, } I_3 = \frac{E}{R_3} \quad \text{--- (4)}$$

putting the value of I_1, I_2 & I_3 in equation

(1)

$$I_0 = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3} \quad \text{--- (5)}$$

So, the pic can also be drawn as like:-

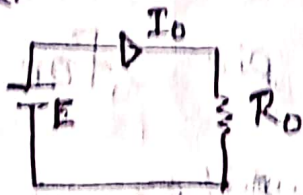

R_0 is the total or equivalent resistance of parallel resistance of pic-3

So, from [pic-4] we may write,

$$I_0 = \frac{E}{R_0} \quad \text{--- (6)}$$

From -5, we can write,

$$\frac{E}{R_0} = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

$$\text{or, } \frac{1}{R_0} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or, } \frac{1}{R_0} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}$$

$$\therefore R_0 = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$\left[\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

The resistance is called the **group** resistance

On the equivalent resistance of parallel circuit.

The rule of calculating parallel resistance can be stated that,

The equivalent resistance of a parallel circuit is the reciprocal sum of the individual resistance.

Conductance:- (परिवहन)

The reciprocal of a resistance is called Conductance. It is denoted

by G . and its unit is represent

mho (spell be of ohm) Also the

symbol of mho is Ω^{-1}

$$G = \frac{1}{R}$$

WIM

Show that if two resistances R_1 & R_2 are in parallel the equivalent resistance is given by,

$$R_0 = \frac{R_1 R_2}{R_1 + R_2}$$

Example

For the parallel network of following

Figure Calculate


a) Find R_T

b) Determine I_T

c) Calculate I_1 & I_2

d) Determine power for each position resistor.

e) Find G_1 & G_2 .

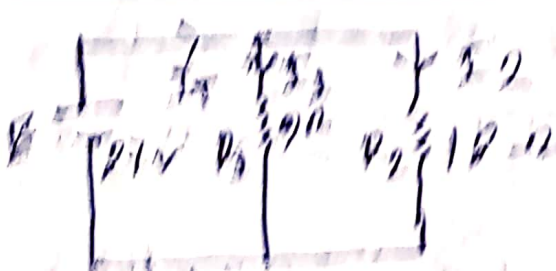

a) $R_T = \frac{P_1 P_2}{P_1 + P_2} = \frac{27 \times 18}{27 + 18} = \frac{27}{1.62} = 16.67 \Omega$

$= \frac{16.67}{27} = 6 \text{ A}$

b) we know,

$E = I_T R_T$ (Total resistance of circuit)


∴ $I_T = \frac{E}{R_T} = \frac{27}{6} = 4.5 \text{ A}$

c) we know, $V_1 = I_1 P_1$

∴ $I_1 = \frac{V_1}{P_1} = \frac{27}{18} = 1.5 \text{ A}$

$V_2 = I_2 P_2$

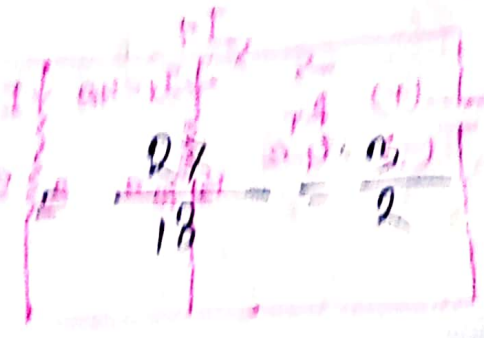∴ $I_2 = \frac{V_2}{P_2} = \frac{27}{18} = 1.5 \text{ A}$



d)

$$P_1 = V_1 I_1 = E I_1 = 27 \times 3 = 81 \text{ watt}$$

$$P_2 = V_2 I_2 = E I_2 = 27 \times 1.5 = 40.5 \text{ watt}$$

e)

$$G_1 = \frac{1}{R_1} = \frac{1}{9} = 0.11 \text{ mho}$$

$$G_2 = \frac{1}{R_2} = \frac{1}{18} = 0.05 \text{ mho}$$


f) Given the information provided in

Fig. Find

a) Determine R_3 b) Calculate E

c) Find I_T d) Find I_2

e) Determine P_2

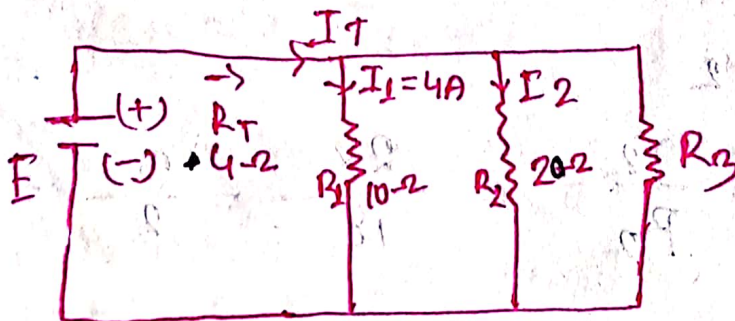

a

We know,

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or, } \frac{1}{4} = \frac{1}{10} + \frac{1}{20} + \frac{1}{R_3}$$

$$\text{or, } 0.25 = 0.1 + 0.05 + \frac{1}{R_3}$$

$$\text{or, } 0.25 - 0.1 - 0.05 = \frac{1}{R_3}$$

$$\text{or, } \frac{1}{R_3} = \frac{1}{20}$$

$$\text{or, } R_3 = 20 \Omega$$

(Ans)

$$\text{b) } E = V = I_1 R_1 = (4 \times 10) = 40 \text{ V}$$

d) we know,

$$V = I_2 R_2 \quad ; \quad \text{or, } I_2 = \frac{V}{R_2} = \frac{40}{20} = 2 \text{ A.}$$

$$\text{So, } I_T = I_1 + I_2$$

$$\text{c) } V = E = I_T R_T = 10 \times 4 = 40 \text{ V}$$


$$\text{or, } I_T = \frac{E}{R_T} = \frac{40}{4} = 10 \text{ A.}$$

$$\text{e) } P_2 = V_2 I_2 = 40 \times 2 = 80 \text{ watt}$$

we can also use,

$$\left[P = I^2 R_2 = \frac{V_2^2}{R_2} \right]$$

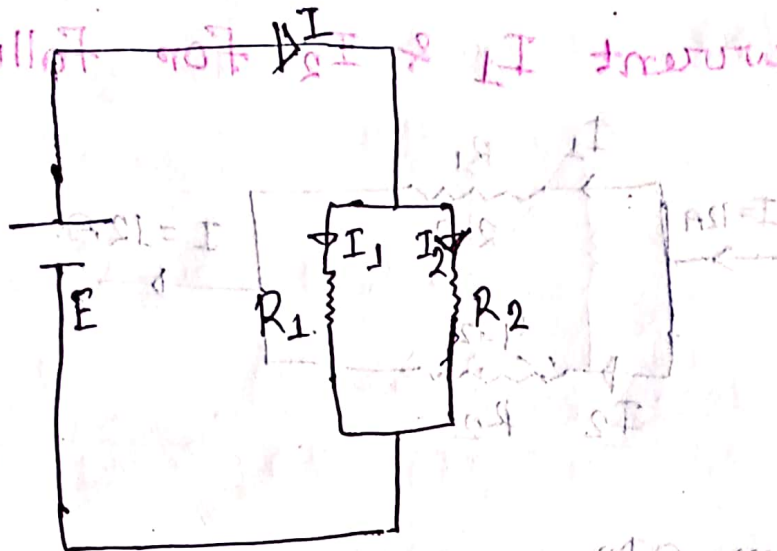For two resistance connected in parallel :-



In here,

$$I = \frac{E}{R_T}$$

& also, $R_T = \frac{R_1 R_2}{R_1 + R_2}$

and, $I_{R_1} = \frac{I \cdot R_2}{R_1 + R_2}$
 $I_{R_2} = \frac{I \cdot R_1}{R_1 + R_2}$

So, $I_1 = \frac{I \cdot R_2}{R_1 + R_2}$

Or, $I_1 = \frac{R_2 R_2}{R_1 + R_2} \cdot I$

$$= \frac{R_2 \cdot R_2}{R_1 + R_2} \cdot I$$

$$\therefore I_1 = \frac{R_2}{R_1 + R_2} \cdot I$$


$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I$$

$$= \frac{R_1 R_1}{R_1 + R_2} \cdot I$$

$$= \frac{R_1 R_1}{R_1 + R_2} \cdot I$$

$$\therefore I_2 = \frac{R_1}{R_1 + R_2} \cdot I$$

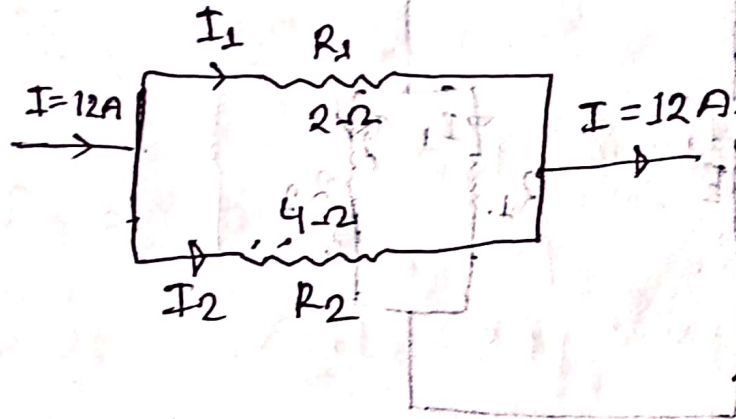Example Determine the magnitude of the current I_1 & I_2 for following figure:-



\Rightarrow From CDR,

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I$$

$$= \frac{4}{2+4} \cdot 12$$

$$= \frac{48}{6} = 8A.$$

From KCL,


$$I = I_1 + I_2$$

$$\text{OR, } 12 = 8 + I_2$$



$$\text{OR, } I_2 = 4A.$$

$$[\because \sum I_{\text{entering}} = \sum I_{\text{leaving}}]$$

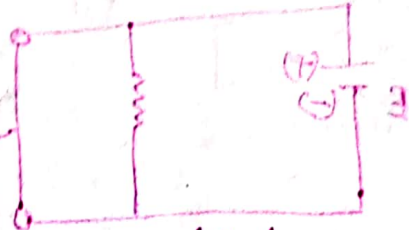
$$\begin{aligned} \text{Or, } I_2 &= \frac{R_1}{R_1 + R_2} \cdot I \\ &= \frac{2}{2+4} \cdot 12 \\ &= 4 \text{ A.} \end{aligned}$$



Voltage source in Parallel:

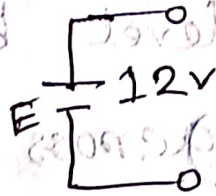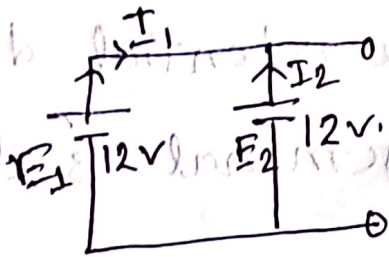


Open & short circuit:

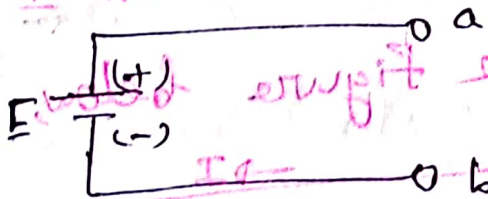

For open circuit current, $I = 0$
& voltage $V_{ab} = E$ (Supply voltage)


An open circuit can have a potential difference (voltage) across its terminals

but the current is always zero amperes.

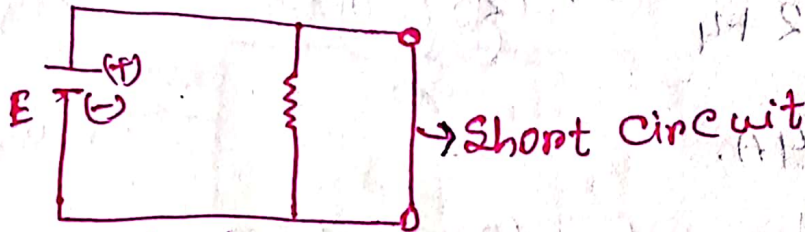


A short circuit can carry a current of any level but the potential difference (voltage) across its terminal is always zero watt.

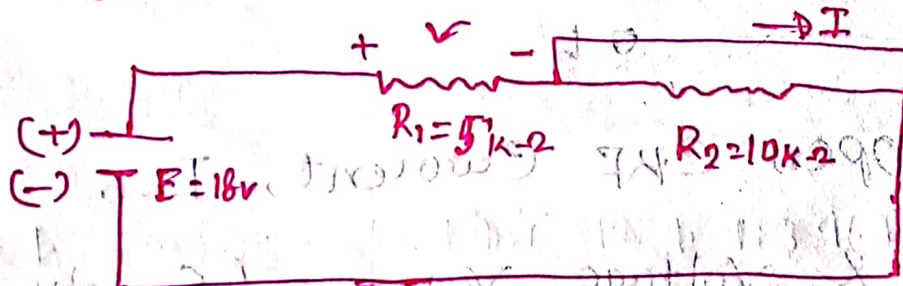Example:- Calculate the current I & the voltage V for the figure below,



Ans:- R_2 is a short circuited

So, $R_2 = 0$ & the circuit will be,

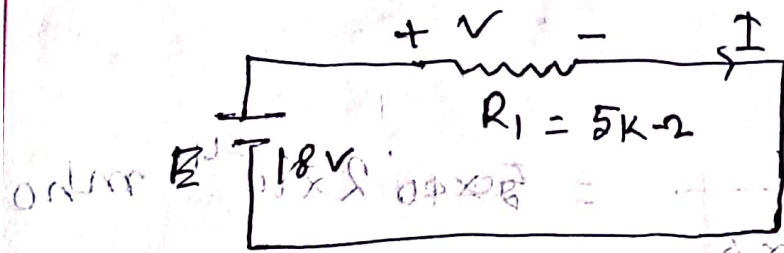

So, $I = \frac{E}{R_1} = \frac{18}{5 \times 10^3} =$

$= 0.0036 \text{ A}$


$= 3.6 \text{ mA}$

and $V = E = 18 \text{ V}$

(Ans)

Math Solve

Type-01

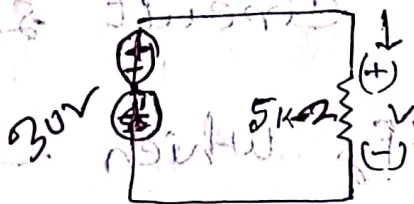

Determine Current (i), the conductance G

and the power P

Solution:-

$E = V = 30 \text{ V}$

$R = 5 \text{ k-}\Omega = 5 \times 10^3 \text{ }\Omega$


$i = \frac{V}{R} = \frac{30}{5 \times 10^3} = 6 \times 10^{-3} = 6 \text{ mA (Ans)}$

Conductance:-

$$G = \frac{1}{R} = \frac{1}{6 \times 10^3 \times 5} = 5 \times 10^{-4} \text{ mho}$$

Power:-
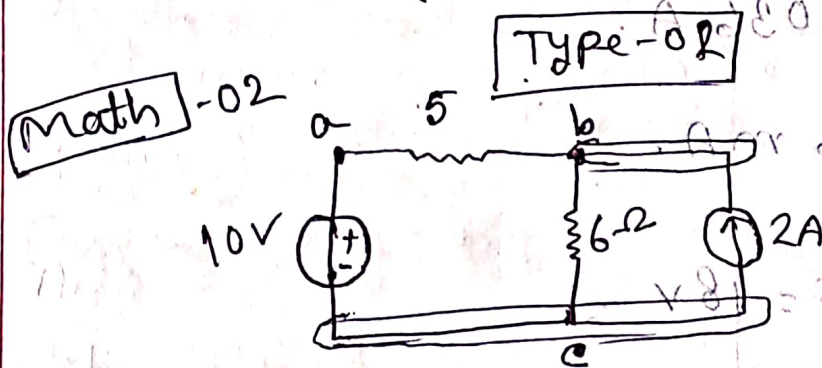
$$P = vi = 30(6 \times 10^{-3}) = 180 \text{ mW}$$



Determine the number of branches and nodes in the circuit shown in figure. Identify which elements are

in series and which are in parallel.

⇒ Branches :- এককটি শাখাকে ব্রাঞ্চ বলে। electricity
বিভক্ত হলে তা ব্রাঞ্চ।

A branch represents a single element such as a voltage source or a resistor.

The element connected to an electrical circuit is generally two terminal element. When, one circuit element is connected to the circuit, it connects itself through through both of its terminals, to be a part of a closed path.

Nodes:- [जहाँ कहीं, एक या अधिक शाखाएँ मिलती हैं]

Node is a point in a network where two or more branches are connected.

A node is usually indicated by a dot in a circuit. If a short circuit connects two nodes, the two nodes constitute a single node.

Answer of math - 02 $10 + 2 + 10 + 21 =$

Total number of branches are 4.


Node:- Total numbers of nodes are 3,

Ohm's law

It is a formula used to calculate the relationship between voltage, current & resistance in an electrical circuit. Law, $E = IR$; $V = IR$

Example 2.5


Type - 03

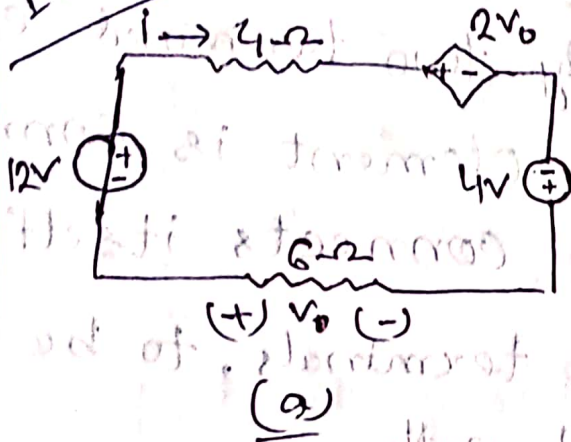

⇒ Determine v_0 & i in the circuit shown in figure.

Ans:-

We apply KVL in the figure,

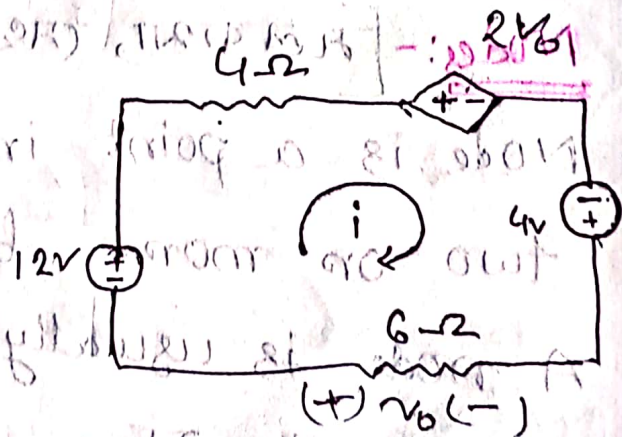

$$-V_1 + V_2 + V_3 + V_4 + V_5$$

$$= -12 + 4i + 2v_0 - 4 + 6i$$

$$= -16 + 10i + 2 \times 6i \quad \therefore v_0 = -6i$$

Applying Ohm's law

$$= -16 + 10i - 12i \quad \text{In relation to the } 6\Omega \text{ resistor}$$

$$= -16 - 2i \quad \text{Or, } i = \frac{-16}{-2} = -8A. \text{ gives}$$

$$= 8A.$$


$$\begin{aligned}
 \text{So, } V_o &= I_o R \\
 &= 8 \times 6 \text{ V} \\
 &= 48 \text{ V}
 \end{aligned}$$

-নিত্যম:-

ব্যক্তি (-) শল (+)
 (খ) একে কুরু। মোড়ে স্থানে চিহ্ন দালাই মাবে।

জোলেই বের করতে বলল জোলেই এক মূল
 ব্যবহার করতে হবে।

Example
2.7

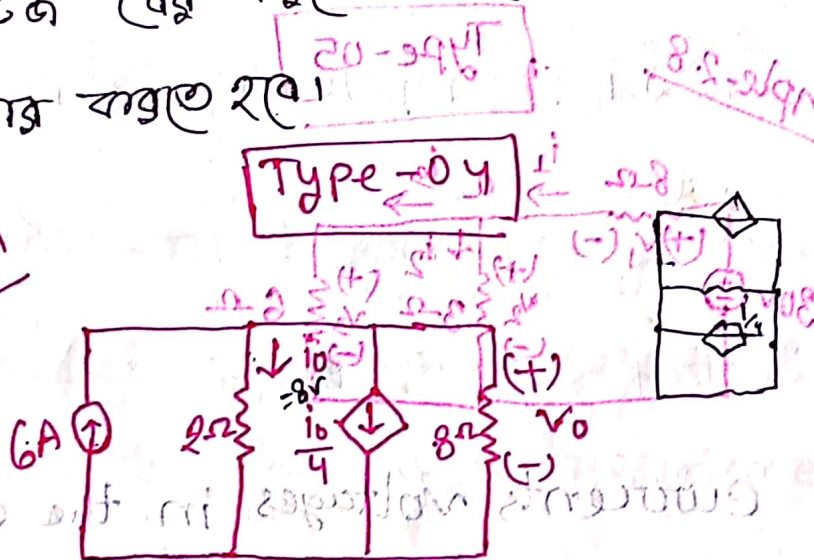

Find V_o and i_o in the circuit.


\Rightarrow Applying KCL,

$$\begin{aligned}
 6 + \frac{i_o}{4} &= i_o \\
 i_o &= \frac{6}{2} = 3 \text{ A} \equiv I_1 \\
 \text{Or, } \frac{24 + i_o}{24} &= i_o
 \end{aligned}$$

$$I_2 = \frac{i_o}{4} = \frac{3}{4}$$

$$\text{Or, } 24 + i_o = 4i_o$$

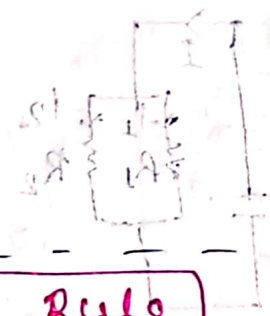... the current through any branch of a parallel resistive network is equal to the total resistance of the parallel network divided by the resistor of interest & multiplied by the total current entering the parallel configuration.



Theory

Current Divider Rule


The current through any branch of a parallel resistive network is equal to the total resistance of the parallel network divided by the resistor of interest & multiplied by the total current entering the parallel configuration.

So, it may write $I_n = \frac{R_T}{R_n} \cdot I$

For two parallel elements of equal value, the current will divide equally,

④ CDR used in parallel circuit

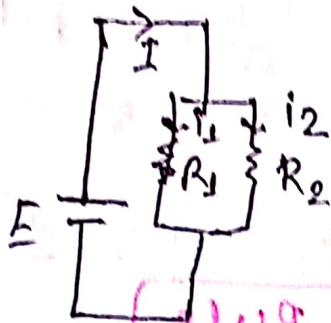For parallel elements with different values, the smaller the resistance, the greater the share of input current.



Let, R_T the equivalent resistance of two parallel resistance R_1 & R_2 .

Equivalent Resistance

$$E = I R_T \quad \text{--- (i)}$$

or, $V = I_1 R_1$

or, $I_1 = \frac{E}{R_1} = \frac{R_T}{R_1} I$ --- (ii)

and $V = I_2 R_2$


or, $I_2 = \frac{E}{R_2} = \frac{R_T}{R_2} I$ --- (iii)

From eqn (ii) & (iii), \rightarrow the current in each branch is proportional to the reciprocal of its resistance.

$$I_x = \frac{R_T}{R_x} I$$

$$I_y = \frac{R_y}{R_x + R_y} I$$

Math of KVL:-

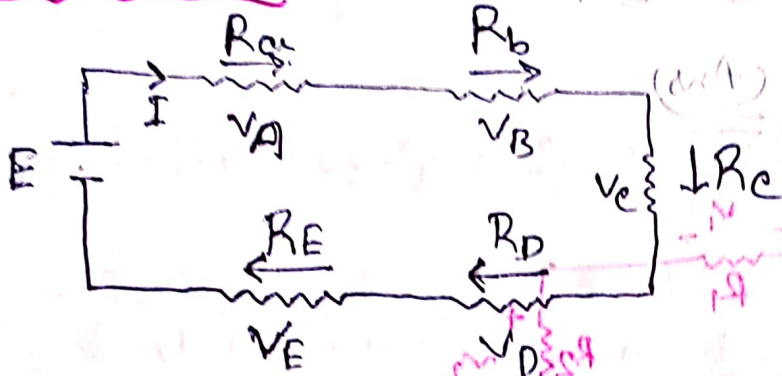

मूलतः, जलद्वारा
electricity एउ
मात्र (मात्रक)
शला = I/I_0
एउ मात्र (मात्रक)
 $V = IR$ एउ मात्र
एउ मात्र (मात्रक)
एउ मात्र $R \text{ उ } V/E$
दिले KVL लेखेको
रु।

Given, $E = 30 \text{ v.}$

$$R_a = R_b = R_c = R_d = R_e = 6 \Omega$$

$$I = ? \quad V = ?$$

Let's use KVL,

$$\begin{aligned} E &= I R_a + I R_b + I R_c + I R_d + I R_e \\ &= I \cdot 6 + I \cdot 6 + I \cdot 6 + I \cdot 6 + I \cdot 6 \\ &= 30I \end{aligned}$$

Here,


$$30I = 30$$

$$\text{OR, } I = 1 \text{ amp.}$$

By ohm's law, the voltage drops V_a, V_b & V_c are each,

$$V = IR = 1 \times 6 = 6v.$$

(Ans)

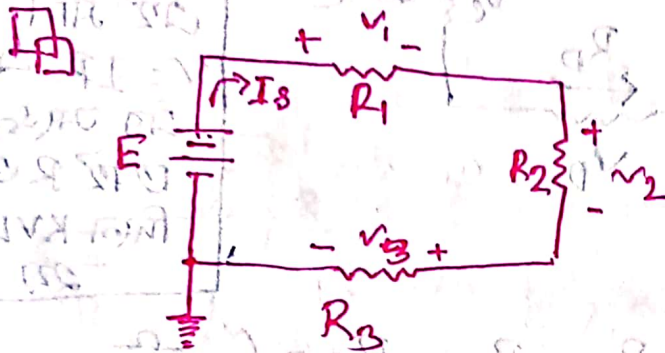

Given, $E = 20v$, $R_1 = 2\Omega$, $R_2 = 1\Omega$, $R_3 = 5\Omega$, $V_3 = 15v$

$$R_T = ?, I_3 = ?, V_1 = ?, V_2 = ?$$

$$\Rightarrow R_T = (2 + 1 + 5) \Omega = 8\Omega$$

$$I = \frac{E}{R_T} = \frac{20}{8} = 2.5A$$

$$I_2 = \frac{E}{R_2} = \frac{20}{1} = 20A$$

$$I_3 = \underline{\underline{\quad}}$$

Applying KVL,

$$E = V_1 + V_2 + V_3$$

$$I_s = \frac{E}{R_T} = \frac{20}{8} = \frac{5}{2} = 2.5 \text{ A.}$$


$$V_1 = I_1 R_1 = I_s R_1 = 2.5 \times 2 = 5 \text{ v.}$$

$$V_2 = I_2 R_2 = I_s R_2 = 2.5 \times 1 = 2.5 \text{ v}$$

(Ans)

Note:-
 - যিহিজে
 Current এর
 মানের কোনো
 পরিবর্তন হয়
 না। তাই,
 $I_s = I_1 = I_2$

Math of voltage Divider Rule:-

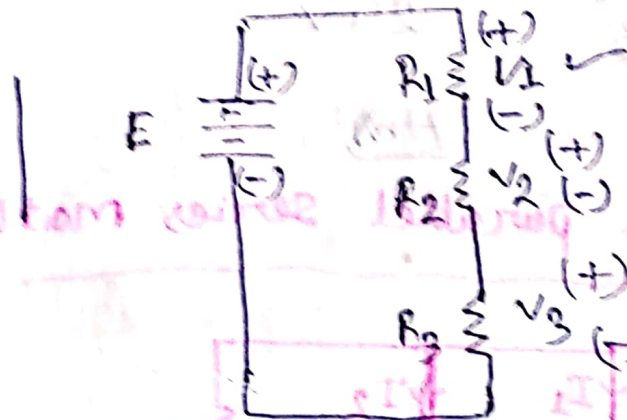

Given, $E = 45 \text{ v}$; $R_1 = 2 \text{ k}\Omega$; $R_2 = 5 \text{ k}\Omega$

$R_3 = 8 \text{ k}\Omega$,

$V_1 = ?$, $V_3 = ? \Rightarrow$ Using VDR

Using VDR on the figure,

$$V_1 = R_1 \cdot \frac{E}{R_T} \quad \text{--- (i)}$$

$$V_3 = R_3 \cdot \frac{E}{R_T} \quad \text{--- (ii)}$$

Here,

$$E = 45\text{V}$$

$$R_T = (2 + 5 + 8)\text{K}\Omega$$

$$= 15\text{K}\Omega$$


Applying them on equation (1) & (2)

$$V_1 = 2 \cdot \frac{45}{15} = 6\text{V}$$

$$V_2 = 8 \cdot \frac{45}{15} = 24\text{V}$$

(Ans)

Normal parallel series math:-

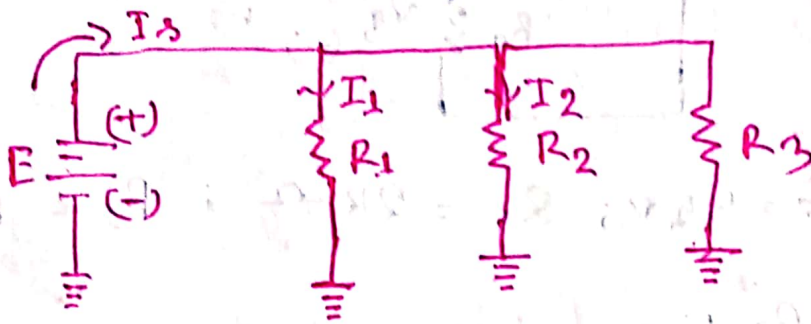

Given,

$$R_T = 4\Omega, R_1 = 10\Omega; R_2 = 20\Omega, I_1 = 4$$

$$R_3 = ? \quad I_2 = ? \quad E = ? \quad I_3 = ?$$

$$\begin{aligned} V &= IR \\ I &= \frac{V}{R} \end{aligned}$$

$$\begin{array}{r} 4, 10, 20 \\ 5 \overline{) 12, 5, 10} \\ \underline{2, 1, 2} \end{array}$$

(a) $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

or, $\frac{1}{R_3} = \frac{1}{R_T} - \frac{1}{R_1} - \frac{1}{R_2}$

or, $\frac{1}{R_3} = \frac{1}{4} - \frac{1}{10} - \frac{1}{20}$

or, $\frac{1}{R_3} = \frac{10 - 4 - 2}{40}$

or, $\frac{1}{R_3} = \frac{4}{40}$

$\therefore R_3 = 10 \Omega$ (Ans)

(b) $I_2 = \frac{E}{R_2}$ (1)


(c) $E = V_1 = I_1 R_1 = 4 \times 10 = 40 \text{ V}$

(d) $I_2 = \frac{E}{R_2} = \frac{40}{20} = 2 \text{ A}$ → R For parallel

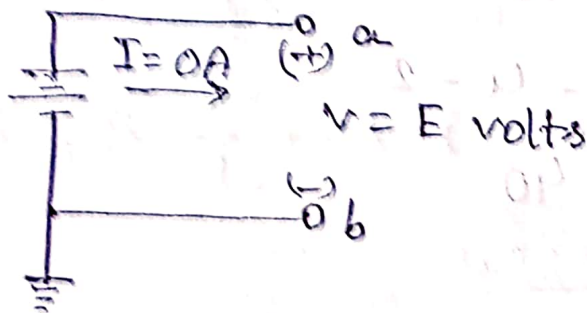(e) Total current, $I_3 = \frac{E}{R_T} = \frac{40}{4} = 10 \text{ A}$.
(Ans)

Open Circuit:- Zero amperes

An open circuit can have a potential difference (voltage) across its terminals, but the current is always zero amperes.




An open circuit exists between terminals a and b. The voltage across the open-circuit terminals is the supply voltage, but the current is zero due to the absence of a complete circuit.

Short Circuit:- Zero volts


A short circuit can carry a level determined by the external circuit but the potential difference (voltage) across the terminal is always (zero) volts.

12.8.2020

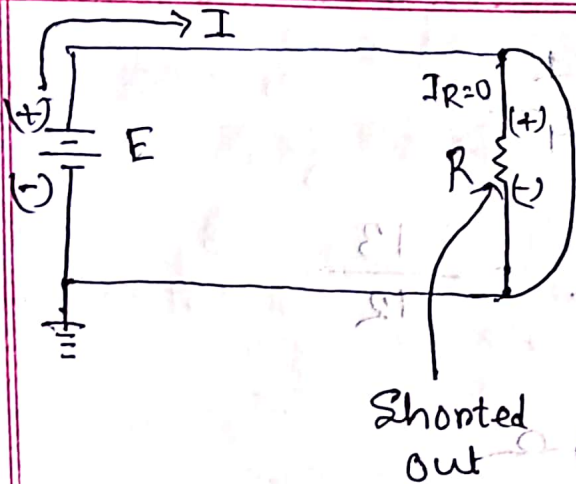

The voltage across the short circuit is always zero volts because the resistance of the short circuit is assumed to be essentially zero ohms, and $V = IR = I(0\Omega) = 0V$.

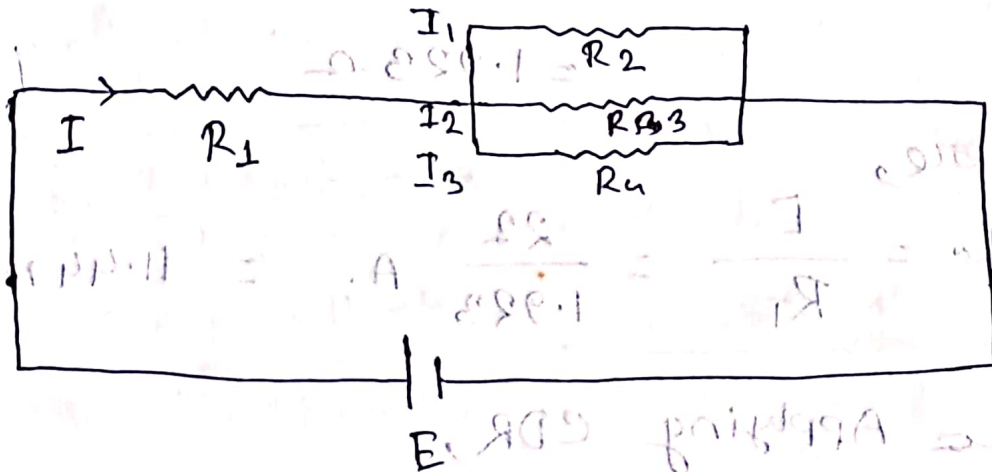Math:- (parallel circuit) \Rightarrow [With 3 Resistance]



Given,

$R_1 = 1\Omega ; R_2 = 2\Omega ; R_3 = 3\Omega ; R_4 = 4\Omega ;$

$E = 22V. \quad I = ? ; I_1 = ? ; I_2 = ? ; I_3 = ?$

\Rightarrow Here, Parallel circuit, $\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$

$$\begin{array}{r} 2 \mid 2, 3, 4 \\ \hline 1, 3, 2 \end{array}$$

$$\text{Or, } \frac{1}{R_p} = \frac{1}{2} + \frac{1}{3} + \frac{1}{4}$$

$$= \frac{6+4+3}{12} = \frac{13}{12}$$

$$\therefore R_p = \frac{12}{13} = 0.923 \Omega$$

$$\therefore R_T = R_s + R_p = (1 + 0.923) \Omega = 1.923 \Omega$$

Here,

$$I = \frac{E}{R_T} = \frac{22}{1.923} \text{ A} = 11.44 \text{ A}$$

$I_1 =$ Applying CDR,

$$I_1 = \frac{1.923}{1.923} \times 22 = 22$$

$$I_1 = \frac{R_3 R_4}{R_2 R_3 + R_3 R_4 + R_4 R_2} \times I$$

$$I_1 = \frac{3 \times 4}{2 \times 3 + 3 \times 4 + 4 \times 2} \times 11.44 = 5.28 \text{ A}$$

$$I_2 = \frac{R_2 R_4}{R_3 R_2 + R_2 R_4 + R_3 R_4}$$

$$= \frac{2 \times 4}{3 \times 2 + 2 \times 4 + 3 \times 2} \times 11.44 = \frac{8}{6 + 8 + 6} = \frac{8}{20} = \frac{2}{5}$$

$$= 0.4$$

$$= \frac{8}{6 + 8 + 12} \times 11.44 = \frac{8}{26} \times 11.44 = 3.52 \text{ A.}$$

$$I_3 = \frac{R_2 \cdot R_3}{R_4 R_2 + R_2 \cdot R_3 + R_4 R_3}$$

$$= \frac{2 \times 3 \times 11.44}{4 \times 2 + 2 \times 3 + 4 \times 3} = \frac{6 \times 11.44}{8 + 6 + 12} = \frac{6}{26} \times 11.44$$



$$= 2.64 \text{ A.}$$

(Ans)

মডি (P) এর মান বের করতে বলে তবে,
 $P = I^2 R$ এর ব্যবহার করতে হবে।

A

Exercise - Different circuit

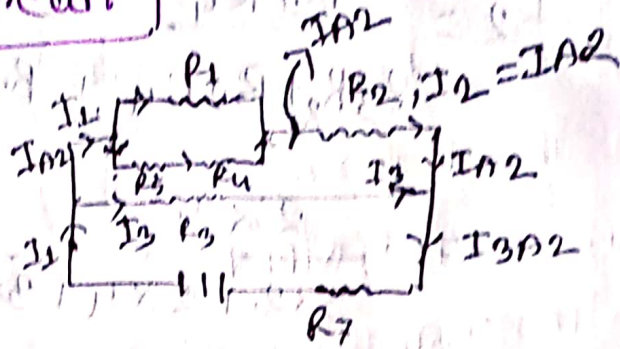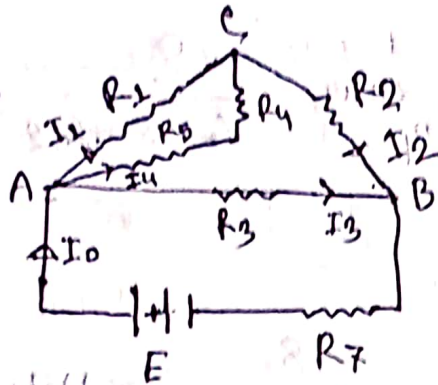

Given,

$$R_1 = 5\Omega ; R_2 = 6\Omega ; R_3 = 7\Omega ; R_4 = 3\Omega ; R_5 = 4\Omega ;$$

$$R_7 = 1\Omega ; E = 10V$$

$I_0 = ?$ all voltage drop = ?

$\Rightarrow R_5$ & R_4 are in series,



$$R_{54} = 4 + 3 = 7\Omega$$

R_1 & R_{54} are in parallel,

$$R_A = \frac{R_1 \times R_{54}}{R_1 + R_{54}} = \frac{5 \times 7}{5 + 7} = \frac{35}{12} = 2.92\Omega$$

So, R_A & R_2 are in series,
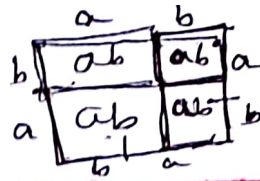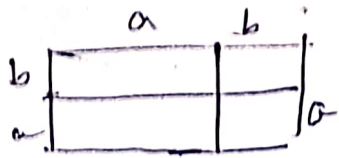
$$R_{A2} = R_A + R_2 = 2.92 + 6 = 8.92\Omega$$



$a+b$
 $2ab + b^2 + a^2$
 $(a+b)^2 = \dots$

R_{A2} & R_3 are in parallel,

$$\text{So, } R_B = \frac{R_{A2} \times R_3}{R_{A2} + R_3} = \frac{8.92 \times 7}{8.92 + 7} = 3.92 \Omega$$

Now, R_B & R_7 are in series.

$$R_{B7} = 3.92 + 1 = 4.92 \Omega$$

$$\text{So, } I_0 = \frac{E}{R_{B7}} = \frac{10}{4.92} \text{ A} = 2.033 \text{ A}$$

So, All voltage Drops:-

Applying, CDR,

$$I_0 \times R_{B7} = I_{A2} \times R_{A2} + I_{A2} \times R_3$$

$$2.033 \times 4.92 = I_{A2} \times 8.92 + I_{A2} \times 7$$

$$10 = I_{A2} \times (8.92 + 7)$$

$$I_{A2} = \frac{10}{15.92} = 0.628 \text{ A}$$

$$I_1 = I_{A2} \times \frac{R_{45}}{R_1 + R_{45}} = 0.628 \times \frac{7}{5 + 7}$$

Note:-

এখানে, I_0 AT দিলে I_{A2} সম্বন্ধে কারণ :-
 সার্কিট কে ছোট করা হয়েছে। Current সম্বন্ধে সার্কিট দু'ভাগে
 একভাগে (I_1, I_2, I_4, I_5) অন্যভাগে I_3 ও I_7 রয়েছে।

আবার আরও দুই জাম্বিকিটে $R_1, R_2, R_5, R_4 (I_1, I_2, I_5, I_4)$

রয়েছে। অর্থাৎ এখানে, I_{A2} ব্যবহার করতে হবে।

CDR এর ক্ষেত্রে আমল হোলেই তাড় মান কমানো - মা যে কারণের মান বেশি করা হয় তার বিপরীত হোলেই কমানো।
এ তার দিয়ে তুলি প্রকার এই তাড় মানেরই সমান। হোলে, কমানো
একই নিয়ম।

Now,

$$I_{A2} = \frac{R_{A2} \cdot R_{A3}}{R_{A2} + R_{A3}} \cdot I_0 = \frac{8.92 \cdot 7}{8.92 + 7} \cdot 2.033$$

$$= 0.9 \text{ A.}$$

$$I_3 = \frac{R_{A2}}{R_3 + R_{A2}} \times I_0$$

$$= \frac{8.92}{7 + 8.92} \times 2.033 \text{ A.}$$

$$= 1.14 \text{ A.}$$

$$I_1 = \frac{R_{45}}{R_1 + R_{45}} \times I_{A2} = \frac{7}{5 + 7} \times 0.9$$

$$= 0.525 \text{ A.}$$

$$I_2 = \frac{I}{5+7} \times I_{A2} = 0.9 \text{ A}$$

$$I_4 = \frac{R_1}{R_1 + R_4} \times I_{A2} = \frac{5}{5+7} \times 0.9$$
$$= 0.375 \text{ A} = I_5$$

$$I_7 = \frac{I}{5+7}$$

$$I_7 = I_3 + I_{A2} =$$

$$= 1.14 + 0.9 = 2.04 \text{ A}$$

Now,

$$V_1 = I_1 R_1 = 0.525 \times 5 = 2.625 \text{ V}$$

$$V_2 = I_2 R_2 = (0.9 \times 6) \text{ V} = 5.4 \text{ V}$$

$$V_3 = I_3 R_3 = (1.14 \times 7) \text{ V} = 7.98 \text{ V}$$


$$V_4 = I_4 R_4 = 0.375 \times 3 = 1.125 \text{ V}$$

$$V_5 = I_5 R_5 = 0.375 \times 4 = 1.5 \text{ V}$$


$$V_6 = I_7 R_7 = 2.04 \times 1 = 2.04 \text{ V}$$

(Ans)


Delta (Δ) - Wye (Y) transformation:-

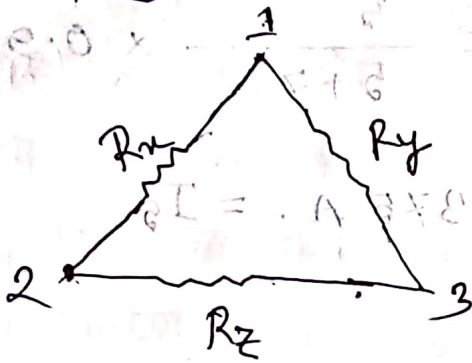

(a)

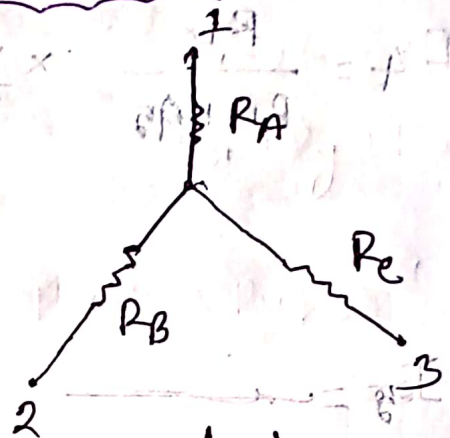

(b)

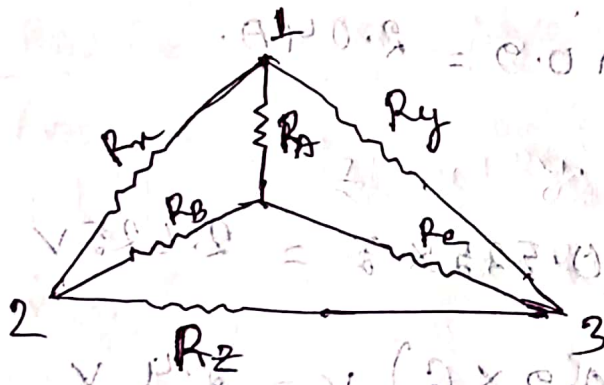

For wye,

$$R_{12} = R_A + R_B \quad \text{--- (i)}$$

$$R_{23} = R_B + R_C \quad \text{--- (ii)}$$

$$R_{31} = R_C + R_A \quad \text{--- (iii)}$$

For Delta,

$$R_{12} = \frac{R_C(R_B + R_C)}{R_A + (R_B + R_C)} \quad \text{--- (iv)}$$

$$R_{23} = \frac{R_z(R_x + R_y)}{R_z + (R_x + R_y)} \quad \text{--- (v)} \quad \text{(iii) changed}$$

$$R_{31} = \frac{R_y(R_z + R_x)}{R_y + (R_z + R_x)} \quad \text{--- (vi)}$$

Now,

$$R_A + R_B = \frac{R_x(R_y + R_z)}{R_x + (R_y + R_z)} \quad \text{--- (vii)}$$

$$R_B + R_C = \frac{R_z(R_x + R_y)}{R_z + (R_x + R_y)} \quad \text{--- (viii)}$$

$$R_C + R_A = \frac{R_y(R_z + R_x)}{R_y + (R_z + R_x)} \quad \text{--- (ix)}$$

Now, (vii) - (ix),

$$R_A + R_B - R_C - R_A = \frac{R_x(R_y + R_z)}{R_x + (R_y + R_z)} - \frac{R_y(R_z + R_x)}{R_y + R_z + R_x}$$

$$\text{Or, } R_B - R_C = \frac{R_x R_y + R_x R_z - R_y R_z - R_x R_y}{R_y + R_z + R_x}$$

$$\text{Or, } R_B - R_C = \frac{R_x R_z - R_y R_z}{R_x + R_y + R_z} \quad \text{--- (x)}$$

$$R_B + R_C - R_B + R_C = \frac{R_x(R_x + R_y)}{R_y + (R_x + R_z)} - \frac{R_x R_z - R_y R_z}{R_x + R_y + R_z}$$

$$\text{or, } 2R_C = \frac{R_x R_x + R_y R_z - R_x R_z + R_y R_z}{R_x + R_y + R_z}$$

$$\text{or, } 2R_C = \frac{2R_y R_z}{R_x + R_y + R_z}$$

$$\text{or, } R_C = \frac{R_y R_z}{R_x + R_y + R_z}$$

$\frac{1}{2}IR$



In the same way,

$$R_A = \frac{R_x R_y}{R_x + R_y + R_z} \quad \text{--- (xii)}$$

$$R_B = \frac{R_x R_z}{R_x + R_y + R_z} \quad \text{--- (xiii)}$$



Math Exercise of Delta & wye circuit

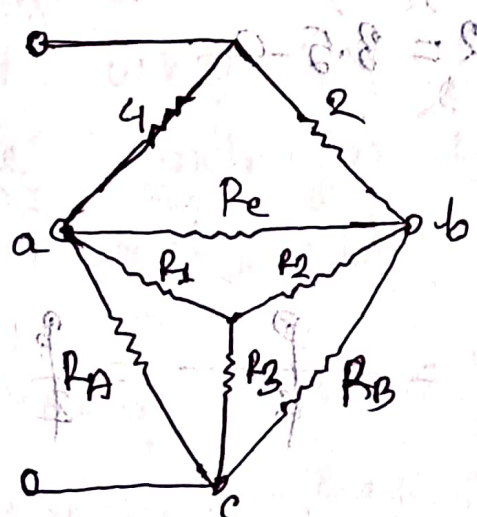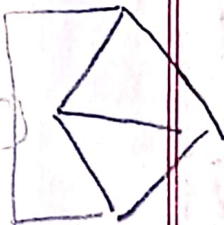

Given,

$$R_A = 3 \Omega$$

$$R_B = 3 \Omega$$

$$R_e = 6 \Omega$$

$$R_f = ?$$


From Δabc to y transformation,

$$R_1 = \frac{R_A R_e}{R_A + R_B + R_e} = \frac{3 \times 6}{3 + 3 + 6} = \frac{18}{12} = \frac{3}{2} \Omega = 1.5 \Omega$$

$$R_2 = \frac{R_A \cdot R_B}{R_A + R_B + R_C} = \frac{3 \times 3}{3 + 3 + 6} = \frac{9}{12} = \frac{3}{4} = 0.75 \Omega$$

$$R_3 = \frac{R_A \cdot R_B}{R_A + R_B + R_C} = \frac{3 \cdot 3}{3 + 3 + 6} = \frac{9}{12} = \frac{3}{4} = 0.75 \Omega$$

Now,

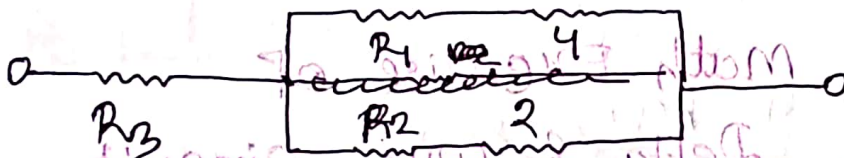

$$R_{A1} = R_1 + 4 = 1.5 + 4 = 5.5 \Omega$$

$$R_{B2} = R_2 + 2 = 1.5 + 2 = 3.5 \Omega$$


$$R_C = R_{A1} \parallel R_{B2}$$

$$= \frac{R_{A1} \cdot R_{B2}}{R_{A1} + R_{B2}}$$

$$= \frac{5.5 \times 3.5}{5.5 + 3.5}$$

$$= \frac{19.25}{9} = 2.14 \Omega$$

$$= 2.14 \Omega$$

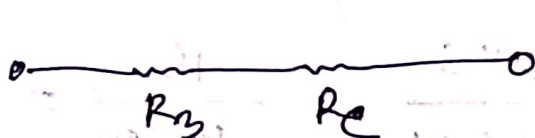

$$R_T = R_3 + R_C$$

$$= 0.75 + 2.14$$

$$= 2.89 \Omega \text{ (Ans)}$$

Electrical Network Theorem

1) Mesh / Loop analysis.

2) Nodal Analysis.

3) Superposition Theorem. (Result of superposition principle suited to the network analysis of electrical circuits.)

4) Reciprocity Theorem:-

⇒ In any branch on current due to a single source of voltage (v) in the network is equal to the current through that branch is which the source was originally placed, when the source is again put in the branch, in which the current was originally obtained.

5) ~~Thevenin's~~ Theorem.

5) Thevenin's Theorem:-

Any linear electrical network containing only voltage sources, current sources & resistances can be replaced at terminals

A-B by an equivalent combination
of a voltage source V_{th} in a
series connection with a resistance

R_{th} .

6] Norton's Theorem:-

Any linear circuit containing several
energy sources and resistances can be
replaced by a single constant current
generator in parallel with a single
resistor.

□ Branch Current Methode :- (১০০০)

১) যদি কোন শাখা (+) তরফে প্রবাহিত হয় তাহলে (+) নিম্নমঃ

১) যদি শাখাটি বেগনে ডিরেকশন বা নাম দেওয়া না থাকে তবে নিজে নিজে দেওয়া হবে।

২) Current এর sign (+) বা (-) দেওয়া। এর মানে KVL বেত্র করতে সুবিধা বেশি হয়।

[বেত্রের উভয় সমষ্টি (-) হলে (+) এ মান]

৩) প্রতিটি Node-এ KCL লিখতে হবে।

KCL বেত্র করার নিম্নমঃ

$$\text{Current entering} = \text{Current outgoing}$$

৪) প্রতিটি Loop-এর মধ্যে KVL লিখতে হবে।

KVL বেত্র করার নিম্নমঃ

i) Clockwise or Anticlockwise

ii) যে দিকেরে ঘুরতে হবে, এই দিকেরে লক্ষ করতে হবে। (+) হলে (-) এ হলে voltage drop.


৫) যে equation পাওয়া যাবে ওগুলো হিসাব

করে solve করতে হবে।

- বেগনো শাখার current বেত্র করে শোনা মনে লক্ষ্য। মাত্র ফল ৯০% কাজে লাগে।

- Note:-
- (i) Resistor এর ডিগ্রি চুক্তি (+) আর (-) শনে (-)। এছাড়াই Current এর Direction এর উন্মুক্ত নির্ভর করবে।
 - (ii) I এর মান = KEL
V এর মান = KVL

Math of B.C.M

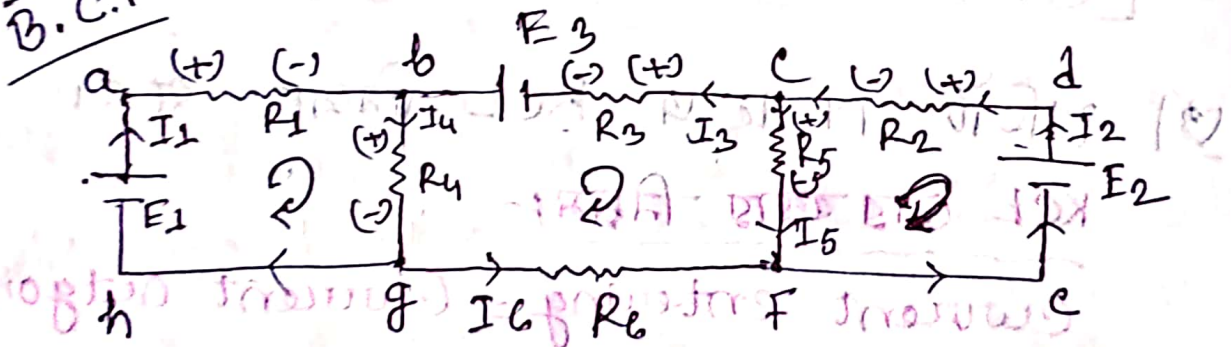

Given;

$$E_1 = 25V ; E_2 = 15V ; E_3 = 10V ; R_1 = 40\Omega ; R_2 = 20\Omega ;$$

$$R_3 = R_6 = 10\Omega ; R_4 = R_5 = 100\Omega$$

Find all Branch Current,

Applying KCL,

$$I_4 = I_1 + I_3 \quad \text{--- (i)}$$

$$I_4 = I_1 + I_6 \quad \text{--- (ii)}$$

$$I_5 = I_2 - I_6$$

$$I_2 - I_3 = I_5$$

$$I_5 = I_2 - I_6$$

Merging equation (i) & (ii)

$$I_1 + I_3 = I_1 + I_6$$

$$\text{Or, } I_3 = I_6$$

~~Merging equation (iii) & (iv)~~

$$\text{Or, } I_3 = I_6$$

$$\text{Or, } I_3 = I_6$$

$$\text{So, } I_1 + I_6 = I_4$$

$$\text{Or, } I_1 = I_4 - I_6$$

$$\text{And, } I_5 = I_2 - I_6$$

$$\text{Or, } I_2 = I_5 + I_6$$

Applying KVL,

$$E_1 = I_1 R_1 + I_4 R_4$$

$$\text{Or, } 25 = I_1 \cdot 40 + I_4 \cdot 100$$

$$E_2 = I_5 R_5 + I_2 R_2$$

$$\text{Or, } 15 = I_5 \cdot 100 + I_2 \cdot 20$$

$$E_3 = I_3 R_3 + I_6 R_6 - I_4 R_4 - I_5 R_5$$

$$\text{Or, } 10 = 10 I_3 + 100 I_6 - 100 I_4 - 100 I_5$$

Again,

$$25 = I_1 \cdot 40 + (I_1 + I_6) 100$$

$$\text{Or, } 25 = 40 I_1 + 100 I_1 + 100 I_6$$

$$\text{Or, } 25 = 140 I_1 + 100 I_6 \quad \text{--- (ix)}$$

And,

$$15 = (I_2 - I_6) 100 + 20 I_2$$

$$\text{Or, } 15 = 100 I_2 - 100 I_6 + 20 I_2$$

$$\text{Or, } 15 = 120 I_2 - 100 I_6 \quad \text{--- (x)}$$

Also,

$$10 = 10 I_3 + 10 R_6 - (I_1 + I_6) 100 + (I_2 + I_6) 100$$

$$\text{Or, } 10 = 10 I_3 + 10 R_6 - 100 I_1 - 100 I_6 - 100 I_2 + 100 I_6$$

[এখানে element প্রোগ্রাম
ভিত্তি চুক্তি সেই চিহ্ন
- হিসাবে বসানো হয়েছে]

Or,

$$10 = 10I_3 + 10E_6 - 100I_1 - 100I_2$$

$$\text{Or, } 10 = 20E_6 - 100I_1 - 100I_2 \quad \text{--- (x)}_i$$

Now,

$$D = \begin{vmatrix} 140 & 0 & 100 \\ 0 & 120 & -100 \\ -100 & -100 & 20 \end{vmatrix}$$

$$= 140 \{ 120 \times 20 + (100 \times 100) \} - 0 \{ (-100 \times 100) \} - 100 (-120 \times 100)$$

$$= 140 \{ 1736000 - 1200000 \}$$

$$= 536000$$

$$I_1 = \frac{\begin{vmatrix} 25 & 0 & 100 \\ 15 & 120 & -100 \\ 10 & -100 & 20 \end{vmatrix}}{D} = \frac{\{ 25(120 \times 20 + (-100 \times -100)) \} - \{ 15(-100 \times 100) \} + \{ 10(120 \times 100) \}}{D}$$

$$= \frac{310000 + 150000 + 120000}{D}$$

$$= \frac{580000}{536000} = 1.08 \text{ A. } \quad \left[\text{शिसावे डूम आ(ह)} \right]$$

$$I_2 = \begin{vmatrix} 140 & 25 & 100 \\ 0 & 15 & -100 \\ -100 & 10 & 120 \end{vmatrix}$$

$$= \{ 140(15 \times 20 + 10 \times 100) - 100(25 \times -100 + 15 \times 100) \}$$

$$= \frac{182000 + 400000}{536000}$$

$$= 1.08 \text{ A.}$$

Note:-

নিম্নম স্কি আছে, হিসাবে হাড়মিল আছে

$$\begin{vmatrix} 100 & 0 & 20 \\ 0 & 15 & -100 \\ 20 & 10 & 120 \end{vmatrix} = \dots$$


নিম্নম স্কি আছে, হিসাবে হাড়মিল আছে

Loop Current Method:- Loop current method

① প্রতি Loop এর মধ্যে Current ধরে নিবে।

② প্রতি লুপে KVL লিখতে হবে। KVL লেখতে Current এর সাপেক্ষে।

(এই Branch Current এর মতো হবে না)

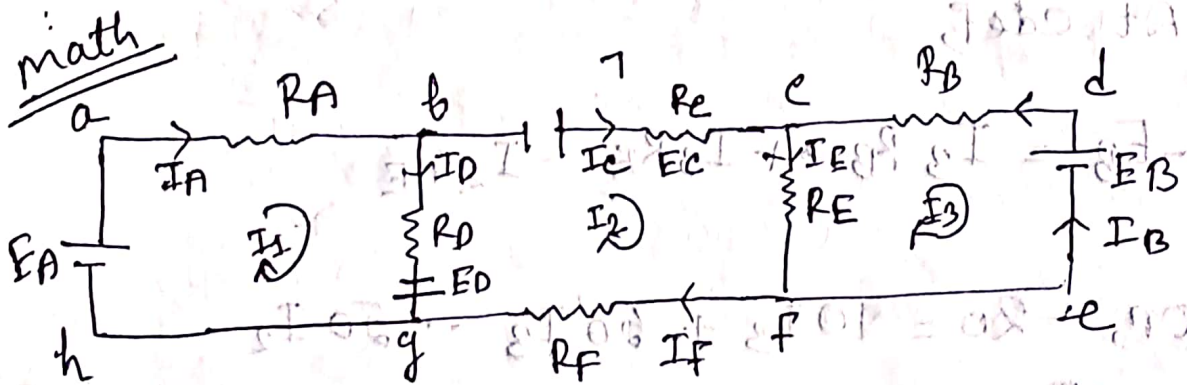

Given;

$E_A = 30; E_B = 20V; E_c = 5V; E_D = 10V.$

$R_A = 20\Omega; R_B = 10\Omega; R_c = 30\Omega; R_D = 40\Omega$

$R_E = 50\Omega; R_F = 25\Omega$

At abgh,

$$E_A + E_D = I_1 R_A + I_1 R_D - I_2 R_D$$

Or, $30 + 10 = I_1 \cdot 20 + I_1 \cdot 40 - I_2 \cdot 40$

$$\text{or, } 40 = 60 I_1 - 40 I_2 \quad \text{--- (i)}$$

At abcfg,

$$E_c - E_D = I_2 R_c + I_2 R_f - E_D I_1 R_D \quad \text{--- (ii)}$$

$$\text{or, } 5 - 10 = 30 I_2 + 25 I_2 - 40 I_1$$

$$\text{or, } -5 = 55 I_2 - 40 I_1 \quad \text{--- (ii)}$$

At cdef,

$$-E_B = I_3 R_B + I_3 R_E - I_2 R_E$$

$$\text{or, } -20 = 10 I_3 + 50 I_3 - 50 I_2$$

~~-E_1~~

$$\text{or, } -20 = 60 I_3 - 50 I_2 \quad \text{--- (iii)}$$

From equation (i), (ii) & (iii)

$$40 = 60 I_1 - 40 I_2 + 0$$


$$\del{-5 = 55 I_2}$$

$$-5 = -40 I_1 + 55 I_2 + 0$$

$$-20 = 0 - 50 I_2 + 60 I_3$$

(काल्पित्वा शून्य माने)

Mesh Current:-

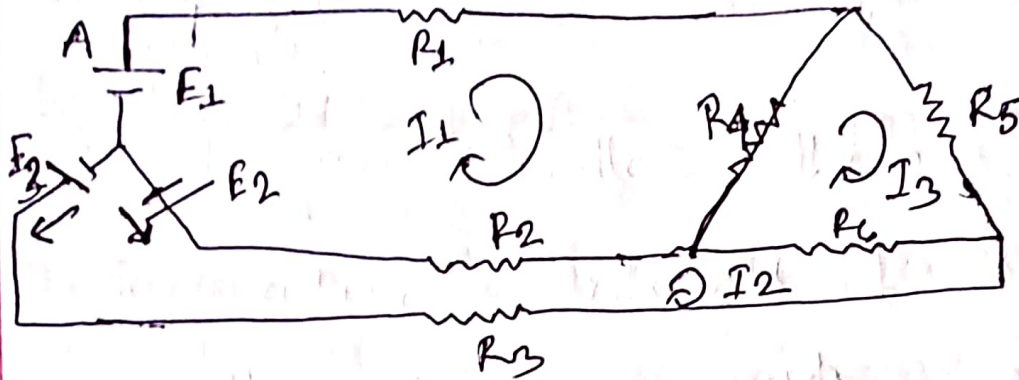

Given,

$$E_1 = 4V \quad R_1 = 11\Omega \quad R_4 = 15\Omega$$

$$E_2 = 12V \quad R_2 = 9\Omega \quad R_5 = 2\Omega$$

$$E_3 = 8V \quad R_3 = 5\Omega \quad R_6 = 6\Omega$$

Mesh current = ?

\Rightarrow

(आगे मात्र)

$$I_1 = -0.3664A$$

$$I_2 = -0.052A$$

$$I_3 = -0.29A$$

Mid Term Finishes here \Leftarrow
Final starts here \Rightarrow



**KEEP
CALM
ITS TIME FOR THE
FINAL
EXAM**

Final

Lesson: AC Circuits

9.1

⊛ A sinusoid is a signal that has the form of the sine or cosine function.

⊛ A sinusoidal current is usually referred to as alternating current (ac).

Such a current reverses at regular time intervals and has alternately positive & negative values.

⊛ Circuits driven by sinusoidal current or voltage sources are called as AC circuits.

⊛ It is form of voltage generated throughout the world and supplied to homes, factories, laboratories, and so on.

⊛ Through Fourier analysis, any practical periodic signal can be represented by a

sum of sinusoids.

x (*) Sinusoid helps to analysis of periodic signals.

(*) It can handle mathematically. The derivative & integral of a sinusoid are themselves sinusoids.

(*) A sinusoidal forcing function produces both a transient (अस्थायी) & a steady-state (स्थायी) response.

The transient response dies with time & only the steady-state response remains.

(*) When transient response has become negligibly small compared with the steady-state response, we say that the circuit is operating at sinusoidal steady-state.


9.2

→ (सिद्ध) वोल्टेज


Sinusoids :-

$$v(t) = V_m \sin \omega t \quad \text{--- (9.1)}$$

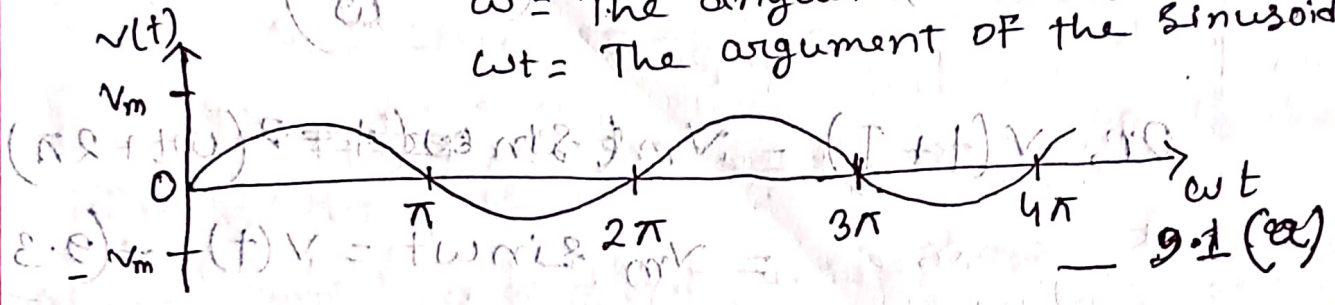V_m = The amplitude of the sinusoid
 ω = The angular (frequency) in rad/s
 ωt = The argument of the sinusoid.



⇒ A function of its argument

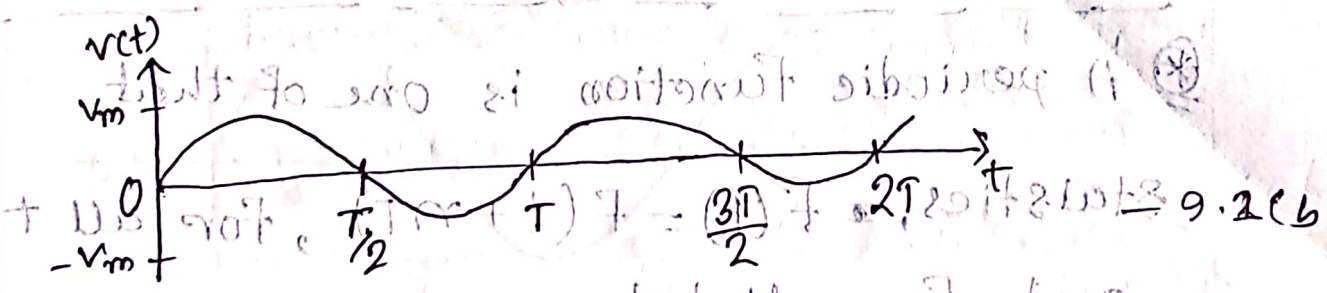

⇒ A function of time.

So, from two plots, $\omega T = 2\pi$

$$\text{or, } T = \frac{2\pi}{\omega} \quad \text{--- (9.2)}$$

So, from 9.1 equation if we replace it

$t \rightarrow (t+T)$ then we get,

$$v(t+T) = v_m \sin \omega(t+T)$$

$$\text{Or, } v(t+T) = v_m \sin \omega \left(t + \frac{2\pi}{\omega} \right)$$

$$\begin{aligned} \text{Or, } v(t+T) &= v_m \sin \omega (t + 2\pi) \\ &= v_m \sin \omega t = v(t) \end{aligned} \quad \text{--- (9.3)}$$

Hence,

$$v(t+T) = v(t) \quad \text{--- (9.4)}$$

(*) A periodic function is one of that satisfies, $f(t) = f(t+nT)$, for all t and for all integers n

(*) $f = \frac{1}{T}$ [T is a periodic function. It is the time of one complete cycle or seconds/cycle.] --- (9.5)

(*) It is clear from (9.5) & (9.2) that

$$\omega = 2\pi f$$


$$\text{rad/s}$$

$$f = \text{Hz or, s}^{-1}$$

More general expression for the sinusoid:-

$$v(t) = v_m \sin(\omega t + \phi) \quad (9.7)$$

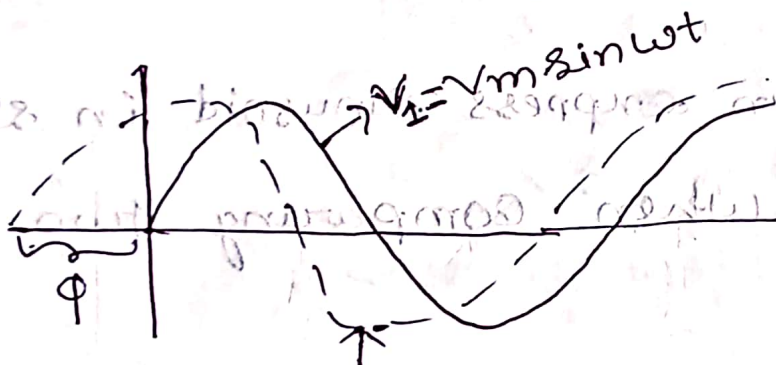Here, $(\omega t + \phi)$ is the argument & ϕ is the phase. Both argument and phase can be in radians or degrees.



$$v_2 = v_m \sin(\omega t + \phi)$$

Here, v_1 starts first in time & v_2 leads

v_1 . & we can say that v_2 leads v_1 by

ϕ . Or, v_1 lags v_2 by ϕ . If $\phi \neq 0$, we

also say that v_1 and v_2 are out

of phase. But, if $\phi = 0$, the v_1 and

v_2 are said to be in phase;

They reach their minima & maxima exactly the same time. \therefore bioassays

We can compare v_1 & v_2 in this

manner. Because they operate at the same frequency, they don't need to have the same amplitude.

□ We can express sinusoid in sine or cosine. When comparing two sinusoids.

But both have to be in sine or cosine with positive amplitudes.

$$\sin(A \pm B) = \sin A \cdot \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cdot \cos B \mp \sin A \sin B$$




And also,

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t \quad (9.10)$$
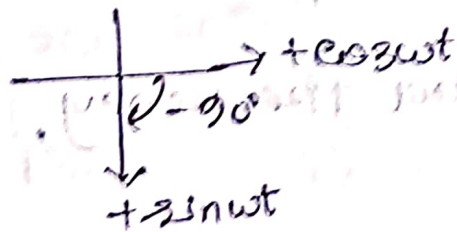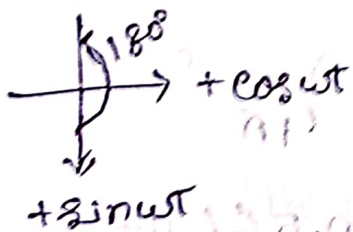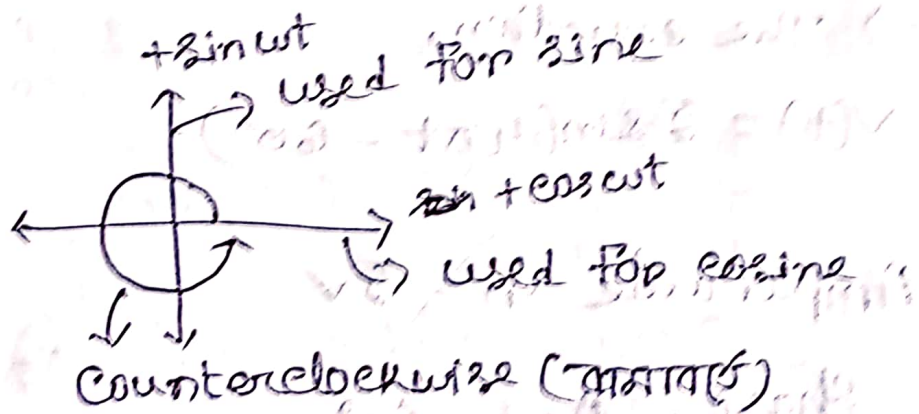
$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$



$$\textcircled{*} A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta) \quad (9.11)$$

where

$$C = \sqrt{A^2 + B^2} \quad ; \quad \theta = \tan^{-1} \frac{B}{A} \quad (9.12)$$

□ Gu

Math-01

Given the sinusoid $5 \sin(4\pi t - 60^\circ)$

Calculate its amplitude, phase, angular frequency, period and frequency.

⇒ The equation,

$$v(t) = 5 \sin(4\pi t - 60^\circ)$$

Amplitude $v_m = 5 \text{ V}$

Phase, $\phi = -60^\circ$

Angular frequency, $\omega = 4\pi$

$$= 12.566 \text{ Hz}$$


$$\text{period, } T = \frac{2\pi}{\omega} = \frac{2\pi}{4\pi} = \frac{1}{2} = 0.5 \text{ s.}$$

$$\text{Frequency, } F = \frac{1}{T} = \frac{1}{0.5} = 2 \text{ Hz}$$

$$\sin(-\theta) = -\sin\theta$$

$$\cos(-\theta) = \cos\theta$$

$$\tan(-\theta) = -\tan\theta$$

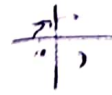

Q Calculate the phase angle between ϕ

$$V_1 = -10 \cos(\omega t + 50^\circ) \text{ and } V_2 = 12 \sin(\omega t - 10^\circ)$$

State which sinusoid is leading.

Method one:-

we will have to convert them into same form.

$$V_1 = -10 \cos(\omega t + 50^\circ) \rightarrow \omega = \frac{2\pi}{T} \text{ not used}$$

$$= -10 \left(\cos\left(\frac{\omega t}{2\pi} + 50^\circ\right) \right) \quad \text{--- } \odot$$

$$= 10 \cos\left(\frac{\omega t}{2\pi} + 50^\circ - 180^\circ\right)$$

$$= 10 \cos\left(\frac{\omega t}{2\pi} - 130^\circ\right) \quad \text{--- } \textcircled{1}$$

and,

$$V_2 = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10^\circ - 90^\circ)$$

$$= 12 \sin(\omega t - 100^\circ) \quad \text{--- } \textcircled{2}$$

From equation $\textcircled{1}$ & $\textcircled{2}$, we can write that the phase difference between

$$\begin{aligned} \cos 120^\circ &= (\cos -) \cos 120^\circ \\ \cos 20^\circ &= (\cos -) \cos 20^\circ \\ \cos 120^\circ &= (\cos -) \cos 120^\circ \end{aligned}$$

v_1 & v_2 is 30° , and the other is 130° (or 130°)

$$v_2 = 12 \cos(\omega t - 130^\circ + 30^\circ)$$

or, $v_2 = 12 \cos(\omega t - 100^\circ)$

method-2

Alternatively, we may express v_1 in sine form:-

$$\begin{aligned} v_1 &= -10 \cos(\omega t + 50^\circ) \\ &= 10 \sin(\omega t + 50^\circ - 90^\circ) \\ &= 10 \sin(\omega t - 40^\circ) \\ &= 10 \sin(\omega t - 10^\circ - 30^\circ) \end{aligned}$$

But, $v_2 = 12 \sin(\omega t - 10^\circ)$

Comparing the two shows that v_1 lags v_2 by 30° . This is the same as saying that v_2 leads v_1 by 30° .

Method-03

We may regard v_1 as simply $-10 \cos \omega t$ with a phase shift of $+50^\circ$. Hence v_1 is


as shown in fig. ~~as~~ similarly, v_2 is ~~is~~

$12 \sin \omega t$ with a phase shift of -10° , as


shown in fig. It is easy to see from


Figure that v_2 leads v_1 by 30°

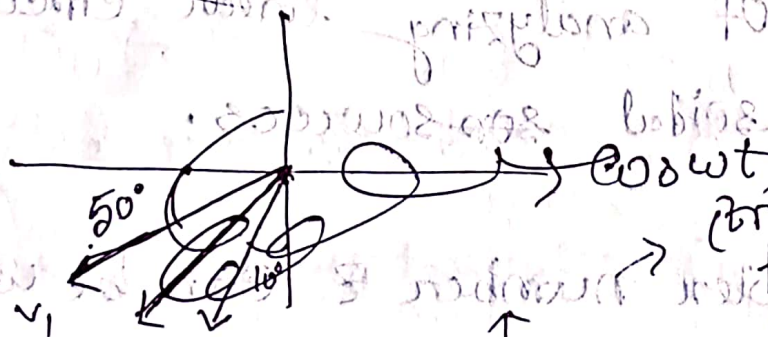that is $(90^\circ - 50^\circ - 10^\circ)$.



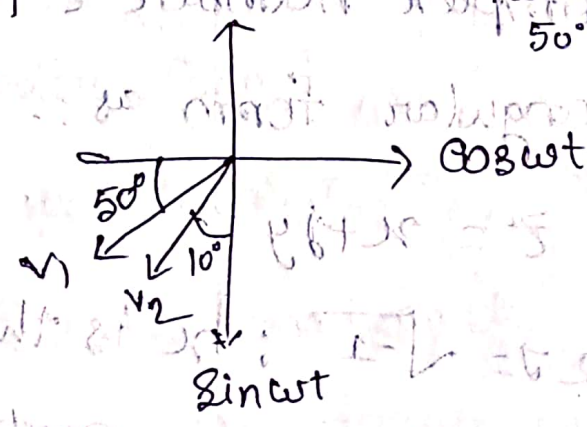here from axis
 $50^\circ = v_1 \ \& \ v_2 = 80^\circ$



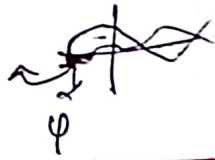

Phasors :-

Sinusoids are easily expressed in terms of Phasors.

A phasor is a complex number that represents the amplitude (magnitude) and phase of a sinusoid.

Phasors provide a simple means of analyzing linear circuits excited by sinusoidal sources.

A complex number z can be written in rectangular form as :-

$$z = x + jy$$

where $j = \sqrt{-1}$; x is the real part of z .

y is the imaginary part of z .

x & y do not represent a location.

as in two dimensional vector analysis, but rather the real and imaginary parts of Z in the complex plane.

The complex number Z can also be written in polar or exponential form

as:-

$$Z = r \angle \phi = r e^{j\phi}$$

where r is the magnitude of Z & ϕ is the phase of Z .

Z can be represented in three ways:-

$$Z = x + jy \quad [\text{Rectangular Form}]$$

$$Z = r \angle \phi \quad [\text{Polar Form}]$$

$$Z = r e^{j\phi} \quad [\text{Exponential Form (Euler's Form)}]$$

x (axis) represent the real part and the y (axis) represents the imaginary part of a complex number.


we can get r and ϕ as,

$$r = \sqrt{x^2 + y^2}; \quad \phi = \tan^{-1} \frac{y}{x}$$

we can obtain x and y as,

$$x = r \cos \phi$$

$$y = r \sin \phi$$

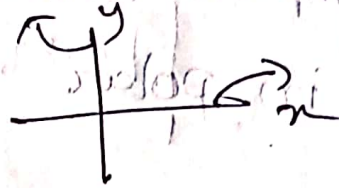

z may be written as,

$$z = x + jy = r \angle \phi = r (\cos \phi + j \sin \phi)$$

In complex numbers are better performed in rectangular form.

multiplication and division are better done in polar form.

$$z = x + jy = r \angle \phi$$

$$z_1 = x_1 + jy_1 = r_1 \angle \phi_1$$

$$z_2 = x_2 + jy_2 = r_2 \angle \phi_2$$

Complex no - शिमाव-तिसका

Addition:

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction:

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication:

$$z_1 \cdot z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

Division:

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

Reciprocal: (आवृत्त/पुस्तक)

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

Square root:

$$\sqrt{z} = \frac{1}{r} \angle -\phi$$

Complex Conjugate:

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

$$\boxed{\frac{1}{j} = -j}$$

The idea of phasor representation is based on Euler's identity.

In general,

$$e^{\pm j\phi} = \cos\phi \pm j\sin\phi$$

which shows that we may regard $\cos\phi$ and $\sin\phi$ as the real and imaginary parts of $e^{j\phi}$; we may write:

$$\cos\phi = \operatorname{Re}(e^{j\phi})$$

$$\sin\phi = \operatorname{Im}(e^{j\phi})$$

$$\left[\begin{array}{l} \operatorname{Re} = \text{real part} \\ \operatorname{Im} = \text{Imaginary part} \\ \text{of } v(t) = v_m \cos(\omega t + \phi) \end{array} \right]$$

So,

$$v(t) = v_m \cos(\omega t + \phi) = \operatorname{Re}(v_m e^{j(\omega t + \phi)})$$

$$v(t) = \operatorname{Re}(v_m e^{j\phi} \cdot e^{j\omega t})$$

where,

$$v = v_m e^{j\phi} = v_m \angle \phi \quad (9.24)$$

where ϕ is the phase angle

A phasor is a complex representation of the magnitude & phase of a sinusoid.

A phasor may be regarded as a mathematical equivalent of a sinusoid with the time dependence dropped.

If we use sine for the phasor instead of cosine, then

$$v(t) = V_m \sin(\omega t + \phi) = \text{Im}(V_m e^{j(\omega t + \phi)})$$

and the corresponding phasor is the same as that eqn (9.24)

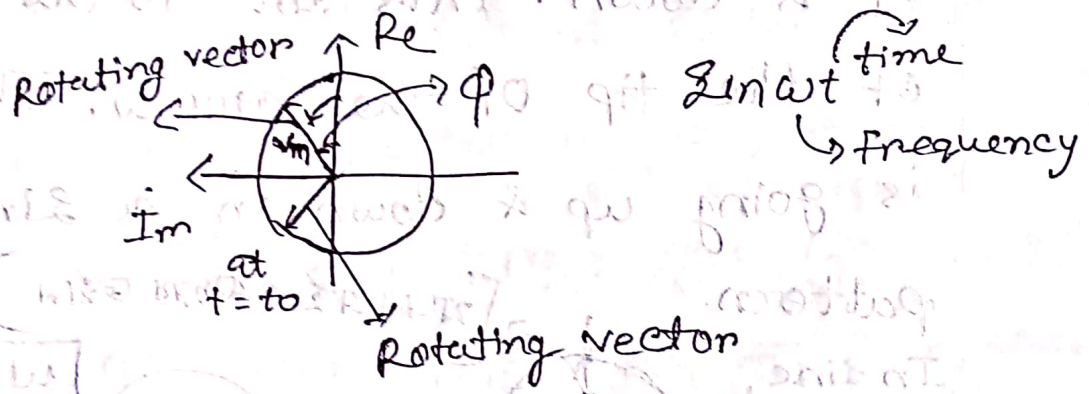


Figure - 9.7(a)

- 1) Sinor rotating counterclockwise.
- 2) Its projections on the real axis, as a function of time.

Sine and Cosine rotating vector

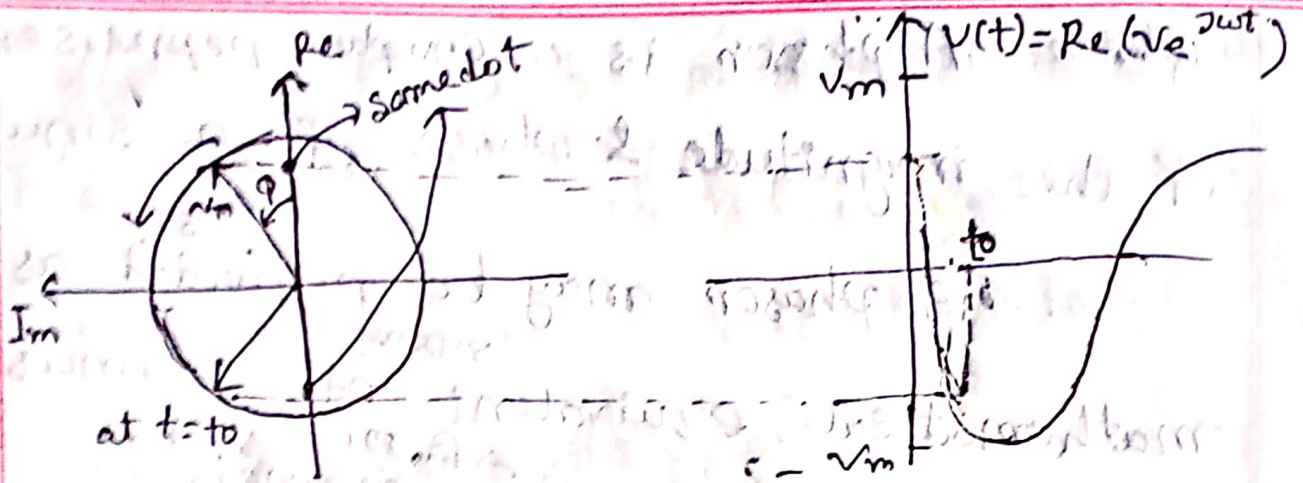


Figure: 9.7(b)

Description:-


$2\pi n t \rightarrow$ time

\rightarrow arrow

\rightarrow Frequency

Here arrow v_m is the rotating vector. And ω making a circle. That dot is going up & down. This dot is the projection of the tip of the arrow. This dot is going up & down in a sine wave pattern.

In sine wave:-

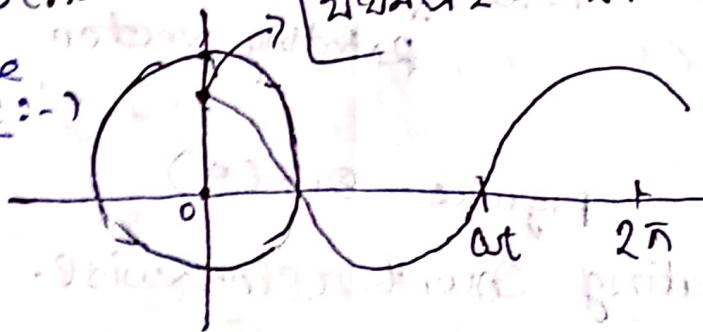


When this curve goes to zero then it is said as $\sin \omega t$

ଏହି ପ୍ରକାରରେ ଏହି ଚର୍ଚ୍ଚା ନାମା କରୁଥିବା ସାକ୍ଷ୍ୟରେ wave ଏବଂ ପରିଚ୍ଛେଦନ ହେବ ।

ଏ ଓ ପାରିବର୍ତ୍ତନ କରା


now in cosine wave;

Coswt

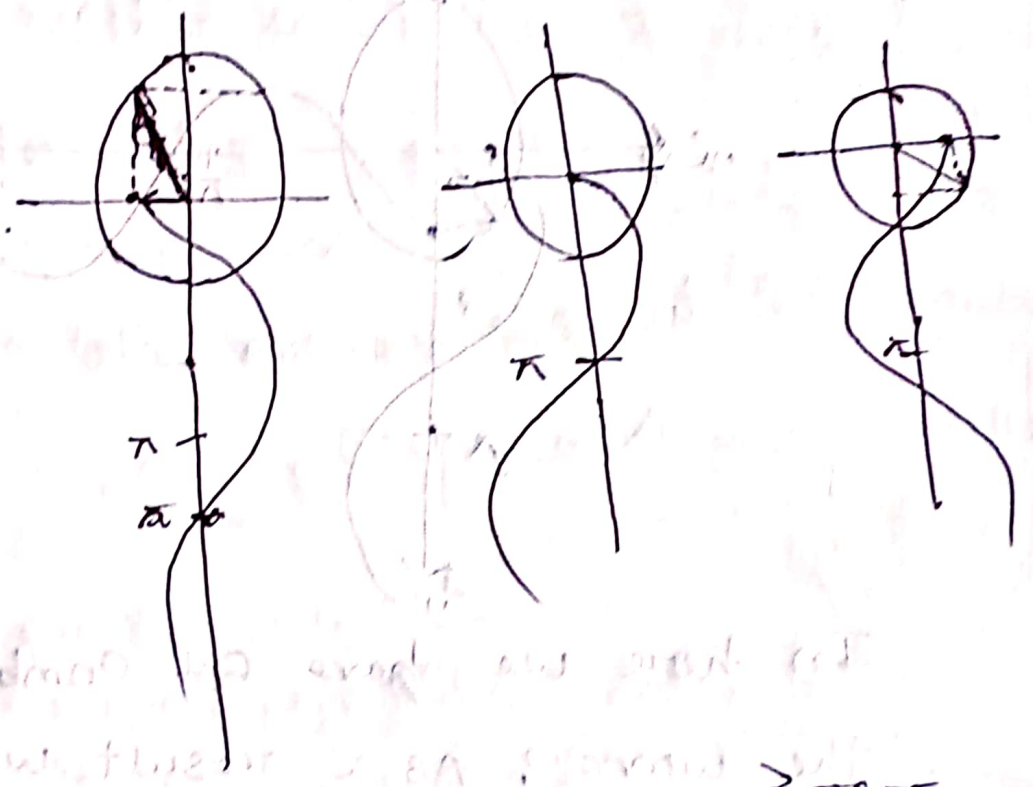

ଏ ଏହି Cosine wave ଠିକ୍ Cosine ଏବଂ ତାହା ସେଥିରୁ
 π axis ଏବଂ ଉପର ଦୃଶ୍ୟ ଖାଲି ଆପଣ
 ଠିକ୍ sine ଏବଂ ମାଧ୍ୟମ ଦୃଶ୍ୟ ଖାଲି ଏବଂ wave ଏବଂ
 ଠିକ୍ ଯାହା π ଉପର ଉପର ଏବଂ ମାଧ୍ୟମ
 ଏବଂ ଦୃଶ୍ୟ ଦେଖିବା ସମ୍ଭବ କରା ଥିବୁ ।

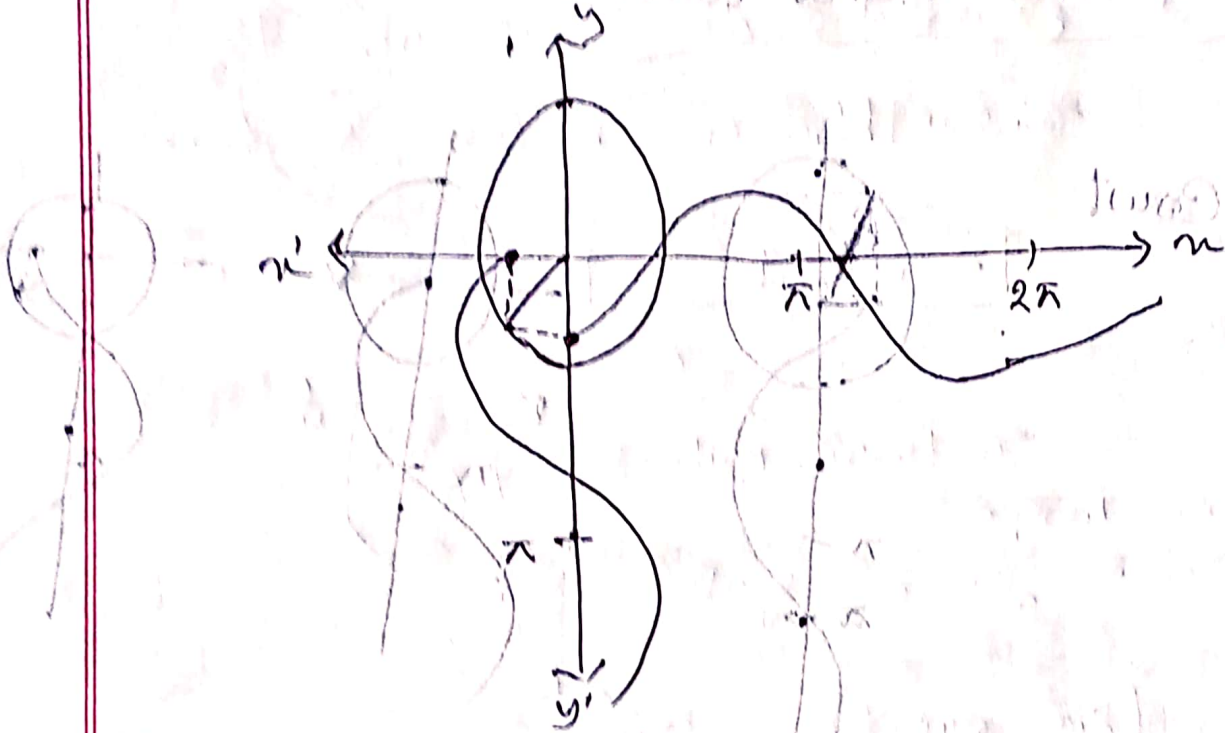If we combine both sine & cosine rotating vector then:-



In here we have not combined both of the wave. As a result we can see both are in their own axis. ~~sin~~ The dot of sin wave is in y axis and the dot of cos wave is in x axis. (It is good in 3D animation)

V is thus the phasor representation of the sinusoid $v(t)$

For figure \rightarrow 9.7(a,b)

• Equation, $v(t) = \text{Re}(V e^{j\omega t}) = V \cos \omega t$ on

the complex plane.

As time increases the vector rotates on a circle of radius V_m at an angular velocity ω in the counterclockwise direction

9.7(a)

we may regard (चित्र) $v(t)$ as the projection of the vector $V e^{j\omega t}$ on the real axis. 9.7(b)


The vector may be regarded as rotating phasor.

Thus, whenever a sinusoid is expressed as a phasor, the term $e^{j\omega t}$ is implicitly present.

When dealing with the phasors to keep in mind the frequency ω of the phasor.

Since a phasor has magnitude and ~~face~~ phase (direction) it behaves as a vector and is printed in boldface.

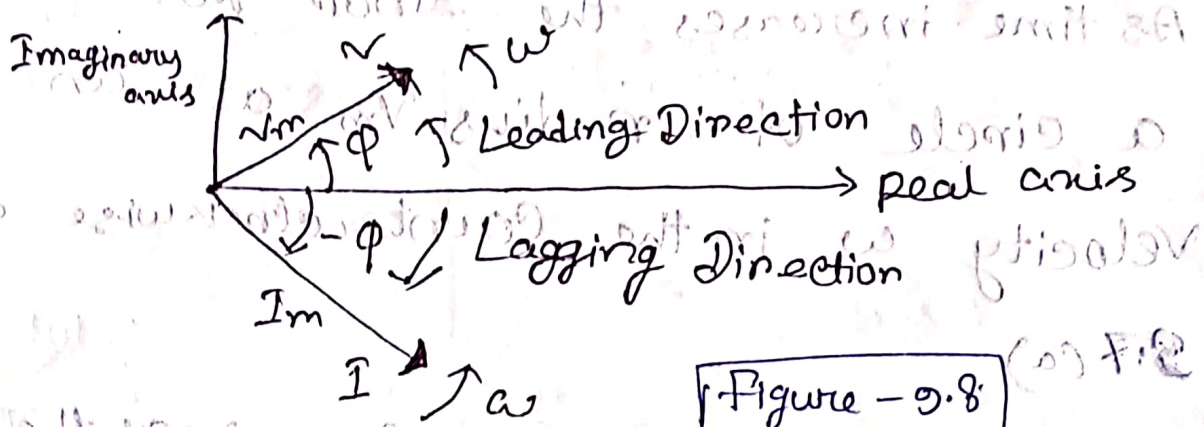So, $\mathbf{V} = V_m \angle \phi$ $\mathbf{I} = I_m \angle \phi$



So, Figure-9.8 a graphical representation of phasors is known as a phasor Diagram.

Lightface letters for complex numbers
and boldface letter for phasors

$$v(t) = V_m \cos(\omega t + \phi)$$

Time-Domain representation

$$\mathbf{V} = V_m \angle \phi$$

Phasor-domain representation

(9.25)

Time Domain representation Phasor D. Rep.

$$V_m \cos(\omega t + \phi) \longrightarrow V_m \angle \phi$$

$$V_m \sin(\omega t + \phi) \longrightarrow V_m \angle \phi - 90^\circ$$

$$I_m \cos(\omega t + \theta) \longrightarrow I_m \angle \theta$$

$$I_m \sin(\omega t + \theta) \longrightarrow I_m \angle \theta - 90^\circ$$

In here, we see that to get the phasor representation of a sinusoid we express it in cosine form to take the magnitude and phase.

The frequency (or time) factor $e^{j\omega t}$ is suppressed in (9.25) equation. The frequency is not explicitly shown in the phasor domain representation because ω is constant. As a result, the phasor domain is

$\omega = \text{frequency}$

$j = \sqrt{-1} \Rightarrow \text{Imaginary number}$

$V = \text{Phasor representation of a sinusoid}$

also known as the Frequency domain.

$$\Rightarrow \text{IF, } v(t) = v_m \sin(\omega t + \phi) = \text{Re}(v_m e^{j(\omega t + \phi)}) = v_m \cos(\omega t + \phi)$$

so that, $\frac{d}{dt} \sin(\omega t + \phi) = \omega \cos(\omega t + \phi)$

$$\frac{dv}{dt} = \omega v_m \cos(\omega t + \phi) = \omega v_m \cos(\omega t + \phi + 90^\circ)$$

$$= \text{Re}(\omega v_m e^{j\omega t} \cdot e^{j\phi} \cdot e^{j90^\circ})$$

$$= \text{Re}(j\omega v_m e^{j\omega t + j\phi})$$

Note:

$$\frac{d}{dt}(v) \Rightarrow j\omega V \quad (9.27)$$

(Time domain) (Phasor Domain)

* Diff. a sinusoid is equivalent to multiplying its corresponding phasor by $j\omega$

$$\int v dt \Rightarrow \frac{V}{j\omega} \quad (9.28)$$

(T. D.) (P. D.)

* Integrating a sinusoid is equivalent to dividing its corresponding phasor by $j\omega$

Difference between $v(t)$ & V

① $v(t)$ is the instantaneous or time domain representation.

V is the frequency or phasor domain representation.

② $v(t)$ is time dependent.

V is not dependent.

③ $v(t)$ is always real.
 V is generally complex.

note:- (A) This phasor actually used when frequency is constant.

It is used for manipulating two or more sinusoidal signals only if they are of the same frequency.

~~Handwritten scribbles~~

How to
Solve phasor's Mathematics

(i)

voltage, $v = \frac{170}{\text{amplitude}} \cos(377t - 40^\circ)$ [v]

$v = 170$



⇒ Phasor, $V = 170 \angle -40^\circ$ [v] unit
 $170 e^{-j40^\circ}$

(b) $i = 10 \sin(1000t + 20^\circ)$ (A)

$i = 10 \cos(1000t + 20^\circ - 90^\circ)$

Phasor, $V = 10 \angle -70^\circ$ [v]


~~Handwritten scribbles~~

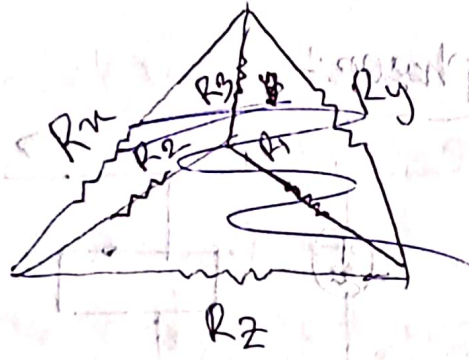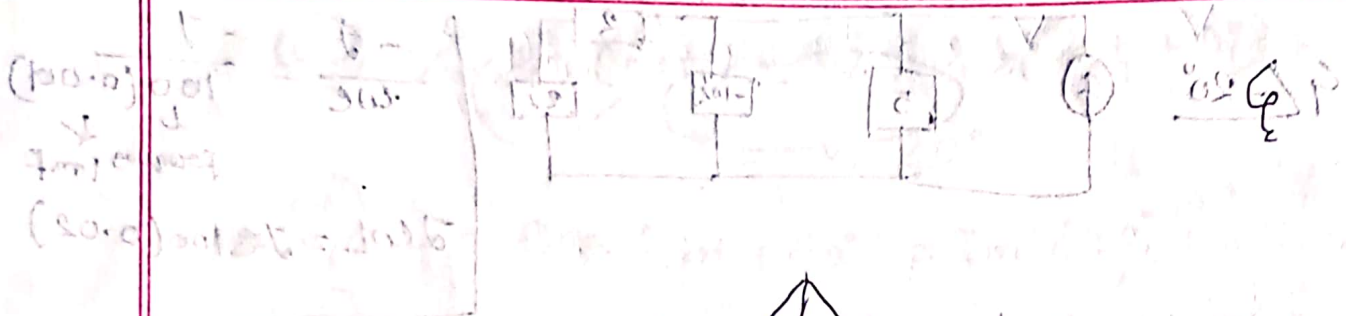

$$R_1 = \frac{R_y R_z}{R_x + R_y + R_z}$$


Extra math

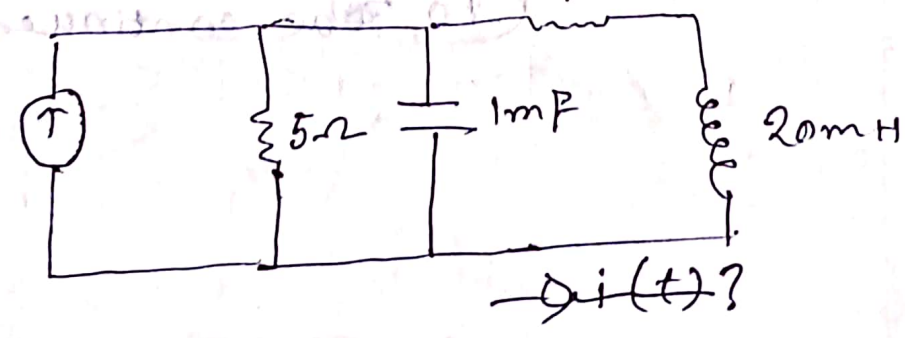$4 \cos(\omega t - 20^\circ) \text{ A.} \rightarrow i(t)?$
 2Ω



\Rightarrow Solve How to solve?

① Convert to phasor:-

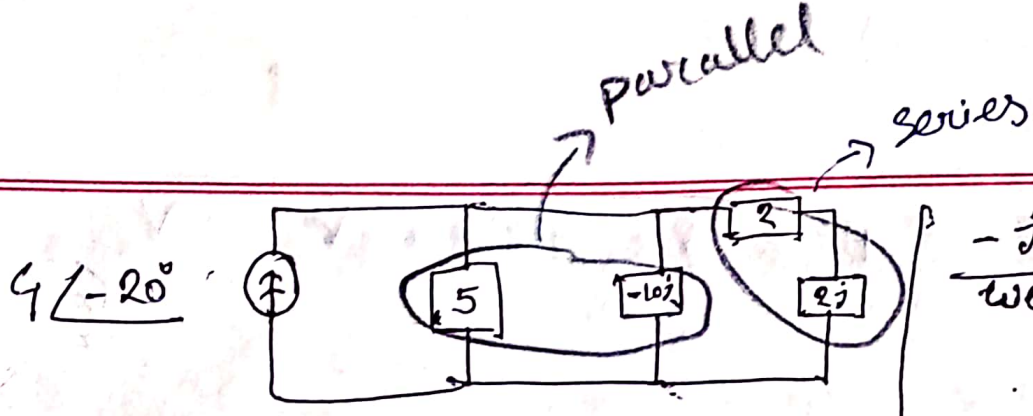


$$\frac{-j}{\omega C} = \frac{-j}{100(0.001)}$$

↓
frequency 1mF

$$j\omega L = j \times 100(0.02)$$


(2) Solve in phasor:-

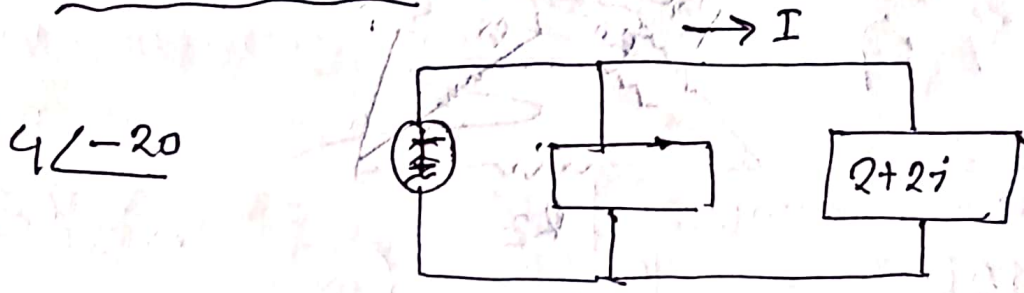

$$\frac{5(-j10)}{5 + j10}$$

$$= \frac{-50j}{5 + j10}$$

(To be continued)

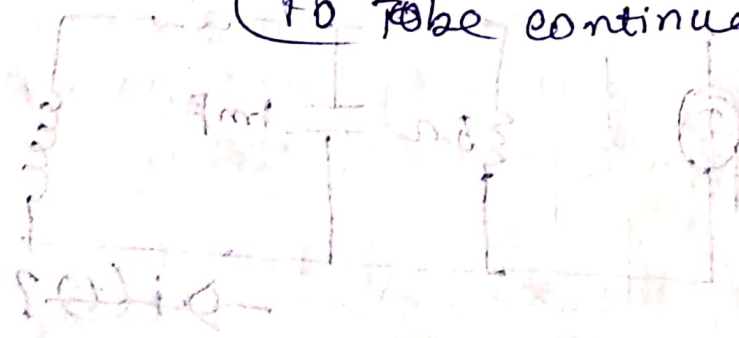

Solve from to solve (1)
ground or terminal (1)

Math Solution (A-2)

#Phasor

$$\textcircled{\pm} V_m \cos(\omega t) = V_m \cos(\omega t + 0^\circ) = V_m \angle 0^\circ$$


$$\textcircled{\pm} I_m \cos(\omega t + 30^\circ) = I_m \angle 30^\circ$$

$$\textcircled{\pm} V_m \sin(\omega t) = V_m \cos(\omega t - 90^\circ) = V_m \angle -90^\circ$$

$$\textcircled{\pm} V_m \sin(\omega t + 40^\circ) = V_m \cos(\omega t + 40^\circ - 90^\circ) = V_m \cos(\omega t - 50^\circ) = V_m \angle -50^\circ$$

$$\textcircled{\pm} 7 \cos(377t + 15^\circ) = 7 \angle 15^\circ \rightarrow \text{Phasor}$$

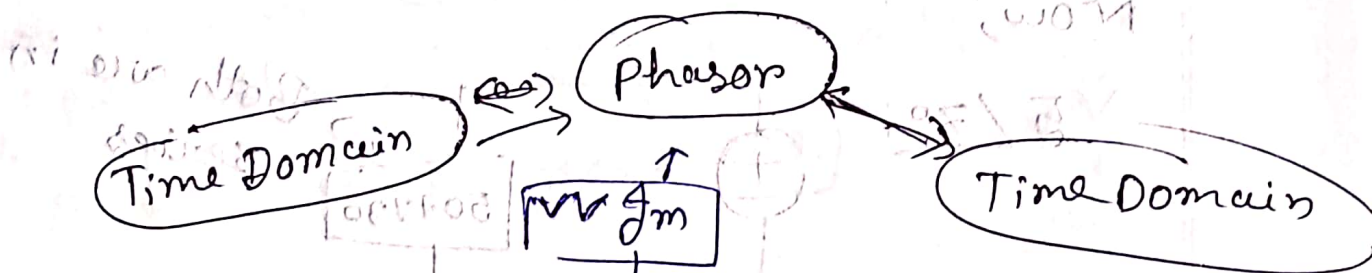Time domain, $i = 7(15^\circ) = 7 \cos(\omega t + 377t + 15^\circ)$



Resistance \Rightarrow $\frac{V}{R} \rightarrow$ Phasor $\frac{R}{j\omega}$

Capacitor \Rightarrow $\frac{1}{C} \rightarrow \frac{1}{j\omega C} = -\frac{j}{\omega C}$

Inductor \Rightarrow $L \rightarrow j\omega L$


(E-A) circuit diagram
 1000911-

$$20 \angle 0^\circ \frac{1}{j\omega C} = \frac{j}{j\omega C} = \frac{j}{j \cdot 10 \cdot 0.01} = \frac{j}{-j} = -1$$

$5 \cos(10t + 7^\circ)$

step

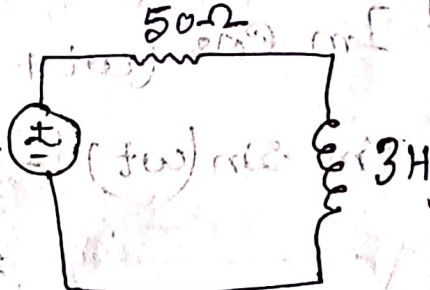① Convert from time domain \rightarrow phasor




$\omega =$

\rightarrow Henry


\rightarrow Henry

$\Rightarrow 5 \angle 7^\circ$

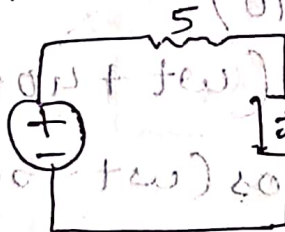

$$j\omega L = j \times 10 \times 3 = j30$$


Or, $5 \angle 7^\circ$

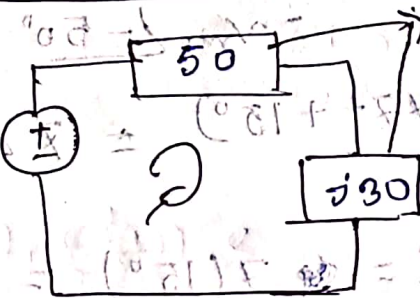

These two are Impedance

Now,

$5 \angle 7^\circ$

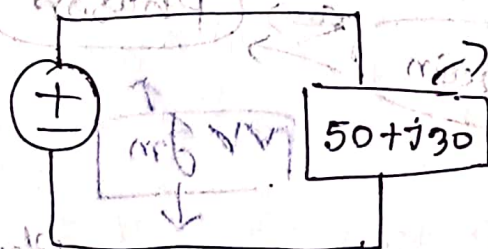

Both are in series

step ②

Solve in phasor!

$$V = I \cdot Z$$

$$\text{Or, } 5 \angle 7^\circ = I \cdot (50 + j30)$$

Polar for $r < \theta \Rightarrow$ কোন থাকবে

Rectangular Form

$j = 1 \angle 90^\circ$

অথবা i/j থাকবে না।
Date:

এ i থাকবে $/ j$ থাকবে

So, $I = \frac{5 \angle 7^\circ}{50 + j30} = 0.086 \angle -24^\circ$

Step-3

Convert from phasor \rightarrow time.

$I = 0.086 \angle -24^\circ \rightarrow \omega$ এর মান 10 তার

$i(t) = 0.086 \cos(10t - 24^\circ)$

Calculator এ সুকতার:-

3. Complex mode \rightarrow সমীকরণ তুলে \rightarrow Ans \rightarrow $\text{S} \Rightarrow$ D

To get in polar:-

Ans \rightarrow shift \rightarrow 2 \rightarrow 3 \rightarrow Ans \Rightarrow S \Rightarrow D

For complex number:-

press button i instead of j

To get the rectangular Form

Ans \rightarrow shift \rightarrow [2] \rightarrow [4] \rightarrow [=]

* If we press S \Rightarrow D we will get decimal form.

Form Form

Summary of voltage-current Relationship

Element	Time Domain	Frequency Domain
Resistance R	$v = Ri$	$V = RI$
Inductor L	$v = L \frac{di}{dt}$	$V = j\omega L I$
Capacitor C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

↓
(Math द्वारा कर शक्य है)

Impedance & Admittance

$$\frac{V}{I} = R ; \frac{V}{I} = j\omega L ; \frac{V}{I} = \frac{1}{j\omega C} \quad (9.39)$$

As all are three expressions, we obtain Ohm's law in phasor form for any type of element,

$$\boxed{Z = \frac{V}{I} \quad \text{or,} \quad V = ZI} \quad (9.40)$$

Where Z is a frequency-dependent quantity known as impedance, measured in ohms.

The impedance Z of a circuit is the ratio of the phasor voltage V to the phasor current I , measured in ohms (Ω)

Although the impedance is the ratio of two phasors, it is not a phasor, because it does not correspond to a sinusoidally varying quantity.

Impedance & admittances of passive elements: - (Table - 9.3)

Element \rightarrow Impedance \rightarrow Admittance

$$R \rightarrow Z = R \rightarrow Y = \frac{1}{R}$$

$$L \rightarrow Z = j\omega L \rightarrow Y = \frac{1}{j\omega L}$$

$$C \rightarrow Z = \frac{1}{j\omega C} \rightarrow Y = j\omega C$$

Although the impedance is the ratio of two phasors, it is not a phasor, because it does not correspond to a sinusoidally varying quantity.

From table (9.3) summarizes their impedances

From there we notice

$$Z_L = j\omega L$$

$$Z_C = -j/\omega C$$

An inductor acts like a short circuit & a capacitor acts like an open circuit.

when $\omega \rightarrow \infty$ ($Z_L \rightarrow \infty$ and $Z_C = 0$),

indicating that the inductor is an open circuit to high frequencies, while the capacitor is a short circuit.

Inductor \rightarrow Short circuit at DC

Capacitor \rightarrow Open circuit at high frequencies

Capacitor \rightarrow Open circuit at DC

Inductor \rightarrow Short circuit at high frequencies

As a complex quantity, the impedance may be expressed,

$$Z = R + jX \quad (9.41)$$

In polar form, $Z = |Z| \angle \theta \quad (9.42)$

$$Z = R + jX = |Z| \angle \theta \quad (9.43)$$

$$|Z| = \sqrt{R^2 + X^2} \quad ; \quad \theta = \tan^{-1} \frac{X}{R} \quad (9.44)$$

$$R = |Z| \cos \theta \quad ; \quad X = |Z| \sin \theta \quad (9.45)$$

The admittance Y of an element (or a circuit) is the ratio of the phasor current through it to the phasor voltage

$$Y = G + jB \quad (9.47)$$

where, $G = \text{Re } Y$ is called the conductance and $B = \text{Im } Y$ is called the susceptance.

B is the imaginary part of admittance, where the real part is conductance. The

reciprocal of admittance is impedance

where the imaginary part is reactance and real part is resistance.

Admittance, conductance and susceptance are all expressed in the unit of Siemens (or mhos).

$$G + jB = \frac{1}{R + jX} \quad (9.48)$$

$$(R+j\omega L)(R-j\omega L) = R^2 - (j\omega L)^2 = R^2 + \omega^2 L^2$$

By rationalization,

$$G + jB = \frac{1}{R + j\omega L} \cdot \frac{R - j\omega L}{R - j\omega L} = \frac{R - j\omega L}{R^2 + \omega^2 L^2} \quad \text{--- (9.49)}$$

Equating the real and imaginary parts gives,

$$G = \frac{R}{R^2 + \omega^2 L^2} \quad , \quad B = -\frac{\omega L}{R^2 + \omega^2 L^2} \quad \text{--- (9.5)}$$

Showing that $G \neq 1/R$ as it is in resistive circuits. Of course, if $\omega = 0$, then $G = 1/R$

Formula of Impedance :-

$$\textcircled{1} Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\textcircled{2} Z = R + \frac{1}{j\omega C}$$

voltage across the capacitor,

$$V = I Z_c = \frac{I}{j\omega C}$$

Z = impedance

R = Resistance

ωL = Inductive Reactance


$\frac{1}{\omega C}$ = Capacitive Reactance

ω = Frequency

C = Capacitance

Incomplete

Math :- Determine $v(t)$ and $i(t)$

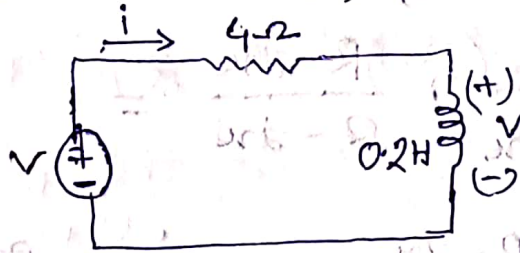

$$v_s = 20 \sin(10t + 30^\circ) \text{ V}$$

⇒ From the voltage source,

$$20 \sin(10t + 30^\circ)$$

$$\text{So, } \omega = 10 ; v_s = 20 \angle 30^\circ \text{ V}$$

The impedance is,

$$Z = R + \frac{1}{j\omega C} = 5 + \frac{1}{j \cdot 10 \cdot 0.2}$$

Kirchoff's Laws in the Frequency

(150.0) Domain $\rightarrow (v_1 + \dots + v_n)$

We cannot do circuit analysis in the frequency domain without Kirchoff's

Current and voltage laws. Therefore, we need to express them in the frequency domain.

For KVL let v_1, v_2, \dots, v_n be the voltage around a closed loop.

$$\text{Then, } v_1 + v_2 + \dots + v_n = 0 \quad \text{--- (9.51)}$$

In the sinusoidal steady state, each voltage may be written as in cosine form, so that equation (9.51) becomes,

$$v_{m1} \cos(\omega t + \theta_1) + v_{m2} \cos(\omega t + \theta_2) + \dots +$$

$$v_{mn} \cos(\omega t + \theta_n) = 0 \quad \text{--- (9.52)}$$

This can be written as,

$$\text{Re}[(v_{m1} e^{j\theta_1} + v_{m2} e^{j\theta_2} + \dots + v_{mn} e^{j\theta_n}) e^{j\omega t}] = 0 \quad \text{--- (9.53)}$$

If we let, $v_k = v_{mk} e^{j\omega t}$, then, then

$$\text{Re} [(v_1 + v_2 + \dots + v_n) e^{j\omega t}] = 0 \quad (9.54)$$

Since, $e^{j\omega t} \neq 0$,

$$v_1 + v_2 + \dots + v_n = 0 \quad (9.55)$$

If we let i_1, i_2, \dots, i_n be the current leaving or entering a closed surface in a network at time t , then

$$i_1 + i_2 + \dots + i_n = 0 \quad (9.56)$$

If these are the phasors form of the sinusoids then,

$$I_1 + I_2 + \dots + I_n = 0 \quad (9.57)$$

which Kirchoff's current law in the frequency domain.

As KVL, KCL holds in the frequency domain, it is easy to do many things, such as impedance combination, nodal and mesh analyses,


Impedances Combinations

N series connected impedances, the same current I flows through the impedances.

Applying KVL around the loop gives,

$$V = V_1 + V_2 + \dots + V_n$$
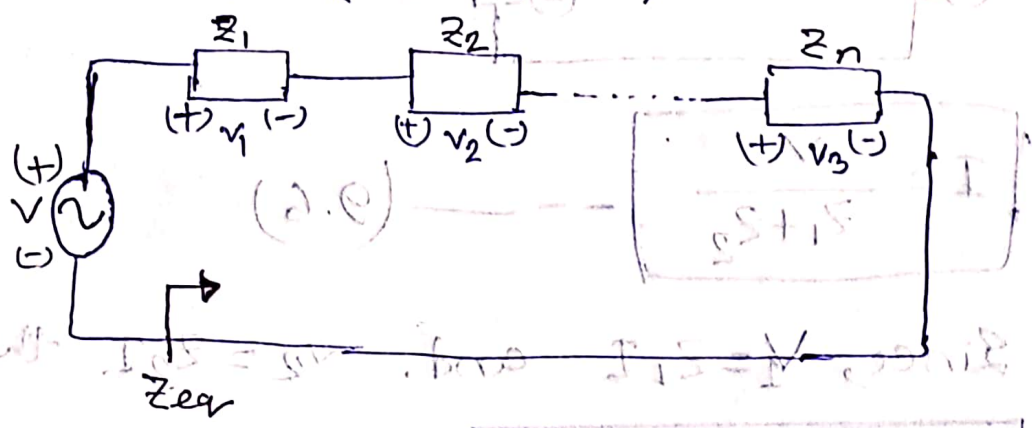
$$\equiv I(Z_1 + Z_2 + \dots + Z_n) \quad \text{--- (9.58)}$$




The equivalent impedances at the input terminal is,

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_n$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n \quad \text{--- (9.59)}$$

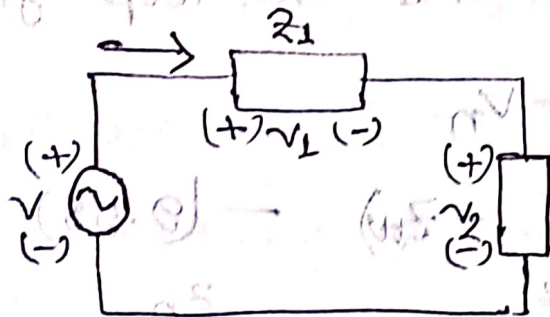The total or equivalent impedance of series connected impedances is the sum of the individual impedances. This is similar to the series connection of resistances.



$$I = \frac{V}{Z_1 + Z_2} \quad (9.6)$$

Since, $V_1 = Z_1 I$ and $V_2 = Z_2 I$ then,

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V$$

$$V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

which is the voltage division relationship.

In the same manner, we can

obtain the equivalent impedance or admittance of the N -parallel connected impedances shown in Fig. 9.2. The voltage across each ...

Lesson- AC circuits


..... [After Notebook-1]

impedance Z_A is the same. Applying KCL at the top node,

$$I = I_1 + I_2 + \dots + I_n$$

$$= V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \right) \quad (9.62)$$

N - impedances in parallel :-

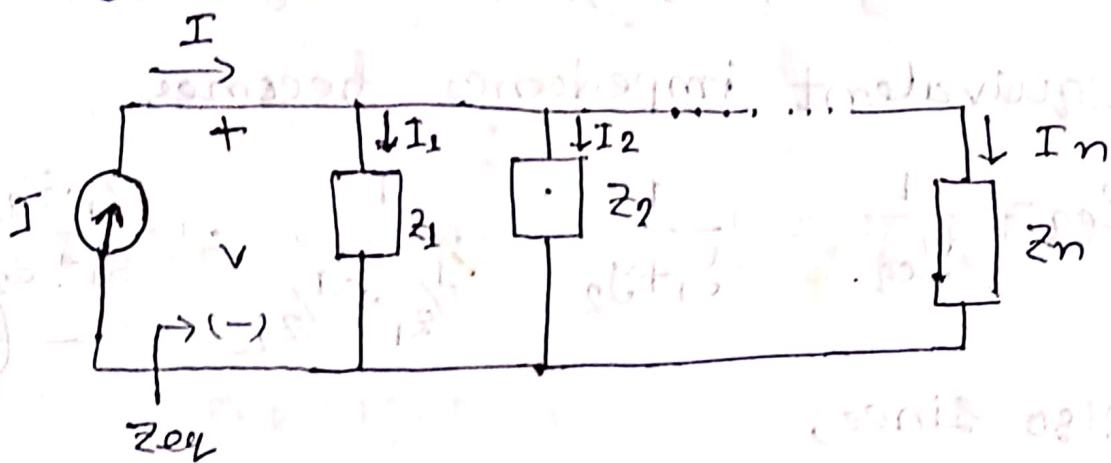


The equivalent impedance is,

$$\frac{1}{Z_{eq}} = \frac{1}{V} = \frac{1}{V Z_1} + \frac{1}{V Z_2} + \dots + \frac{1}{V Z_n} \quad (9.63)$$

and the equivalent admittance is,

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_n \quad (9.64)$$

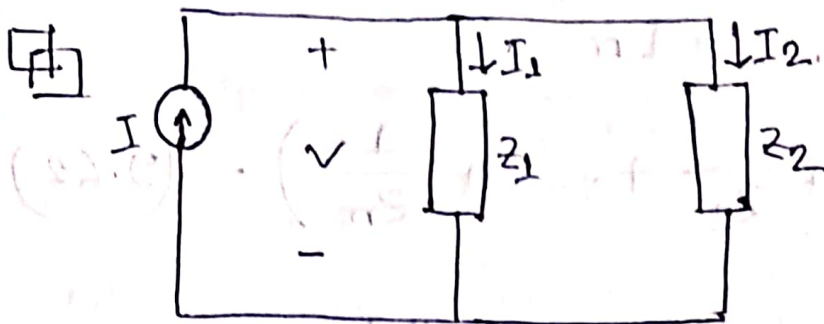This indicates that the equivalent admittance of a parallel connection of admittances is the sum of the individual admittances.



When $N=2$, as shown in Figure, the equivalent impedance becomes,

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} \quad (9.65)$$

Also since,

$$V = I Z_{eq} = I_1 Z_1 = I_2 Z_2$$

the currents in the impedances are,

$$I_1 = \frac{Z_2}{Z_1 + Z_2} \cdot I$$

$$I_2 = \frac{Z_1}{Z_1 + Z_2} \cdot I$$

(9.66)

which is the current-division principle.
 The delta-to-ye and ye-to-delta trans-
 formations that we applied to resistive
 circuits are also valid for impedances.
 With reference to Fig (9.22) the conversion
 formulas are as follows.

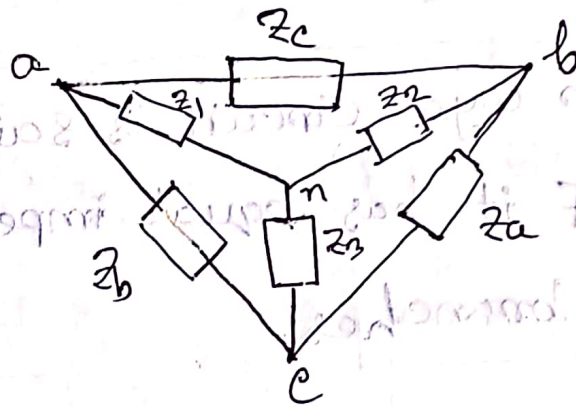


Figure - 9.22 (Superimposed Y and Δ networks).

Y-Δ conversion:-

$$1. Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$2. Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$3. Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

7 Δ -Y conversion:

$$1) Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$2) Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$3) Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

* A delta or wye circuit is said to be balanced if it has equal impedances in all three branches.

When a Δ -Y circuit is balanced,

Equation (9.67) and (9.68) become,

$$Z_\Delta = 3Z_Y \quad \text{or} \quad Z_Y = \frac{1}{3} Z_\Delta \quad - (9.69)$$

where, $Z_Y = Z_1 = Z_2 = Z_3$

and, $Z_\Delta = Z_a = Z_b = Z_c$


Applications:-

9.8.1

Phase Shifters:-

A phase-shifting circuit is often employed to correct an undesirable phase shift already present in a circuit or to produce special desired effects.

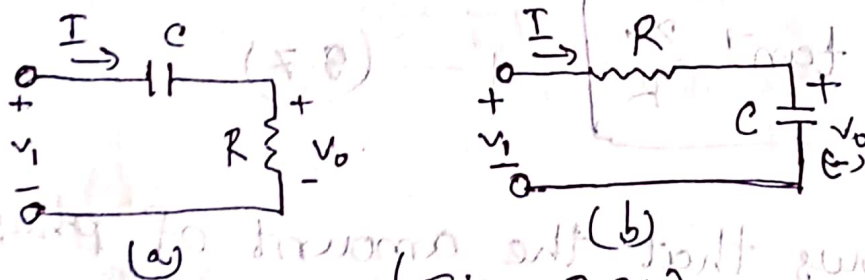An RC circuit is suitable for this purpose



(Fig → 9.31)

because its capacitor causes the circuit current to lead the applied voltage.

Two commonly used RC circuits are shown

in Figure 9.31. (RL circuits or any reactive

circuits could also serve the same purpose).

(9.1) (a) The circuit current I leads the applied voltage v_i by some phase angle θ ,

where $0 < \theta < 90^\circ$, depending on the values of R and C .

If $X_c = -1/\omega C$,


then the total impedance is $Z = R + jX_c$

and the phase shift is given by,

$$\theta = \tan^{-1} \frac{X_c}{R} \quad (9.7)$$

This shows that the amount of phase shift depends on the values of R , C , and the operating frequency. Since the output voltage v_o across the resistor is in phase with the current, v_o leads (positive phase shift) v_i .

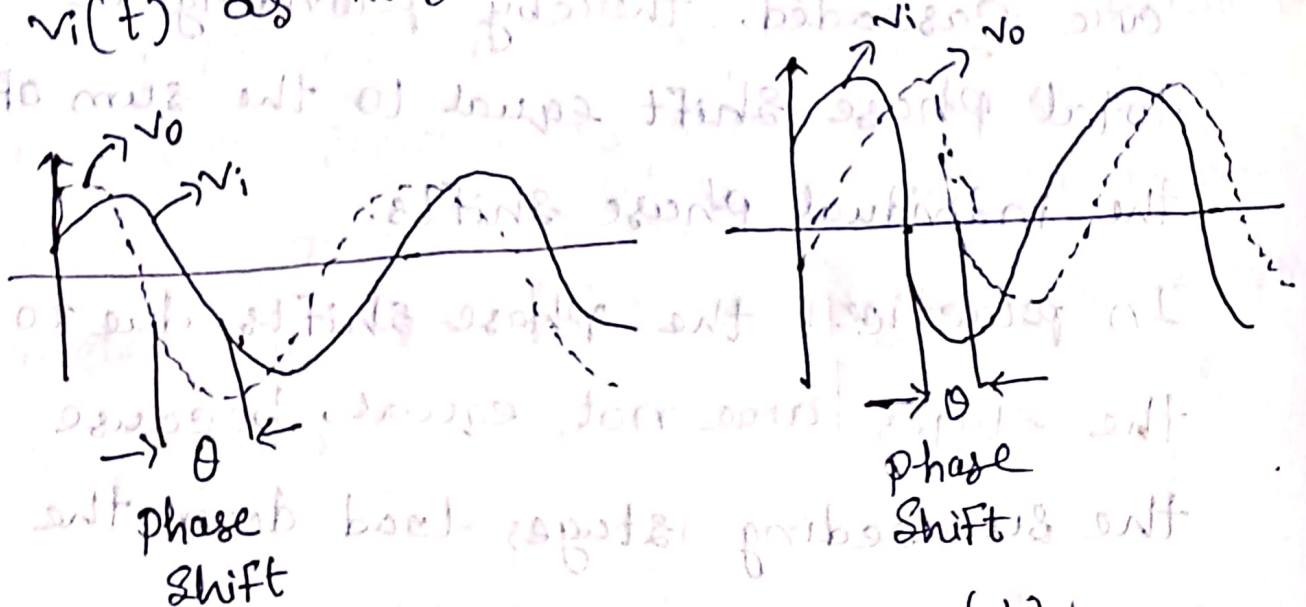9.31(b)!- The output is taken across the capacitor. The current I leads the input voltage v_i by θ , but the output voltage $v_o(t)$ across the capacitor lags (negative phase shift) the input voltage $v_i(t)$ as illustrated below!-



(a)

(b)

We should keep in mind that the simple RC circuits in Fig (9.31) also act as voltage dividers.

As the phase shift θ approaches 90° , the

Output voltage v_o approaches zero. For this reason, these simple RC circuits are used only when small amounts of phase shift are required.

If it is desired to have phase shifts greater than 60° , simple RC networks are cascaded, thereby providing a total phase shift equal to the sum of the individual phase shifts.

In practice, the phase shifts due to the stages are not equal, because the succeeding stages load down the earlier stages unless op amps are used to separate the stages.



9.8.2 (AC Bridges) :-

An AC bridge circuit is used in measuring the inductance L of an inductor or the capacitance C of a capacitor.

It is similar in form to the wheatstone bridge for measuring an unknown resistance and follows the same principle. To measure L and C , however, an ac source is needed as well as an ac meter instead of the galvanometer. The ac meter may be a sensitive ac ammeter or voltmeter.

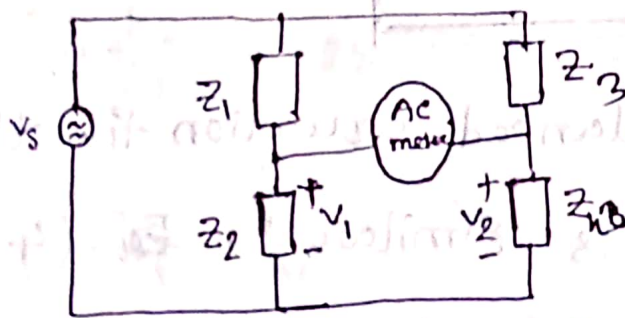


Figure: 9.37 (A general ac bridge)

Consider the general ac bridge circuit displayed in (Fig. 9.37). The bridge is

balanced when no current flows through the meter. This means that $V_1 = V_2$.

Applying the voltage division principle,

$$V_1 = \frac{Z_2}{Z_1 + Z_2} \cdot V_s = V_2 = \frac{Z_x}{Z_3 + Z_x} \cdot V_s \quad (9.71)$$

Thus,

$$\frac{Z_2}{Z_1 + Z_2} = \frac{Z_x}{Z_3 + Z_x}$$

$$\Rightarrow Z_2 Z_3 = Z_1 Z_x \quad (9.72)$$

or,
$$Z_x = \frac{Z_3}{Z_1} \cdot Z_2$$



This is the balanced equation for the ac bridge and is similar to Eq. (4.30) for the resistance bridge except that the R's are replaced by Z's.

Specific, ac bridges for measuring L and C are shown in Figure (9.38), where L_x and C_x are the unknown inductance and capacitance to be measured, while L_s and C_s are a standard inductance and capacitance (the value of which are known to great precision). In each case, two resistors R_1 and R_2 are varied until the ac meter reads zero. Then the bridge is balanced.

From Eq. (9.73) we obtain,

$$L_x = \frac{R_2}{R_1} L_s \quad (9.74)$$
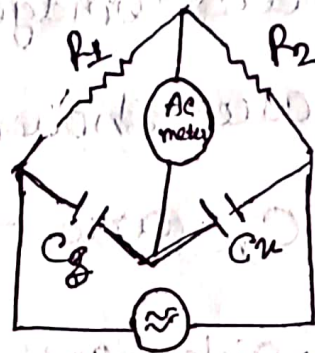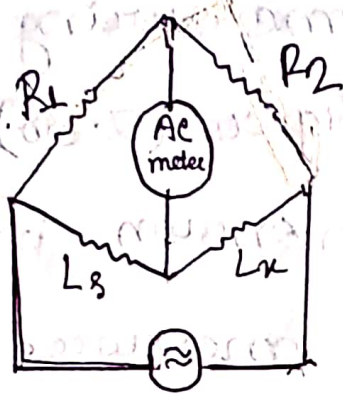
$$\text{and, } C_s = \frac{R_1}{R_2} C_x \quad (9.75)$$



(a) Fig-9.38. (b)

The ~~blan~~ (Specific ac bridges: (a) for measuring L
 (b) for measuring C .)

The balancing of the ac bridges in Fig (9.38) does not depend on the frequency f of the ac source. Since f does not appear in the relationships in Eqs (9.74) and (9.75)

(9.74)

Summary

1. A Sinusoid is a signal in the form of the sine or cosine function. It has the general form,

$$v(t) = V_m \cos(\omega t + \phi)$$

Where V_m is the amplitude, $\omega = 2\pi f$ is the angular frequency, $(\omega t + \phi)$ is the argument and ϕ is the phase.

2. A phasor is a complex quantity that represents both the magnitude and the phase of a sinusoid. Given the sinusoid,

$$v(t) = V_m \cos(\omega t + \phi)$$

its phasor V is,

$$V = V_m \angle \phi$$

3. In ac circuits, voltage and current phasors always have a fixed relation to

to one another. At any moment of time. If $v(t) = V_m \cos(\omega t + \phi)$ represents its phasor V is, the current through the $Z = V_m \angle \phi$ element, then $\phi_i = \phi_v$.

if the element is a resistor, ϕ_i leads ϕ_v by 90° if the element is a capacitor, and ϕ_i lags ϕ_v by 90° if the element is a capacitor, and ϕ_i lags ϕ_v by 90° if the element is an inductor.

Q. The impedance Z of a circuit is the ratio of the phasor voltage across it to the phasor (current) through it :-

$$Z = \frac{V}{I} = R(\omega) + jX(\omega)$$

The admittance Y is the reciprocal of impedance :-

$$Y = \frac{1}{Z} = G(\omega) + jB(\omega)$$

Impedances are combined in series or in parallel in the same way as resistances in series or parallel; that is, impedances in series add while admittances in parallel add.

5] For a resistor, $Z = R$ For an inductor

$$Z = jX = j\omega L, \text{ and for a Capacitor}$$

$$Z = -jX = 1/j\omega C$$

6] Basic circuit laws (Ohm's and Kirchhoff's) apply to ac circuits in the same manner as they do for dc circuits, that

is,

$$V = ZI$$

$$\sum I_k = 0 \text{ (KCL)}$$

$$\sum V_k = 0 \text{ (KVL)}$$

7] The techniques of voltage/current division, series/parallel combination of impedance/admittance, circuit reduction, and $Y-\Delta$ transformation, all apply to ac circuit analysis.

8] AC circuits are applied in phase-shifters and bridges.

Math of Phasor & AC Circuit will be after lesson-116-5

Lesson-11

AC Power Analysis

11.1 :-

Introduction :-

$$(i) \cdot (V) = (P)$$

power analysis is of paramount importance. Power is the most important quantity in electric utilities, electric and communication systems, because such systems involve transmission of power from one point to another. Also every industrial and household device has a power rating that indicates how much power the equipment requires. The most common form of electric power is 50 or 60 Hz ac power. The choice of ac over dc allowed high-voltage power transmission from the power generating plant to the consumer.

11.2 :-

Instantaneous and Average power :-

$$P(t) = v(t) \cdot i(t)$$

The instantaneous power $p(t)$ absorbed by an element is the product of the instantaneous voltage $v(t)$ across the element and the instantaneous current $i(t)$ through it. Assuming the passive sign convention:

* The instantaneous power (in watts) is the power at any instant of time.

It is the rate at which an element absorbs energy. Consider the general case of instantaneous power absorbed by an arbitrary combination of circuit elements under sinusoidal excitation.

$$v(t) = V_m \cos(\omega t + \theta_v) \quad \text{--- (11.2a)}$$

$$i(t) = I_m \cos(\omega t + \theta_i) \quad \text{--- (11.2b)}$$

Here,

V_m & I_m = ~~The~~ amplitudes (or, peak values)

θ_v & θ_i = The phase angles of the voltage and current.

The instantaneous power absorbed by the circuit is :-

$$P(t) = v(t) \cdot i(t)$$

$$= V_m I_m \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$$

If we apply trigonometric identity,

$$\cos A \cdot \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)] \quad \text{--- (11.4)}$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

(11.5)


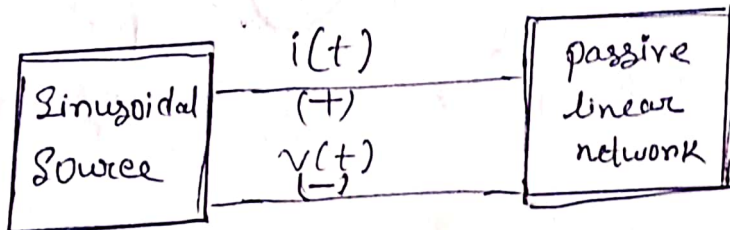


Figure: 11.1

This shows us that the instantaneous power has two parts. The first part is constant or time independent. Its value depends on the phase difference between the voltage and the current.

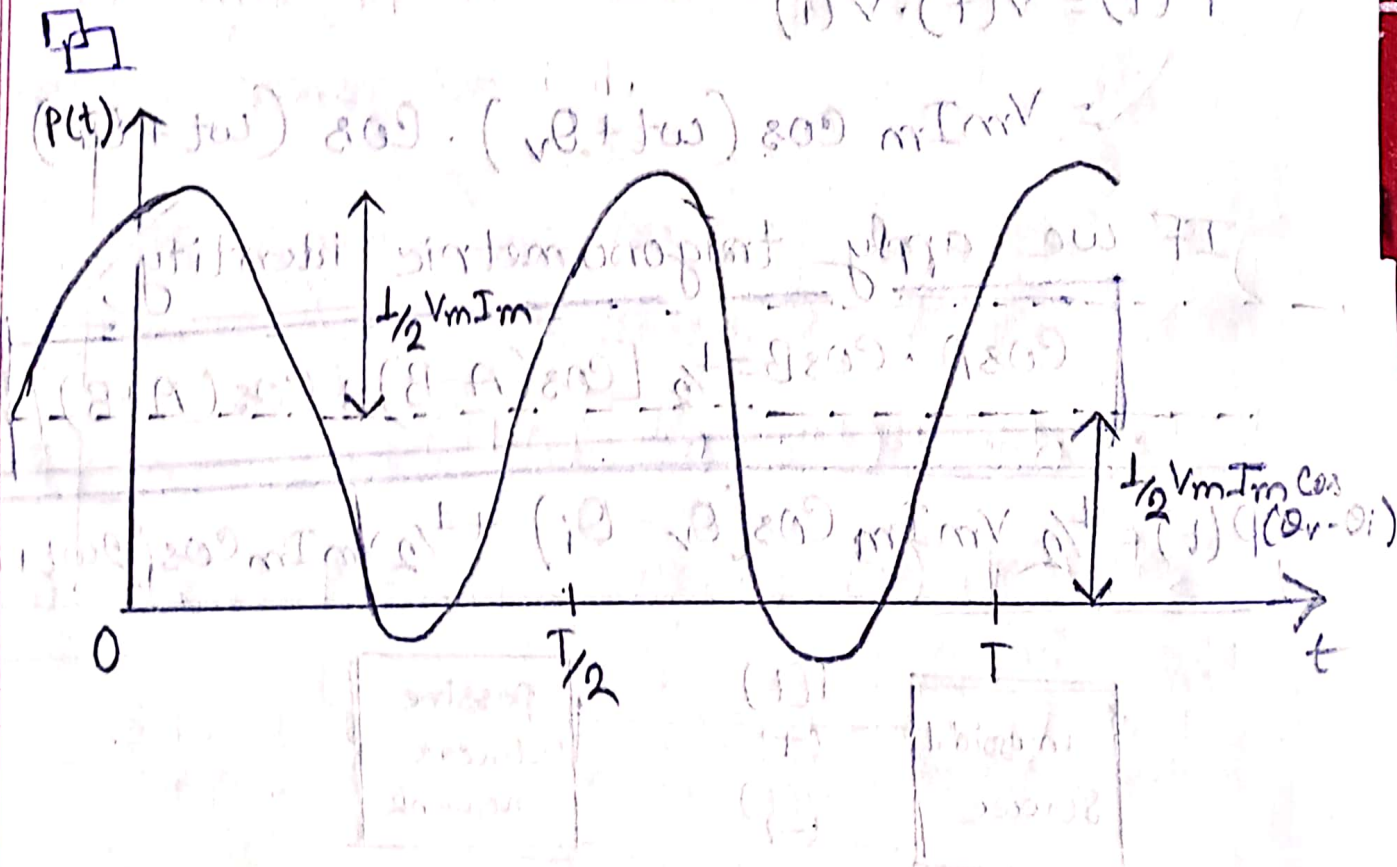The second part is a sinusoidal function whose frequency is 2ω , which is twice the angular frequency of the voltage or current.



Here, $T = 2\pi/\omega$ which is the period of voltage or current. We observe that $p(t)$

is periodic, $p(t) = p(t + T_0)$ & has a period of $T_0 = T/2$.

Since its frequency is twice that of voltage or current.

We also observe that $p(t)$ is positive for some part of each cycle and negative for the rest of the cycle.

When $p(t)$ is positive, power is absorbed by the circuit. When negative, power is absorbed by the source.

That is, the power is transferred from the circuit to the source.

This is possible because of the storage elements (capacitors and inductors) in the circuit.

The instantaneous power changes with time and is therefore difficult to measure.

The average power is more convenient (सुविधिकरण) to measure.

In fact, the wattmeter, the instrument for measuring power, responds to average power.

⊛ The average power, in watts, is the average of the instantaneous power over one period.

$$\text{The average power, } P = \frac{1}{T} \int_0^T p(t) dt \quad (11.6)$$

If we apply (11.6) on $p(t)$ which is $T_0 = T/2$,

$$P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt + \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt \quad \text{--- (11.7)}$$

The first integrand is constant, and the average of a constant is the same constant.

The second integrand is a sine sinusoid. We know that the average of a sinusoid over its period is zero because the area under the sinusoid during a positive half cycle is canceled by the area under it during the following negative half-cycle.

As the second term in (Eq 11.7) vanishes and the average power becomes,

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \text{--- (11.8)}$$

Since, $\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v)$, what is important is the difference in the phases of the voltage and current.

$P(t)$ is time varying while P doesn't depend on time.

To find the instantaneous power, we must necessarily have $v(t)$ and $i(t)$ in the time domain. But we can find the average power when voltage and current are expressed in the time domain as in eq(11.8) or when they are expressed in the time domain. Frequency domain.

The phasor forms of $v(t)$ and $i(t)$,

$$V = V_m \angle \theta_v \quad \text{and} \quad I = I_m \angle \theta_i \quad \text{respectively.}$$

P is calculated using eq(11.8) or using phasors V and I .

To use phasors,

$$\begin{aligned} \frac{1}{2} VI^* &= \frac{1}{2} V_m I_m \angle \theta_v - \theta_i \\ &= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)] \end{aligned} \quad (11.9)$$

We recognize the real part of this expression as the average power, P , according to Equation (11.8). Thus,

$$\begin{aligned}
 P &= \frac{1}{2} \operatorname{Re}[V I^*] \\
 &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \text{--- (11.10)}
 \end{aligned}$$

Consider two special cases (eqn 11.10) A (A)

When $\theta_v = \theta_i$, the voltage and current are in phase. This implies a purely resistive circuit or resistive load R ,

$$\begin{aligned}
 P &= \frac{1}{2} V_m I_m \\
 &= \frac{1}{2} I_m^2 R \\
 &= \frac{1}{2} |I|^2 R \quad \text{--- (11.11)}
 \end{aligned}$$

where $|I|^2 = I \times I^*$.

Equation (11.11) shows that a purely resistive

Circuit or resistive load R , absorbs power at all times. When $\theta_v - \theta_i = \pm 90^\circ$, we have a purely reactive circuit, and

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

(*) A resistive load (R) absorbs power at all times, ~~while a~~ ~~reactive~~

(*) A reactive load (L or C) absorbs zero average power.

$$P = \frac{1}{2} V_m I_m \cos \theta$$


Lesson

Resonance (तुलना)

Electrical resonance occurs in an electric circuit at a particular resonant frequency when the impedances or admittances of circuit elements cancel each other. In some circuits, this happens when the impedance between the input and output of the circuit is almost zero and the transfer function is close to one.

Series Resonance Circuit:-

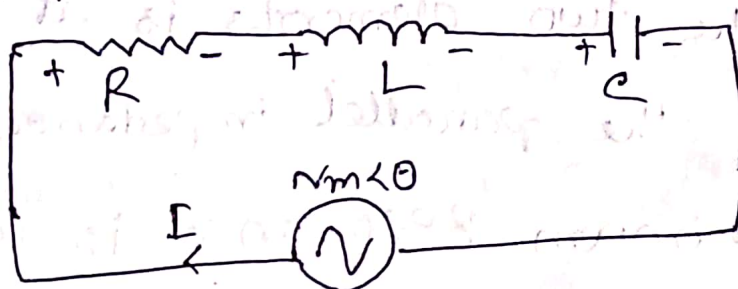Resonance occurs in a series circuit when the supply frequency causes the voltages across L and C to be equal and opposite in phase.



LC circuit:-

Resonance of a circuit involving capacitors and inductors occurs because the

collapsing magnetic field of the inductor

generates an electric current in its windings and charges the capacitor, and

then the discharging capacitor provides

an electric current that builds the magnetic field in the inductor. This

process is repeated ~~successfully~~ continuously.

An analogy is a mechanical pendulum,

and both are a form of simple

harmonic oscillator.

At resonance, the series impedance

of the two elements is at a minimum

and the parallel impedance is at

maximum. Resonance is used for

tuning and filtering, because it occurs at a particular frequency for given values of inductance and capacitance.

parallel resonance:-

parallel resonance or near-to-resonance circuits can be used to prevent the waste of electrical energy, which would

otherwise occur while the inductor built its field or capacitor charged and discharged.

Example:-

Asynchronous motors waste inductive

current while synchronous ones waste

capacitive current.

The use of the two types in parallel makes the inductor feed the capacitor

maintaining the same resonant current in the circuit, and converting all the current into useful.

Formula:-

$$\omega L = \frac{1}{\omega C}$$

$$\text{So, } \omega = \frac{1}{\sqrt{LC}}$$

where, $\omega = 2\pi F$

in which F is the resonance frequency in hertz, $L =$ Inductance henries, $C =$ Farads,

Quality Factor:-

The quality of the resonance

(how long it will ring when excited) is determined by its Q Factor (A function of resistance) :-

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

An idealized lossless LC circuit has infinite Q ,

but all actual circuits have some resistance and finite Q , and are usually approximated more realistically by an RLC circuit.

RLC/CILR Circuit :-

An electrical circuit consisting of a resistor, an inductor, and a capacitor connected in series or in parallel.

The circuit forms a harmonic oscillator for current and resonates similarly to an LC circuit.

There are many applications of this circuit. It is used in many different types of oscillator circuits. An important application is for tuning, such as in radio receivers or television sets, where

they are used to select a narrow range of frequencies from the ambient radio waves. In this role, the circuit is often referred to as a tuned circuit. An RLC circuit can be used as a passive filter.

Passive Filters:-

These passive filters are made up of passive components such as resistors, capacitors and inductors and have no amplifying elements (~~transistors~~, op-amps, etc) so have no signal gain, therefore their output level is always less than the input.

Types of passive filters :-


1) Low pass filters:-

A low-pass filter is a filter that passes signals with a frequency lower


than a certain cutoff frequency and attenuates signals with frequencies higher than the cut-off frequency.

The frequency between the pass-and-stop bands is called the cut-off frequency.

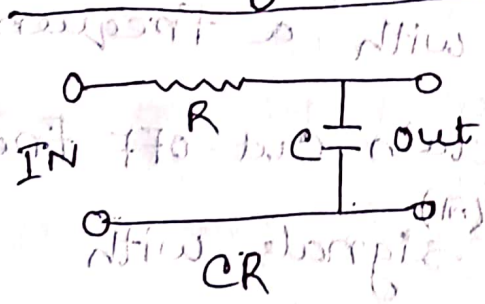
It is used to remove high frequency signals and allow through low frequency signals.




RC-Low pass Filter

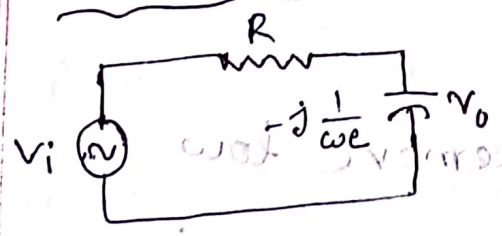
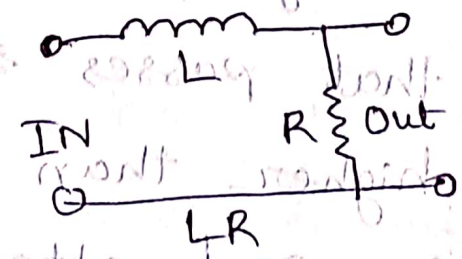
$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$



RL - Low pass Filter

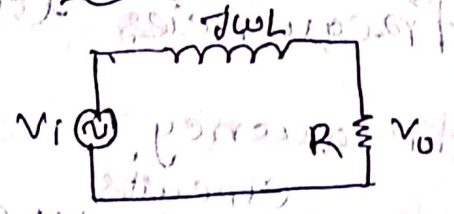

$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega L/R}$$

$$\frac{|V_o|}{|V_i|} = \frac{1}{[1 + (\omega RC)^2]^{1/2}}$$

$$\theta = -\tan^{-1} \omega RC$$

At cutoff Frequency

$$\text{gain} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{RC}$$

$$\frac{|V_o|}{|V_i|} = \frac{1}{[1 + (\omega \frac{L}{R})^2]^{1/2}}$$

$$\theta = -\tan^{-1} \omega \frac{L}{R}$$


$$\omega_c = \frac{R}{L}$$

High pass Filters :-

A high pass filter is an electronic filter that passes signals with a frequency higher than a certain cut-off frequency and attenuates signals with frequencies lower than the cut-off frequency.

These circuits are used to remove low frequency signals and allow high frequency signals.

RC - High pass Filter

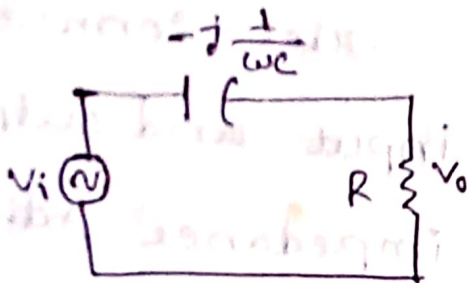


$$\frac{v_o}{v_i} = \frac{\omega RC}{\omega RC - j1}$$

$$\theta = \tan^{-1} \frac{1}{\omega RC}$$

$$\omega_c = \frac{1}{RC}$$

RL - High pass Filter

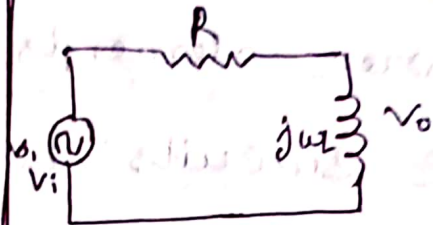

$$\frac{v_o}{v_i} = \frac{\omega L/R}{\omega L/R - j1}$$

$$\theta = \tan^{-1} \frac{R}{\omega L}$$

Acutoff gain = $1/\sqrt{2}$

$$\omega_c = \frac{R}{L}$$


• They are used to remove or attenuate the lower frequencies in amplifiers.

Band pass Filters


Band pass filters allow only a required band of frequencies to pass, while rejecting signals at all frequencies above and below this band. It is also

Called as a T Filter. It consists three elements, two series-connected LC circuits between input and output which form a low impedance path to signals of the required frequency but have a high impedance to all other frequencies.

~~By Bus stop~~

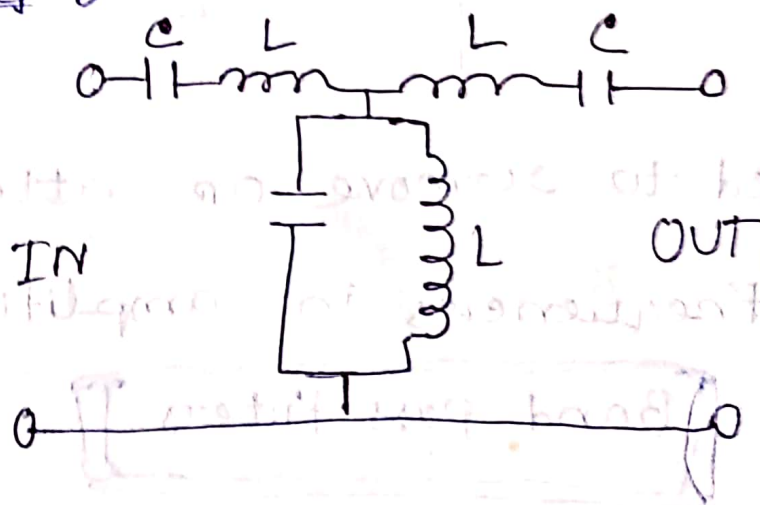

Band Stop Filters

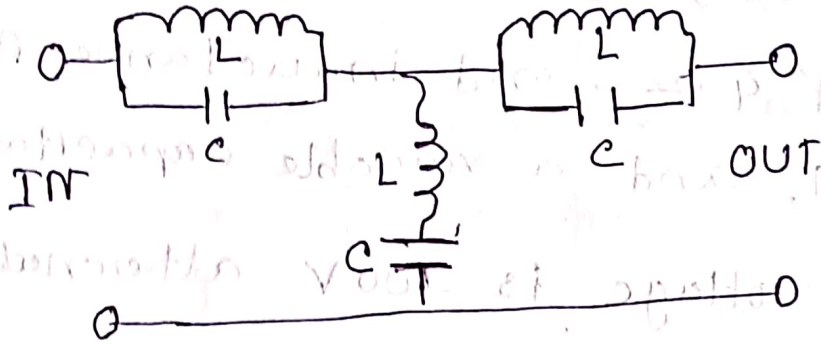

=> These filters have the opposite effect to band pass filters.

There are two parallel LC circuits in the signal path to form high impedance at the unwanted signal frequency, and a series circuit forming a low impedance path to ground at the same frequency, to add the rejection.

Math

□ A series RLC circuit has resistance of $4\ \Omega$, and inductance of $500\ \text{mH}$, and a variable capacitance. Supply voltage is $100\ \text{V}$ alternating

at $50\ \text{Hz}$. At resonance $X_L = X_C$.

The capacitance required to give series resonance is calculated as:

⇒ Here,

$$X_C = X_L = 2\pi fL = 2\pi \times 50 \times 0.5\ \text{H}$$

$$= 157.1\ \Omega$$

$$\therefore C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 157.1}$$

$$= 2.03 \times 10^{-5}\ \text{F.}$$

Resonance voltages across the inductor and the capacitor, V_L and V_C will be,

$$V_L = I \times Z = \frac{V}{Z} = \frac{100 \text{ V}}{4 \Omega} = 25 \text{ A.}$$

Now,

$$V_L = V_C = I \times L = 25 \text{ A} \times 157.1 \Omega$$

$$= 3.93 \times 10^3$$

$$= 3927.5 \text{ V}$$

(Ans)

From this math,
when the series RLC circuit is
at resonance, the magnitudes of the
voltages across the inductor and

capacitor can become many times larger
than the supply voltage.

Tuned circuit:-

An LC circuit also called a resonant
circuit, tank circuit, or tuned circuit,
is an electric circuit consisting of
an inductor, represented by the letter L,
connected together.

Lesson

polyphase System

A polyphase system is a means of distributing alternating-current electrical power where the power transfer is constant during each electrical cycle.

Polyphase systems have three or more energized electrical conductors carrying alternating currents with a defined phase angle between the voltage waves in each conductor.

This system is useful for transmitting power to electric motors which rely alternating current to rotate.

Three phase power system is the most common example used for industrial applications and for power transmission.

Three phase balanced System

The electrical system is of two types, the single-phase system and the three phase system.

The single-phase system has only one phase wire and one return wire thus it is used for low power transmission.

The three-phase system has three live wires and one return path. The three-phase system is used for transmitting a large amount of power.

This 3 phased system is divided mainly into two types.

- 1) ~~One~~ Balanced three-phase system.
- 2) unbalanced three-phase system.

Balanced 3-phase Circuit.

The balance system is one in which the load are equally distributed in all the three phases of the system.

Analysis of Balanced 3 phase circuit:

It is always better to solve the balanced three phase circuits on the basis of each phase.

To solve the balanced three-phase circuits:

1. Draw the circuit Diagram.
2. Determine $X_{LP} = X_L / \text{phase} = 2\pi FL$
3. Determine $X_{CP} = X_C / \text{phase} = 1 / 2\pi FC$
4. Determine $X_p = X / \text{phase} = X_L - X_C$
5. Determine $Z_p = Z / \text{phase} = \sqrt{R_p^2 + X_p^2}$
6. Determine, $\cos \phi = R_p / Z_p$

[The power factor is lagging when $X_{LP} > X_{CP}$
The power factor is leading when $X_{CP} > X_{LP}$

7] Determine V_{phase} ,
[For star connection, $V_p = V_L / \sqrt{3}$ and for
delta connection, $V_p = V_L$]

8] Determine $I_p = V_p / Z_p$

9] Determine the line current I_L

For star connection;

$$I_L = I_p$$

For Delta connection;

$$I_L = \sqrt{3} I_p$$

10] Determine the Active, Reactive and
Apparent power.

Unbalanced 3-phase System

The load is connected either as star or



Delta. In a three-phase AC generator,

there are three windings. Each winding
has two terminals. (Start & Finish)

* An unbalanced system is due to unbalanced
voltage sources or an unbalanced load.

There are two basic three-phase configurations: wye (γ) and delta (Δ).

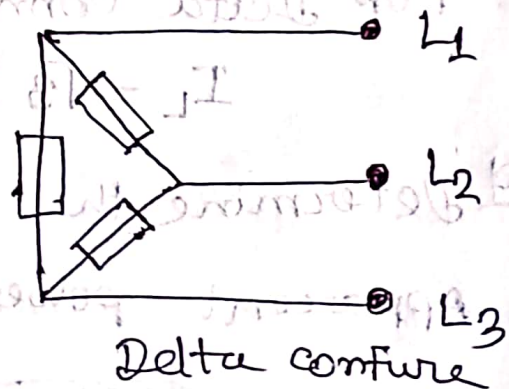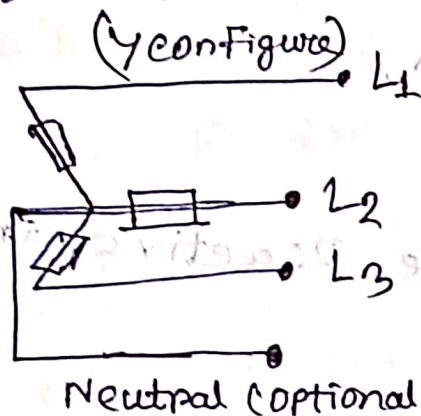A delta (Δ) configuration requires only three wires for transmission but a wye (star) configuration may have a fourth wire. The fourth wire, is provided as a neutral and is normally grounded.




Generally, there are four different types of three-phase transformer winding connections for transmission and distribution purposes.

It consists of a balanced
 Δ-Connected source Feeding
 a balanced Y-Connected source

- Wye (Y) - Wye (Y) is used for small current and high voltage. It is a three phase system with a balanced Y-connected source and balanced Y-connected load
- Delta (Δ) - Delta (Δ) is used for large currents and low voltages. Both balanced source and balanced load are Δ-connected
- Delta (Δ) - Wye (Y) is used for step-up transformers at generating stations.
- Wye (Y) - Delta (Δ) is used for step-down transformers, at the end of the transmission.

Y-Connected source
 Feeding a balanced
 Δ-Connected load

Y-Y System:-

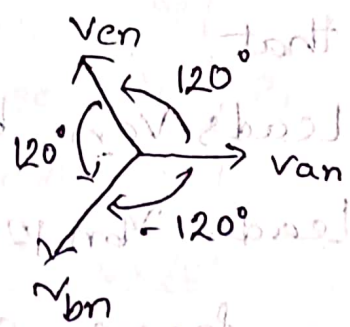

$$V_{an} + V_{bn} + V_{cn} = 0$$

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

Balanced phase voltages are equal in magnitude and are out of phase with each other by 120°.



$$V_{an} = V_p \angle 0^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$

$$V_{bn} = V_p \angle -120^\circ = V_p \angle +120^\circ$$

*) Determine the phase sequence of the set of

voltages, $V_{an} = 200 \cos(\omega t + 10^\circ)$

$$V_{bn} = 200 \cos(\omega t - 230^\circ)$$

$$V_{cn} = 200 \cos(\omega t - 110^\circ)$$

\Rightarrow The voltages can be expressed in phasor form as,

$$V_{an} = 200 \angle 10^\circ \text{ V}; V_{bn} = 200 \angle -230^\circ \text{ V}; V_{cn} = 200 \angle -110^\circ$$

We notice that,

V_{an} leads V_{cn} by 120° and V_{cn}

in turn leads V_{bn} 120° .

Hence, we have a acb sequence.

Summary of phase and line voltages/currents

For balanced three-phase systems :-

Connection	Phase voltages / currents	Line voltages / currents
1] Δ - Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Same as line current	$V_{ab} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{ab} / Z_L$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
2] Δ - Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB} / Z_L$ $I_{BC} = V_{BC} / Z_L$ $I_{CA} = V_{CA} / Z_L$	$V_{ab} = V_{AB} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$ (Same as phase voltages)
3] Δ - Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = V_{ab} / Z_L$ $I_{BC} = V_{bc} / Z_L$ $I_{CA} = V_{ca} / Z_L$	$I_a = I_{AB} \sqrt{3} \angle -30^\circ$ Same as phase voltage, $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

$$\Delta - Y \rightarrow V_{ab} = V_p \angle 0^\circ$$

$$V_{bc} = V_p \angle -120^\circ$$

$$V_{ca} = V_p \angle +120^\circ$$

Same as line
current

Same as phase
voltages:

$$I_a = \frac{V_p \angle -30^\circ}{\sqrt{3} Z_Y}$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

Lesson -

Machine Basics

\Rightarrow An electrical machine is a device that can convert either mechanical energy to electrical energy (generator) or electrical energy to mechanical energy (motor). Since any electrical machine can convert power in either direction, any machine can be used as either a generator or a motor.

Principle of generator and motor:-

Generator is a machine that converts mechanical energy into electrical energy. Based on the principle of Faraday's law of ~~electr~~ electromagnetic induction.

The principle of an electrical motor is based on the magnetic effect of electric current. A current carrying loop experiences a force and rotates when placed in a magnetic field. The direction of rotation of the loop is according to the Fleming's left-hand rule.

Significance of back e.m.f:-

When something like a refrigerator or an air conditioner (anything with a motor)

First turns on, & the light often dim momentarily.

To understand this, realize that a spinning motor also acts like a generator. A motor has coils turning inside a magnetic field, and a coil turning inside a magnetic field induces an emf.

This emf, known as the back emf, acts against the applied voltage that's causing the motor to spin in the first place, and reduces the current flowing through the coils of the motor.

At the motor's operating system, enough current flows to overcome any losses due to friction and other sources and to provide the necessary energy required for the motor to do work.

This is generally much less than the current that is required to get the motor spinning in the first place.

Here,

$$I = \frac{DV}{R}$$

$I =$ Initial current

$DV =$ Applied voltage

$R =$ Resistance.

[A device drawing that much current reduces the voltage and current provided to other electrical equipment in your house, causing lights to dim.]

When the motor is spinning and generating a back emf e , the current is reduced to:-

$$I = \frac{(DV - e)}{R}$$

$$\left[\text{Back, emf} = e \right]$$

[It takes very little time for the motor to reach operating speed and for the current to drop from its high initial value. This is

Why the lights dim only briefly?

When the motor starts, it draws a large current from the supply.

This causes a voltage drop in the supply lines.

The voltage drop is only for a short time.

As the motor reaches its normal speed, the current drawn is much less.

The voltage drop also disappears.

The lights return to their normal brightness.

The dimming is only a momentary phenomenon.

It is due to the inrush current at the start of the motor.

The inrush current is several times the normal current.

This is because the motor is initially at rest.

As it starts to rotate, the back EMF is induced.

This back EMF opposes the applied voltage.

Therefore, the current drawn decreases.

The voltage drop also disappears.

The lights return to their normal brightness.

The dimming is only a momentary phenomenon.

It is due to the inrush current at the start of the motor.

The inrush current is several times the normal current.

This is because the motor is initially at rest.


As it starts to rotate, the back EMF is induced.

This back EMF opposes the applied voltage.

Therefore, the current drawn decreases.

The voltage drop also disappears.

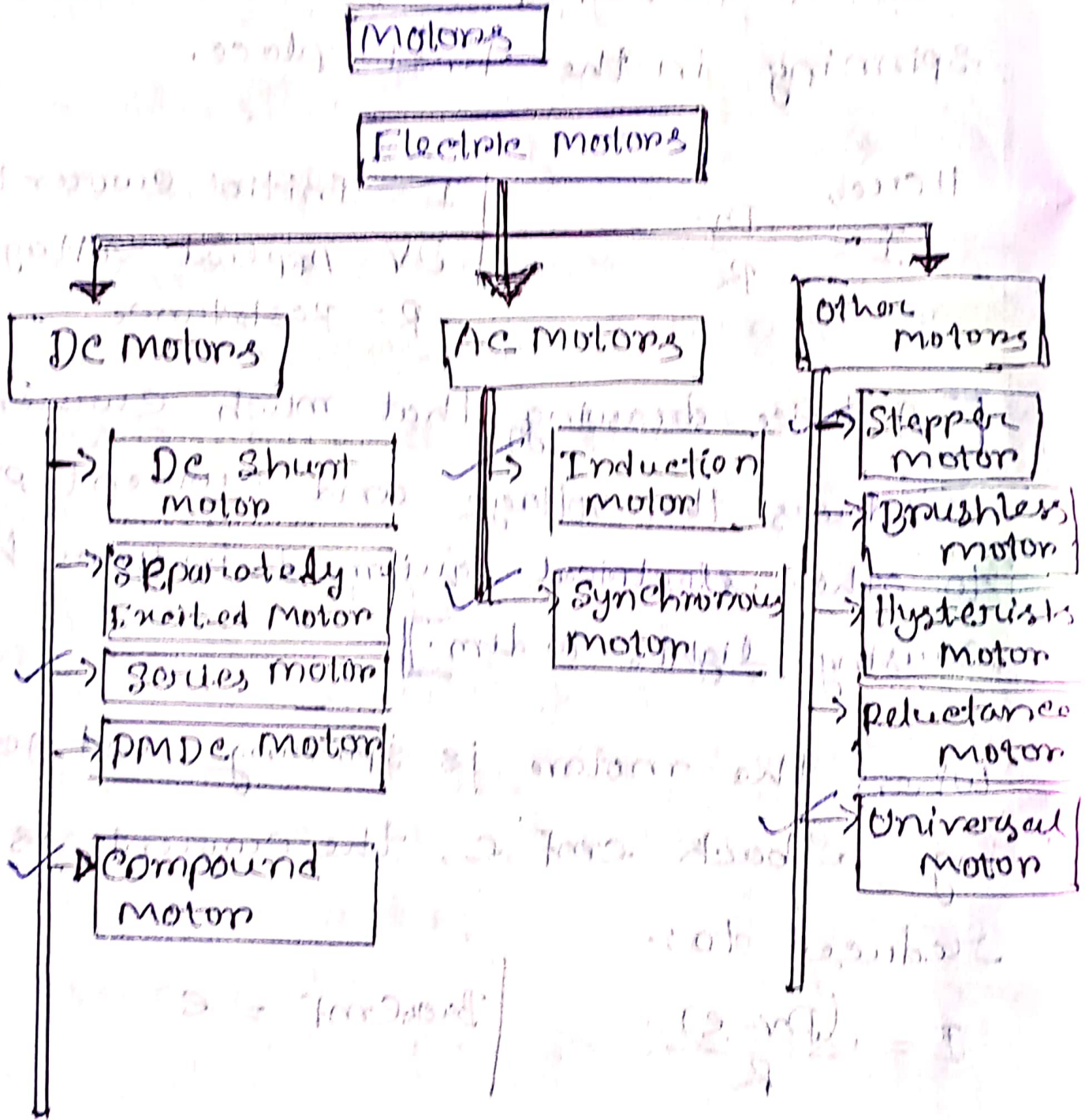The lights return to their normal brightness.



DC motors

DC motors can be powered by batteries, motor vehicles or rectifiers.

Series motors:-

In DC series motor, rotor windings are connected & in series. The operation principle of this electric motor mainly depends on a simple electromagnetic law.

The law is, whenever a magnetic field can be formed around conductor & interacts with an external field to generate the rotational motion. These motors are mainly used in starter motors which are used in elevators and cars.

De Compound motor :-

De motor is a hybrid component of De series and shunt motors. In this type of motor, both the fields like series and shunt are present.

In this type of electric motor, the stator and rotor can be connected to each other through a series & shunt windings compound.

This series winding can be designed with few windings of wide copper wires, which gives a small resistance path.

The shunt winding can be designed with multiple windings of copper wire to get the full i/p voltage.

AC motors

AC motors are powered by power grid, inverters, electrical generators.

Synchronous motor:-

The working of the synchronous motor mainly depends on the 3-phase supply. The stator in the electric motor generates the field current which rotates in a stable speed based on the AC frequency.

As well as the rotor depends on the similar speed of the stator current.

There is no air gap among the speed of stator current and rotor.

When the rotation accuracy level is high, then these motors are applicable in automation, robotics etc.

2) Induction Motor:-

The electric motor which runs asynchronous speed is known as induction motor, and an alternate name of

this motor is the asynchronous motor.

Induction motor mainly uses electromagnetic induction for changing

the energy from electric to mechanical.

Based on the rotor construction, these

motors are classified into two types

namely squirrel cage & phase wound.

Special purpose motors.

Stepper motor:-

The stepper motor can be used to offer step angle revolution, as an alternative to stable revolution. We know that for any motor, the whole revolution angle is 360 degrees. However, in a stepper motor, the complete revolution angle can be separated in numerous steps like 10 degree $\times 18$ steps. This means, in a total revolution cycle the motor will go stepwise eighteen times, every time 10 degree.

It is used in plotters, circuit fabrication, process control tools, usual movement generators etc.

Universal motor :-

This is a special kind of motor and this motor works on single AC supply otherwise DC supply.

Universal motors are series wound where the field and armature windings are connected in series and thus generates high starting torque.

These motors are mainly designed for operating at high-speed above 3500 rpm.


They utilize AC supply at low-speed and DC supply of similar voltage.

Thyristor :-

A Thyristor is a solid-state semiconductor device with four layers of alternating p- and N-type materials.

Thyristors are mainly used where high currents and voltages are involved, and are often used to control alternating currents, where the change of polarity of the current causes the device to switch off automatically, referred to as zero cross operation. It also used as the control elements for phase angle triggered controllers. This ~~is~~ use is being used for decades as light dimmers in

TV, motion pictures, theater,

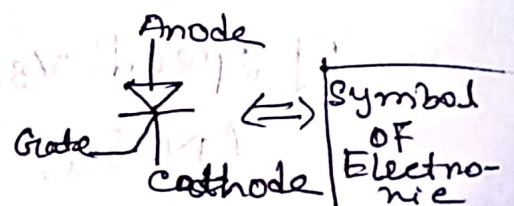

Torque - speed characteristics of Shunt

Shunt motor:-

A DC Shunt motor (also known as a shunt wound DC motor) is a type of self excited DC motor where the field windings are shunted to or are connected in parallel in armature winding of the motor.

Since, they are connected in parallel, the armature and field windings are exposed to the same supply voltage.

The three important shunt characteristic curves are:-

- 1] Torque vs Armature Current Characteristic (T_a/I_a)
- 2] Speed vs Armature Current Characteristic (N/I_a)

3] Speed vs Torque characteristic (N/T_a)

=>


Torque vs Armature Current Characteristic

Stie:-

We know that in DC motor $T_a \propto \Phi I_a$.

In this the Flux Φ is continuous, by ignoring the armature reaction,

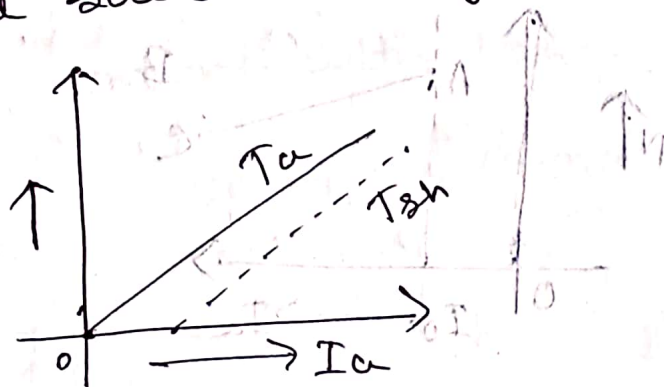
since the motor is working from a continual source voltage



This graph between Torque vs armature current is a straight line transitory through the origin which is shown in figure. The shaft torque (T_{sh}) is a

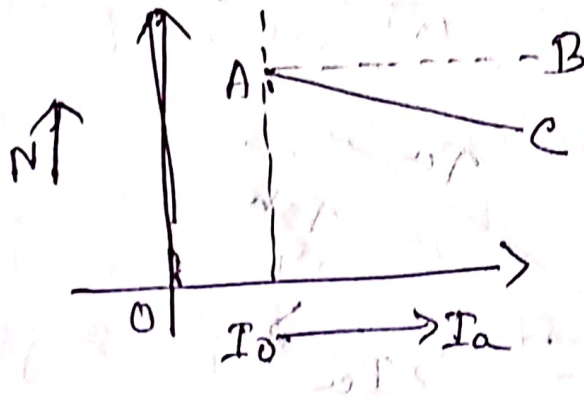(iii) smaller amount than armature torque and is shown in the figure by a dotted line. From this curve it is proved that to start a heavy load very large current is requisite. Hence, the shunt DC motor shouldn't be started at full load.

Speed vs Armature current characteristics




At normal condition the back emf E_b and Flux ϕ both are constant in a DC shunt motor. Hence, the armature current differs and the speed of a

DC shunt motor will continue to run at a constant speed which is shown in figure (line AB). Whenever, the shunt motor load is increased, $E_b = V - I_a R_a$ and flux reduces as a result drop in the armature resistance and armature reaction.

On the other hand, back emf reduces marginally more than that the speed of the shunt motor decreases to some extent with load.

Speed vs Armature Torque

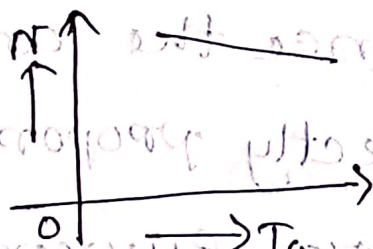

This curve is drawn between the speed of the motor and armature current

with various amps as shown in

Figure.

From the curve it is understood, that the speed reduces when the load torque increases.

So, we can say from all three

characteristics that,

when the shunt motor runs from no loads to full load there is slight change in speed.

Thus, it is essentially a constant speed motor, runs from no load

to full load since the armature

torque is directly proportional

to the armature current, the

starting torque is not high

Extra

1] Rotor:-

Rotor is a moving component of an electromagnetic system in the electric motor, electric generator, or alternator. Its rotation is due to the interaction between the windings and magnetic fields which produces a torque around rotor's axis.



Con: - Rotor

2] Armature:-

An armature is the component of an electric machine which carries alternating current.

The armature winding conduct AC even on DC machines, due to the commutator action (which periodically reverses

current direction) or due to electronic commutation, as in Brushless DC motor.



Armature.

Difference between Rotor & Armature:-

A rotor is the rotating part in AC motors whilst an armature is the rotating part in DC motors.

A rotor has no commutator


bars but an armature has commutator bars which carry current from the supplier to the windings.

Commutator:-

A commutator is a rotary electrical switch in certain types of electrical motors and electrical generators that periodically

reverses the current direction between the rotor and the external circuit.

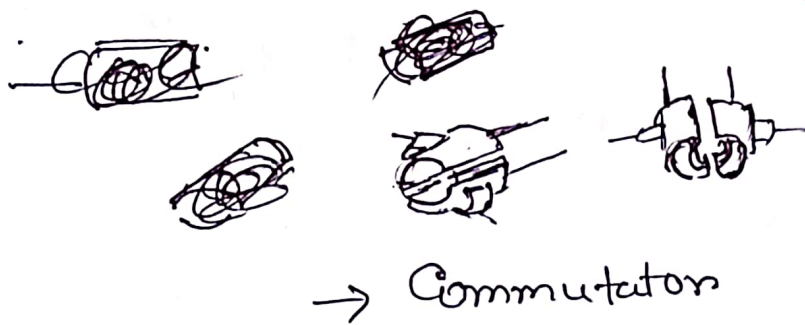It also used for insure that the current flowing through the rotor windings is always in the same direction. And the proper coil on the stator is energized in respect to the field coils.



windings in electrical motors :-

The electric motor winding definition is windings in electric motors are wires that are placed within coils, generally enclosed around a coated flexible iron magnetic core to shape magnetic poles while strengthened

with the current.

Generally, these are power driven with electromagnetic induction.



→ Coil windings



→ Commutator

The electrical motor winding

definition is winding in electric motor

are tubes that are placed within coils

generally enclosed around a central

flexible iron core magnetic circuit

of one magnetic pole while stationary